

CMP 334 (2/25/19)

HW 6 (unsigned binary subtraction)

Signed binary arithmetic (introduction)

TOY assembly language

Other ALU ops: **sub, and, nor**

Combinational circuit design process

1 bit full adder circuits

Building block circuits:

Inverters

Decoders

Multiplexers

HW 6: Unsigned Binary Subtraction

For each of the $\langle X, Y \rangle$ pairs below:

- Convert X and $Y \rightarrow$ binary
- Compute \bar{Y} , the 2's complement of Y
- Compute 8-bit diff using 2's complement addition
- Convert $\text{diff} \rightarrow$ hexadecimal
- Indicate whether 8-bit subtraction produces a **carry**
- Convert $X, Y, \bar{Y}, \text{diff} \rightarrow$ decimal (check your work)

Where $\langle X, Y \rangle =$

- $\langle 0x4F, 0x6D \rangle$
- $\langle 0xC8, 0x2B \rangle$
- $\langle 0xA3, 0x95 \rangle$
- $\langle 0xB4, 0xE1 \rangle$

HW 6 #1

$$X = 0x4F,$$

$$Y = 0x6D$$

$$X = 0b01001111,$$

$$Y = 0b01101101$$

$$\bar{Y} = 10010010$$

$$\bar{Y} + 1 = 10010011$$

$$\begin{array}{r} X \text{ --- } Y \\ \hline 01001111 \\ 10010011 \\ \hline \end{array}$$

carry

0 0 0 1 1 1 1 1

$$011100010 \rightarrow 0xE2 \quad (+ \quad 0x0)$$

$$X = 4 \cdot 16 + 15 = 79$$

$$Y = 6 \cdot 16 + 13 = 109$$

$$\bar{Y} = 9 \cdot 16 + 3 = 147$$

$$X \text{ --- } Y = 14 \cdot 16 + 2 = 226$$

$$X - Y = -30 = 226 - 256$$

HW 6 #2

$$X = 0x\text{C8},$$

$$Y = 0x\text{2B}$$

$$X = 0b\text{11001000},$$

$$Y = 0b\text{00101011}$$

$$\bar{Y} = 11010100$$

$$\bar{Y} + 1 = 11010101$$

$$\begin{array}{r} X \\ - Y \\ \hline \end{array} = \begin{array}{r} 11001000 \\ 11010101 \\ \hline \end{array}$$

carry

1 1 0 0 0 0 0 0

$$110011101 \rightarrow 0x\text{9D} (+ 0x\text{100})$$

$$X = 12 \cdot 16 + 8 = 200$$

$$Y = 2 \cdot 16 + 11 = 43$$

$$\bar{Y} = 13 \cdot 16 + 5 = 213$$

$$X - Y = 9 \cdot 16 + 13 = 157$$

$$X - Y = 157 = 157$$

HW 6 #3

$$X = 0x\text{A3},$$

$$Y = 0x\text{95}$$

$$X = 0b\text{10100011},$$

$$Y = 0b\text{10010101}$$

$$\bar{Y} = 01101010$$

$$\bar{Y} + 1 = 01101011$$

$$\begin{array}{r} X \\ - Y \\ \hline \end{array} = \begin{array}{r} 10100011 \\ 01101011 \\ \hline \end{array}$$

carry

1 1 1 0 0 0 1 1

$$100001110 \rightarrow 0x\text{0E} (+ 0x\text{100})$$

$$X = 10 \cdot 16 + 3 = 163$$

$$Y = 9 \cdot 16 + 5 = 149$$

$$\bar{Y} = 6 \cdot 16 + 10 = 106$$

$$X - Y = 0 \cdot 16 + 14 = 14$$

$$X - Y = 14 = 14$$

HW 6 #4

$$X = 0x\text{B4},$$

$$Y = 0x\text{E1}$$

$$X = 0b\text{10110100},$$

$$Y = 0b\text{11100001}$$

$$\bar{Y} = 00011110$$

$$\bar{Y} + 1 = 00011111$$

$$\begin{array}{r} X \text{ --- } Y \\ \begin{array}{r} 10110100 \\ 00011111 \\ \hline \end{array} \end{array}$$

carry

0 0 1 1 1 1 0 0

$$011010011 \rightarrow 0x\text{D3} \quad (+ \quad 0x0)$$

$$X = 11 \cdot 16 + 4 = 180$$

$$Y = 14 \cdot 16 + 1 = 225$$

$$\bar{Y} = 1 \cdot 16 + 15 = 31$$

$$X \text{ --- } Y = 13 \cdot 16 + 3 = 211$$

$$X - Y = -45 = 211 - 256$$

Unsigned n-bit Subtraction ($0 == 2^n$)

$$\mathbf{A \geq B}$$

$$A \overset{\dots}{-} B \equiv A - B \text{ (natural numbers)}$$

$$\mathbf{A < B} \quad A - B \text{ undefined on natural numbers}$$

$$\overset{\dots}{B} \equiv 2^n - B = (2^n - 1 - B) + 1 = \overline{B} + 1$$

$$B \overset{\dots}{-} B = B \overset{\dots}{+} \overset{\dots}{B} = 0 \quad (0 == 2^n)$$

$$(A \overset{\dots}{-} B) \overset{\dots}{+} C = (A \overset{\dots}{+} C) \overset{\dots}{-} B$$

$$A \overset{\dots}{-} B \equiv A \overset{\dots}{+} (\overline{B} + 1)$$

n-bit Binary Numbers

Unsigned: $b_{n-1} b_{n-2} \dots b_1 b_0$ ($b_i = 0$ or $b_i = 1$)

value: $b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_1 2^1 + b_0 2^0$

range: $[0 .. 2^n - 1]$

n-bit sum: $A \overset{\dots}{+} B + \textcolor{violet}{c} \cdot 2^n = A + B$

n-bit diff: $A \overset{\dots}{-} B \equiv A \overset{\dots}{+} (2^n - B) = A \overset{\dots}{+} \overline{B} + 1 = A - B + 2^n - \textcolor{violet}{c} \cdot 2^n$

Unsigned Integers


$2 \cdot 2^N$

$1\frac{1}{2} \cdot 2^N$

$1 \cdot 2^N$

$\frac{1}{2} \cdot 2^N$

$0 \cdot 2^N$

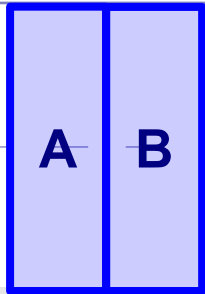


$-\frac{1}{2} \cdot 2^N$

$-1 \cdot 2^N$


$-1\frac{1}{2} \cdot 2^N$

$-2 \cdot 2^N$


Unsigned Sum

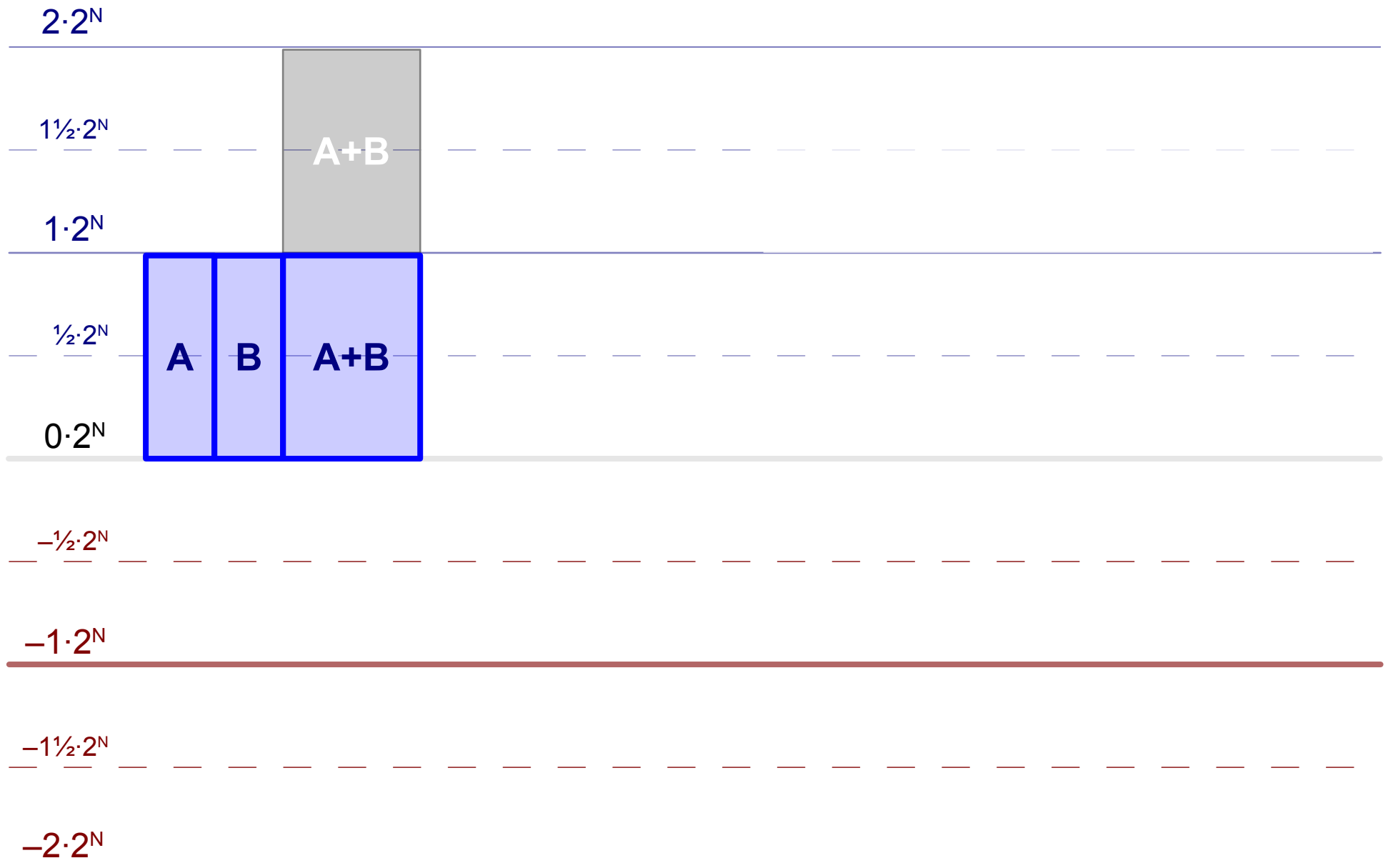


Unsigned Sum

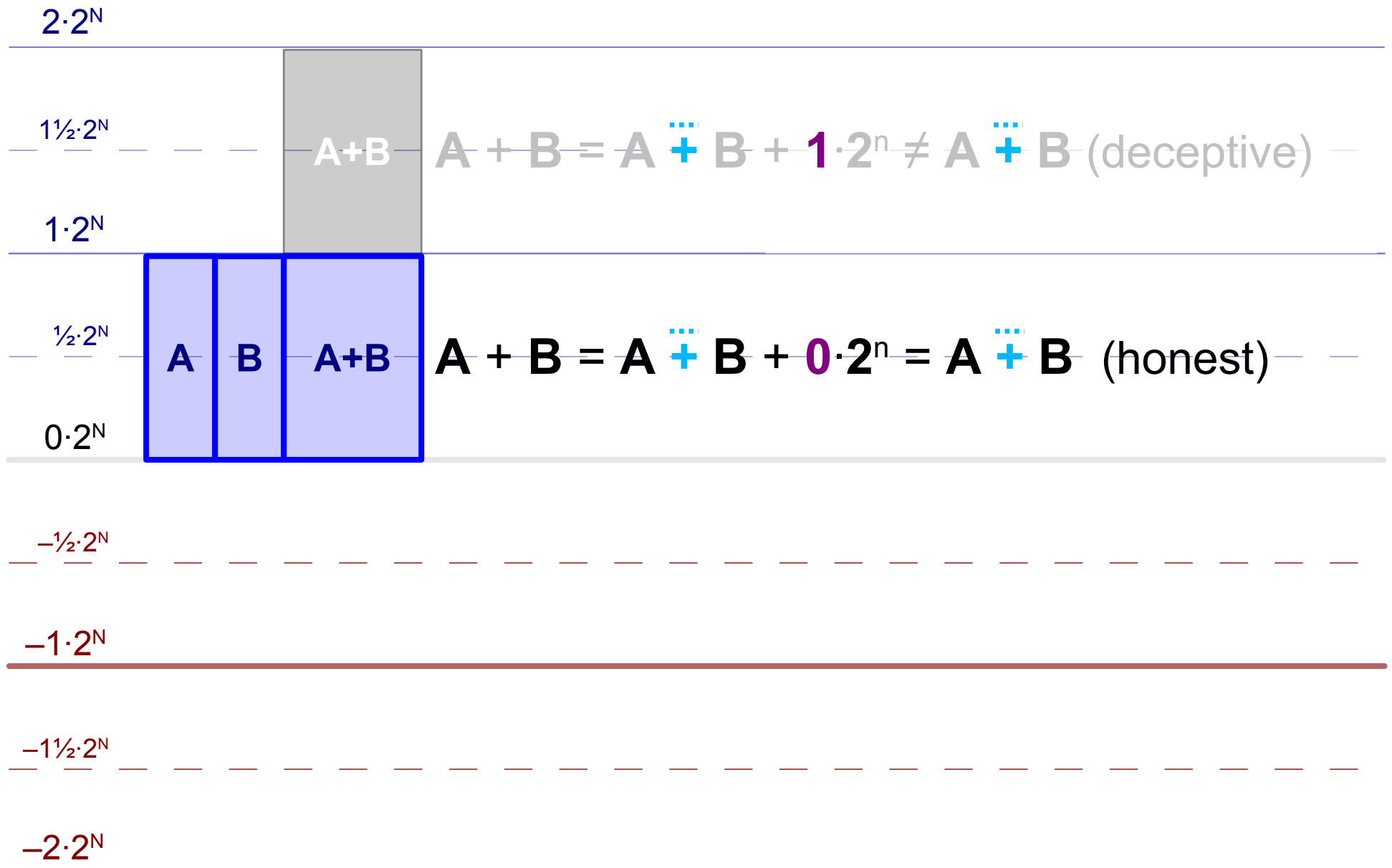

Unsigned Sum and Difference

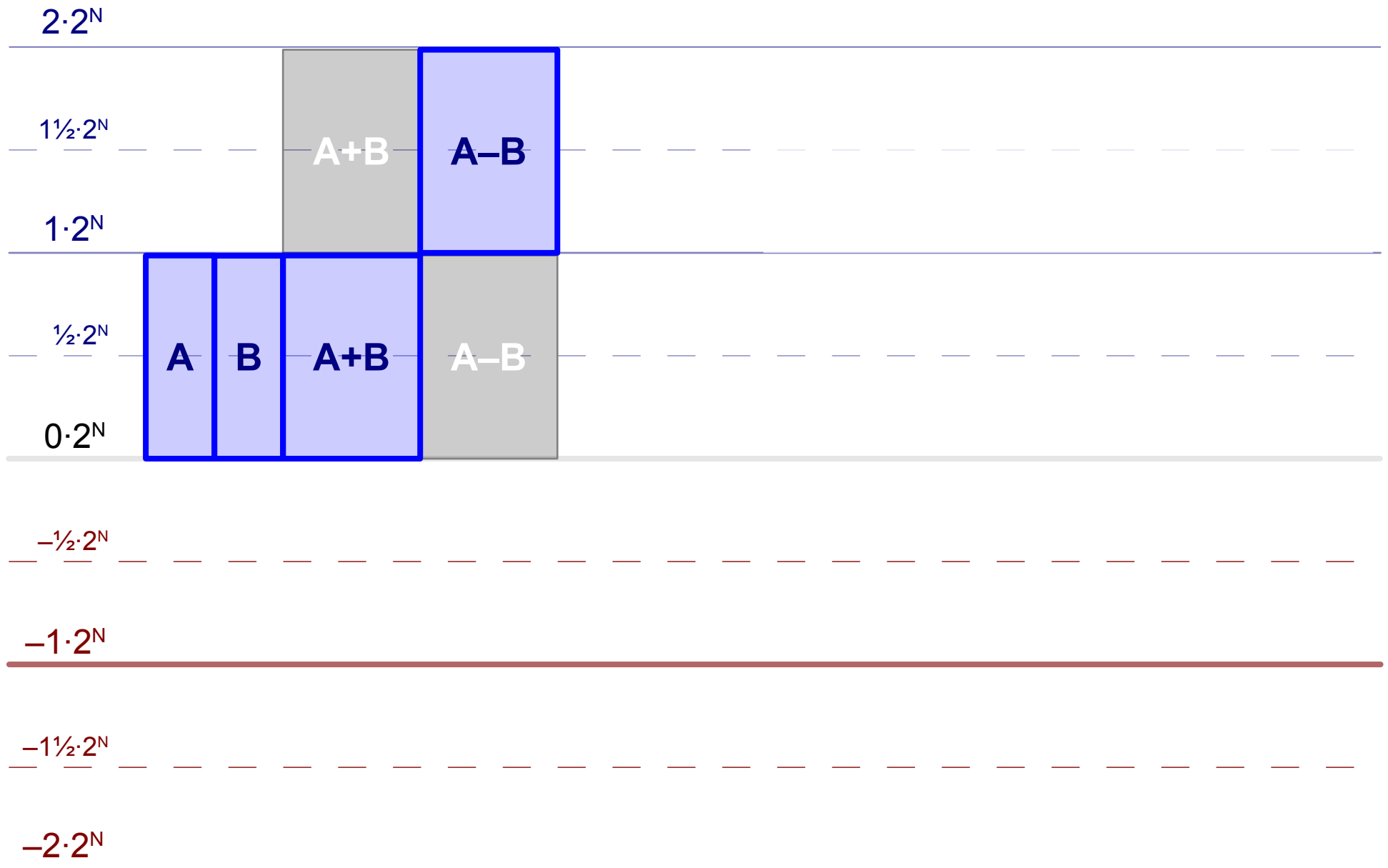

Unsigned Sum and Difference

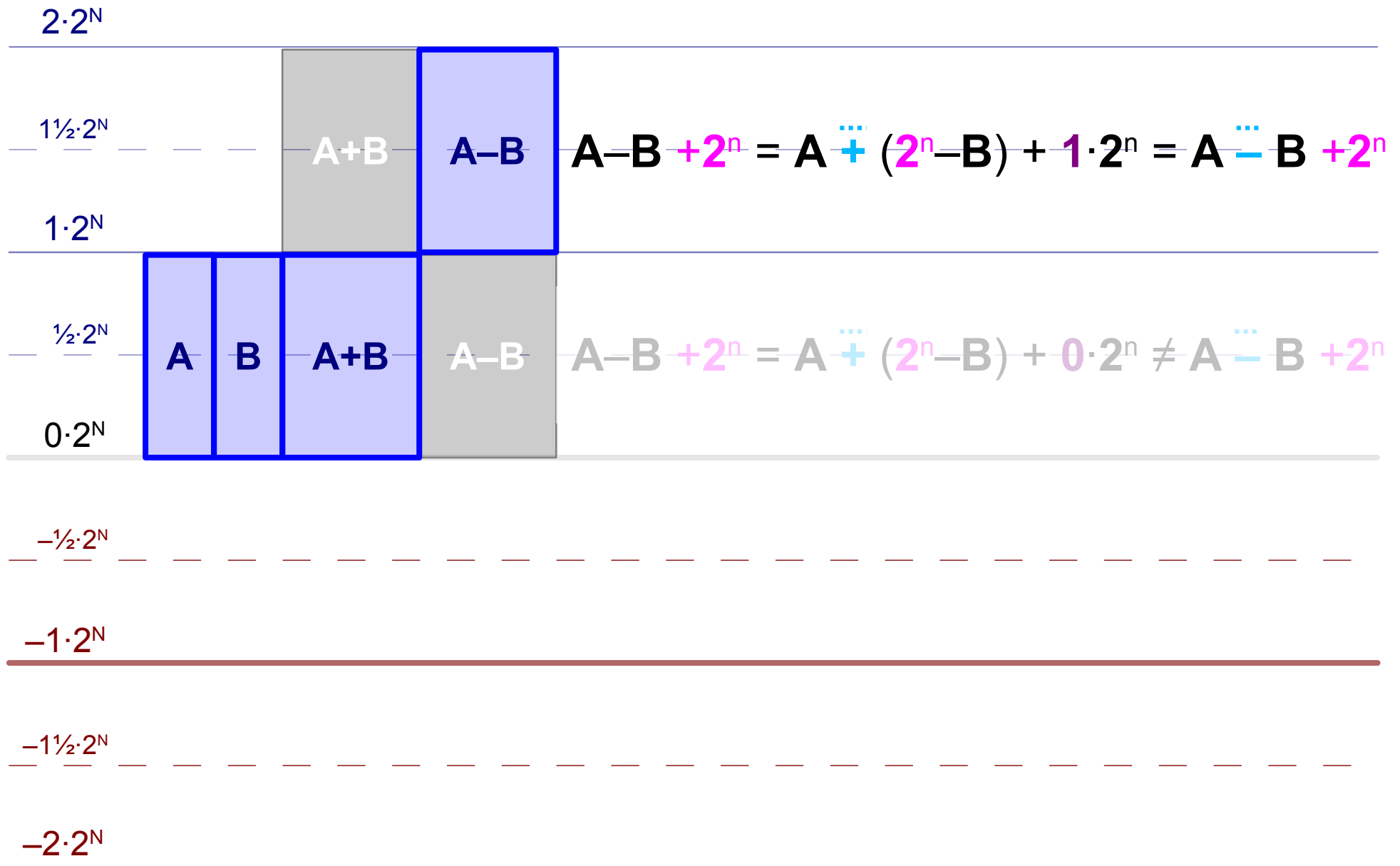

n-bit Binary Numbers

Unsigned: $b_{n-1} b_{n-2} \dots b_1 b_0$ ($b_i = 0$ or $b_i = 1$)

value: $b_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_12^1 + b_02^0$

range: $[0 \dots 2^n - 1]$

n-bit sum: $A \overset{\text{---}}{+} B + c \cdot 2^n = A + B$

n-bit diff: $A \overset{\text{---}}{-} B \equiv A \overset{\text{---}}{+} (2^n - B) = A \overset{\text{---}}{+} \bar{B} + 1 = A - B + 2^n - c \cdot 2^n$

Signed: $b_{n-1} b_{n-2} \dots b_1 b_0$

value: $-b_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_12^1 + b_02^0$

range: $[-2^{n-1} \dots 2^{n-1} - 1]$

n-bit Binary Numbers

Unsigned: $b_{n-1} b_{n-2} \dots b_1 b_0$ ($b_i = 0$ or $b_i = 1$)

value: $b_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_12^1 + b_02^0$

range: $[0 \dots 2^n - 1]$

n-bit sum: $A \overset{\text{---}}{+} B + \text{c} \cdot 2^n = A + B$

n-bit diff: $A \overset{\text{---}}{-} B \equiv A \overset{\text{---}}{+} (2^n - B) = A \overset{\text{---}}{+} \bar{B} + 1 = A - B + 2^n - \text{c} \cdot 2^n$


Signed: $b_{n-1} b_{n-2} \dots b_1 b_0$

value: $-b_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_12^1 + b_02^0$

range: $[-2^{n-1} \dots 2^{n-1} - 1]$

n-bit sum: $A \overset{\text{---}}{+} B = A + B$ iff $v=0$

Whole Numbers (binary)



...001000	+8
...000111	+7
...000110	+6
...000101	+5
...000100	+4
...000011	+3
...000010	+2
...000001	+1
...000000	+0
...111111	-1
...111110	-2
...111101	-3
...111100	-4
...111011	-5
...111010	-6
...111001	-7
...111000	-8

unbounded integers

... -2, -1, 0, 1, 2, ...

Closed under addition

Closed under subtraction

“Sign”

Negative integers => leading 1's

Positive integers => leading 0's

0 is an honorary positive integer

$$0 + 0 = 0$$

$$3 + -3 = 0$$

$$6 + -6 = 0$$

$$1 + -1 = 0$$

$$4 + -4 = 0$$



$$7 + -7 = 0$$

$$2 + -2 = 0$$

$$5 + -5 = 0$$

$$8 + -8 = 0$$

Additive Inverse





.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Additive Inverse



.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:


If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

Additive Inverse

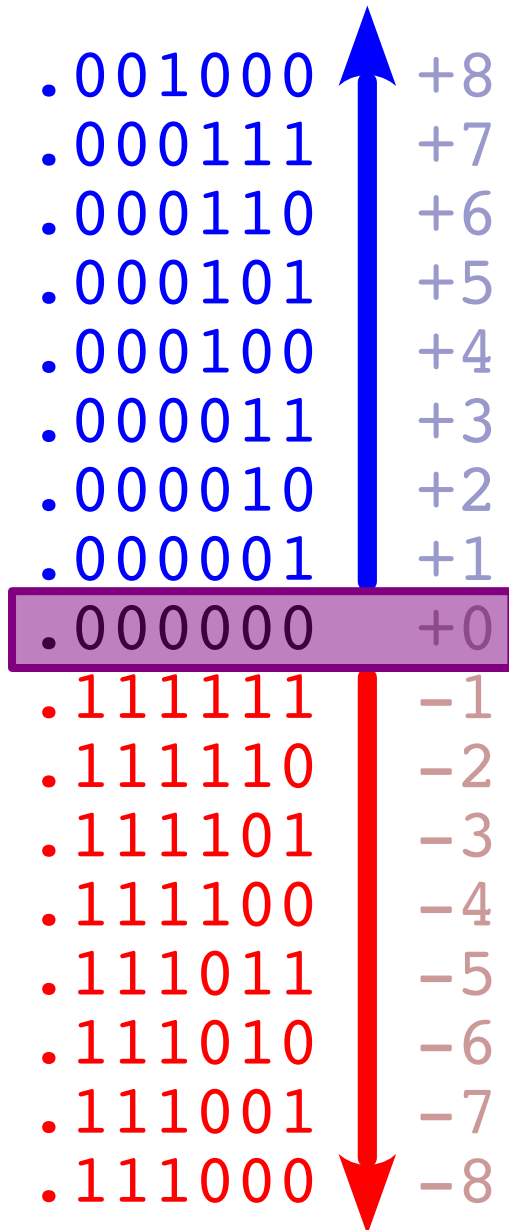

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then


$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

– .0000

Additive Inverse

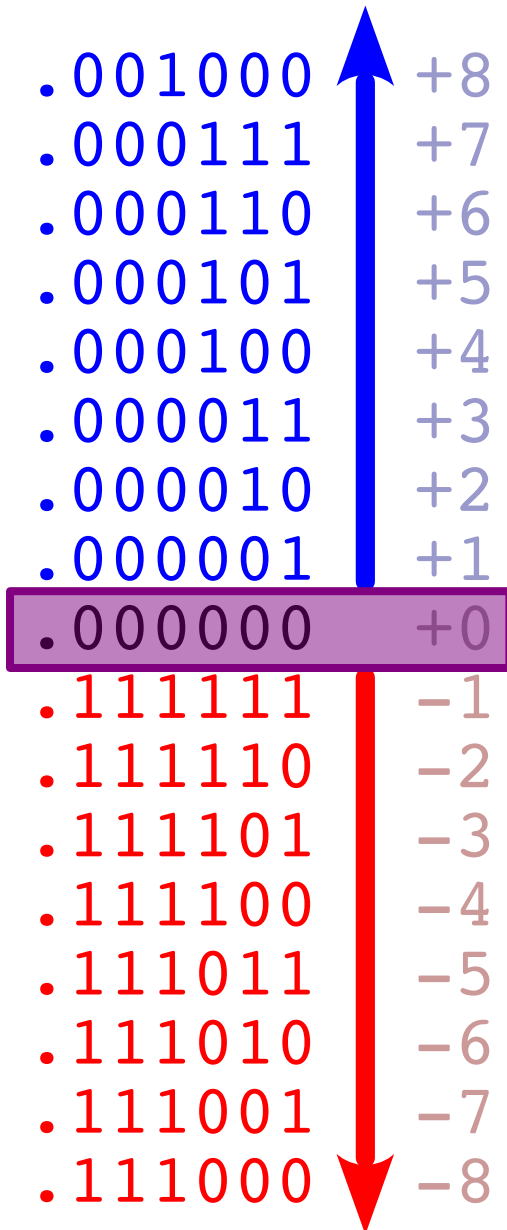

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then


$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$\mathbf{-.0000 = \overline{.0000} + 1}$$

Additive Inverse

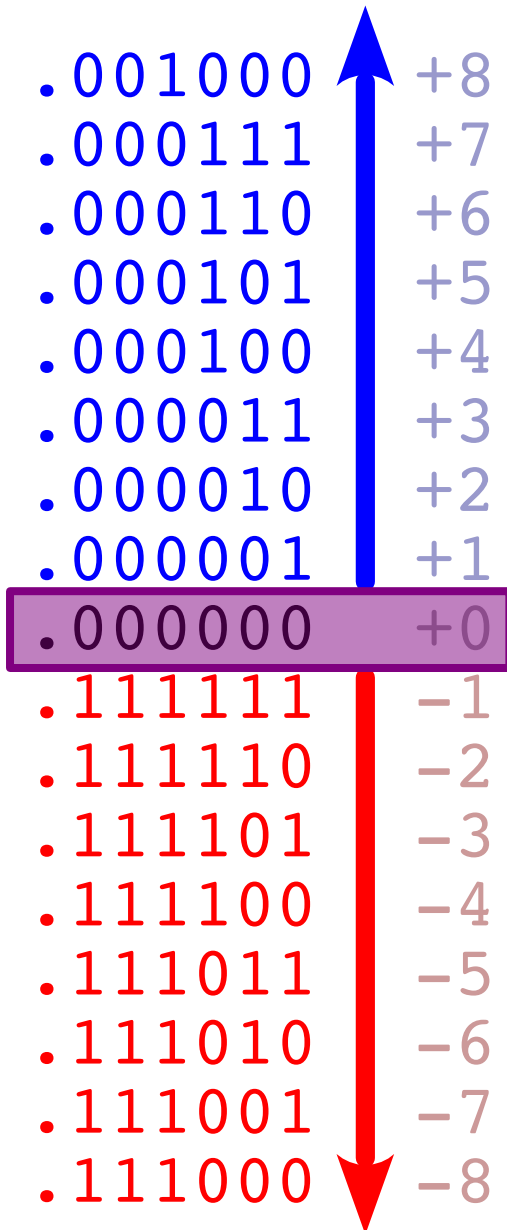

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then


$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$\mathbf{-.0000 = \overline{.0000} + 1 = .1111 + 1}$$

Additive Inverse

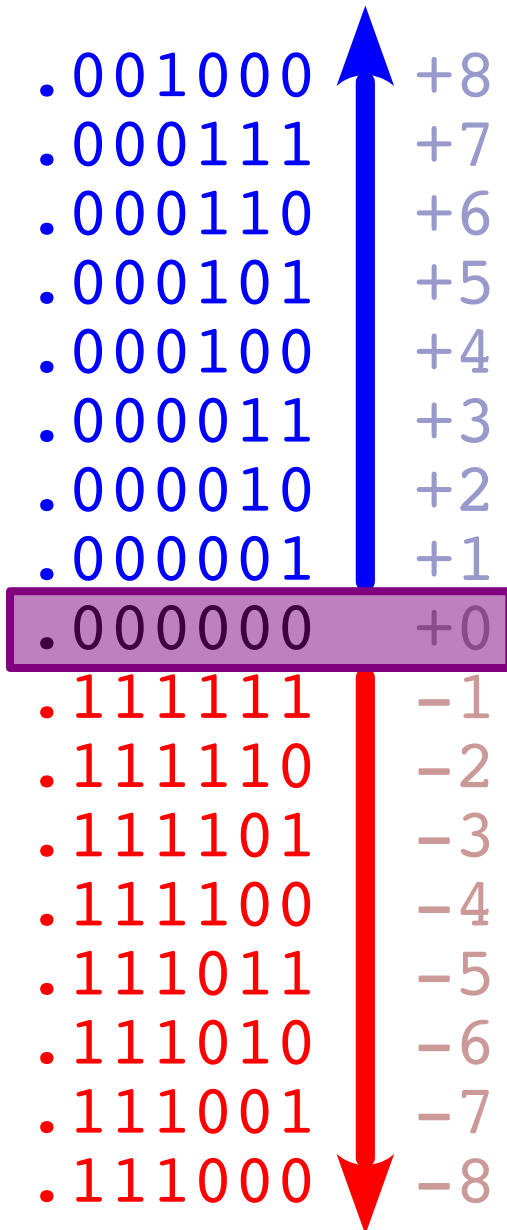

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then


$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$\mathbf{-.0000 = \overline{.0000} + 1 = .1111 + 1 = .0000}$$

Additive Inverse

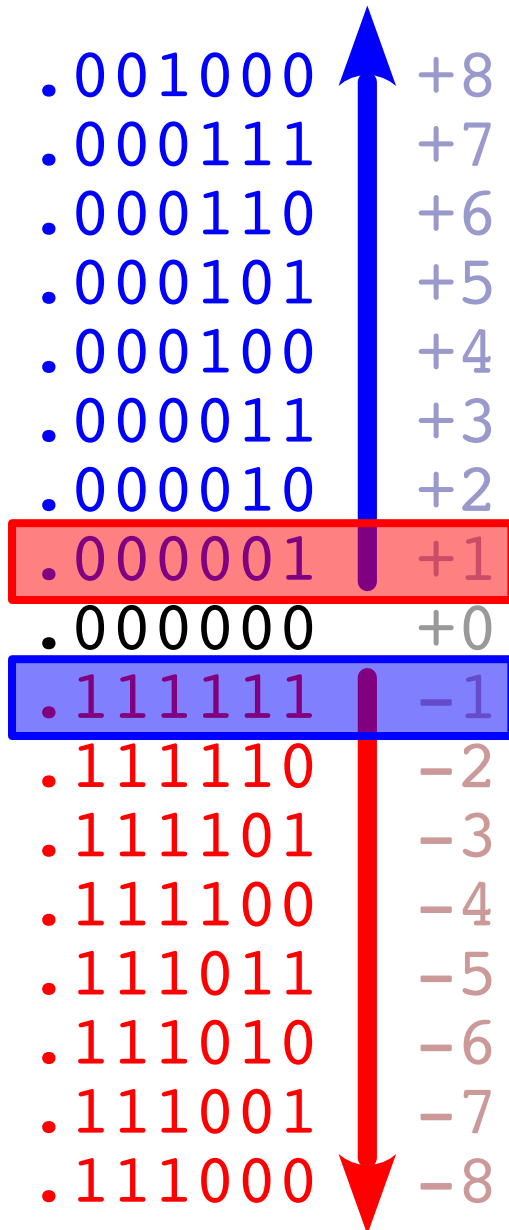

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$\mathbf{- .0001}$$

$$\mathbf{- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000}$$

Additive Inverse

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$


Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$- .0001 = \overline{.0001} + 1$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

Additive Inverse

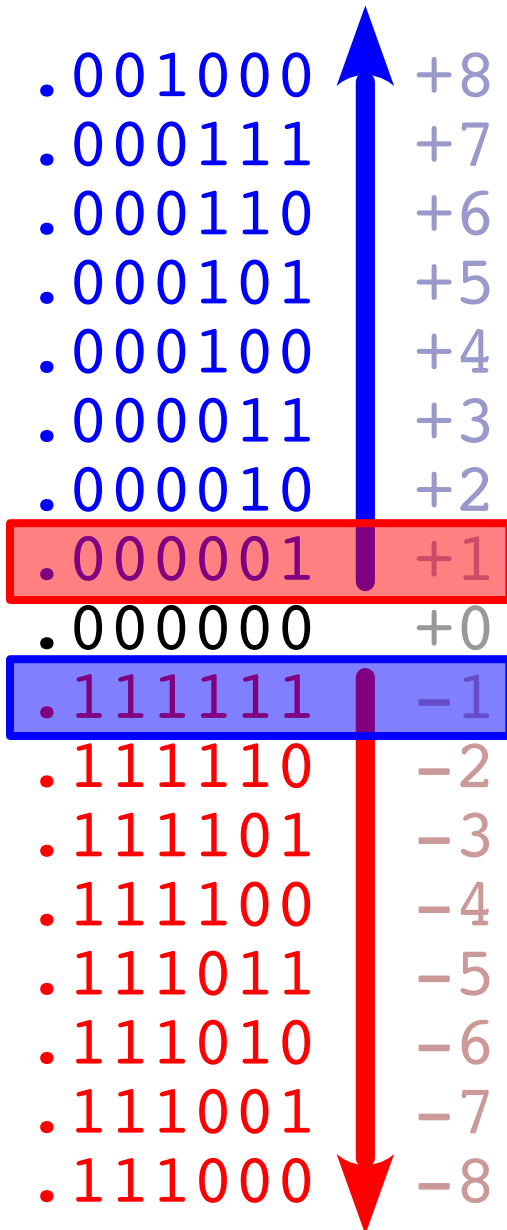

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$


Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$- .0001 = \overline{.0001} + 1 = .1110 + 1$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

Additive Inverse



.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then


$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$-\mathbf{Y = \bar{Y} + 1}$$

$$\begin{aligned} - .0001 &= \overline{.0001} + 1 = .1110 + 1 = .1111 \\ - .0000 &= \overline{.0000} + 1 = .1111 + 1 = .0000 \end{aligned}$$

Additive Inverse



.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then


$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$\begin{aligned} - .0001 &= \overline{.0001} + 1 = .1110 + 1 = .1111 \\ - .0000 &= \overline{.0000} + 1 = .1111 + 1 = .0000 \\ - .1111 & \end{aligned}$$

Additive Inverse

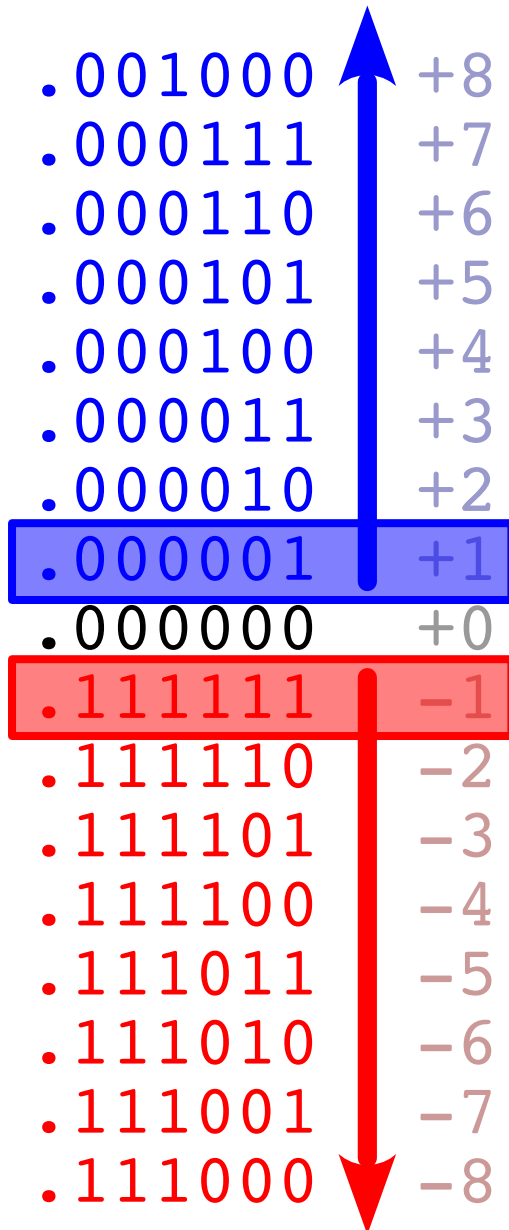

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then


$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$\begin{aligned} - .0001 &= \overline{.0001} + 1 = .1110 + 1 = .1111 \\ - .0000 &= \overline{.0000} + 1 = .1111 + 1 = .0000 \\ - .1111 &= \overline{.1111} + 1 \end{aligned}$$

Additive Inverse

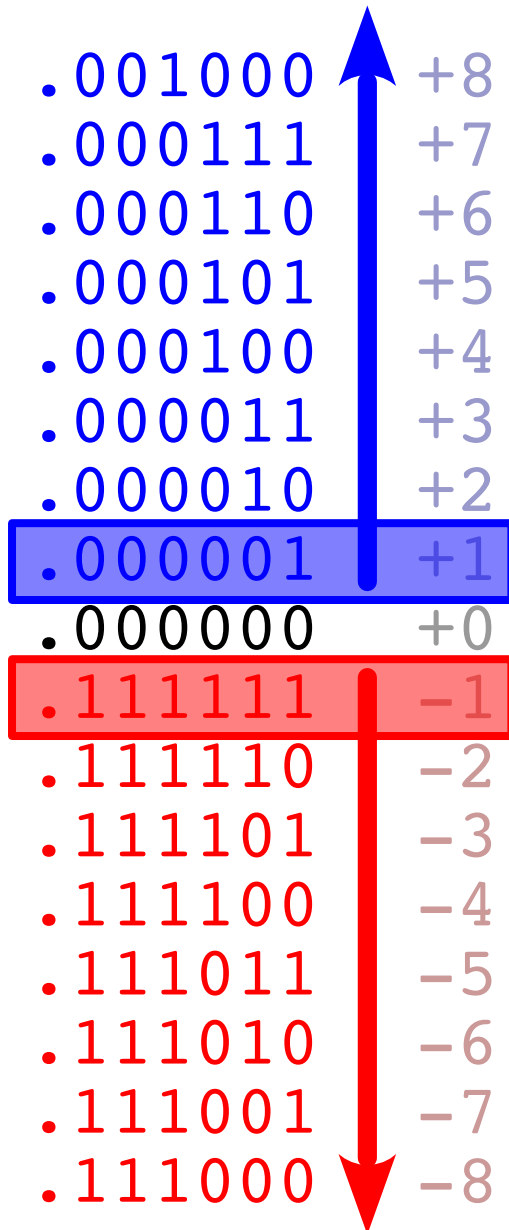

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEOREM:

If X and Y are signed integers then

$$X - Y = X + \bar{Y} + 1$$

Corollary:

$$-Y = \bar{Y} + 1$$

$$\begin{aligned}
 - .0001 &= \overline{.0001} + 1 = .1110 + 1 = .1111 \\
 - .0000 &= \overline{.0000} + 1 = .1111 + 1 = .0000 \\
 - .1111 &= \overline{.1111} + 1 = .0000 + 1
 \end{aligned}$$

Additive Inverse

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEOREM:

If X and Y are signed integers then

$$X - Y = X + \bar{Y} + 1$$

Corollary:

$$-Y = \bar{Y} + 1$$

$$\begin{aligned}
 -.0001 &= \overline{.0001} + 1 = .1110 + 1 = .1111 \\
 -.0000 &= \overline{.0000} + 1 = .1111 + 1 = .0000 \\
 -.1111 &= \overline{.1111} + 1 = .0000 + 1 = .0001
 \end{aligned}$$

Additive Inverse

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEOREM:

If X and Y are signed integers then

$$X - Y = X + \bar{Y} + 1$$

Corollary:

$$-Y = \bar{Y} + 1$$

$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011$$

Additive Inverse

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$-\mathbf{Y = \bar{Y} + 1}$$


$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011 = \overline{.1011} + 1$$

Additive Inverse



.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$


$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011 = \overline{.1011} + 1 = .0100 + 1$$

Additive Inverse

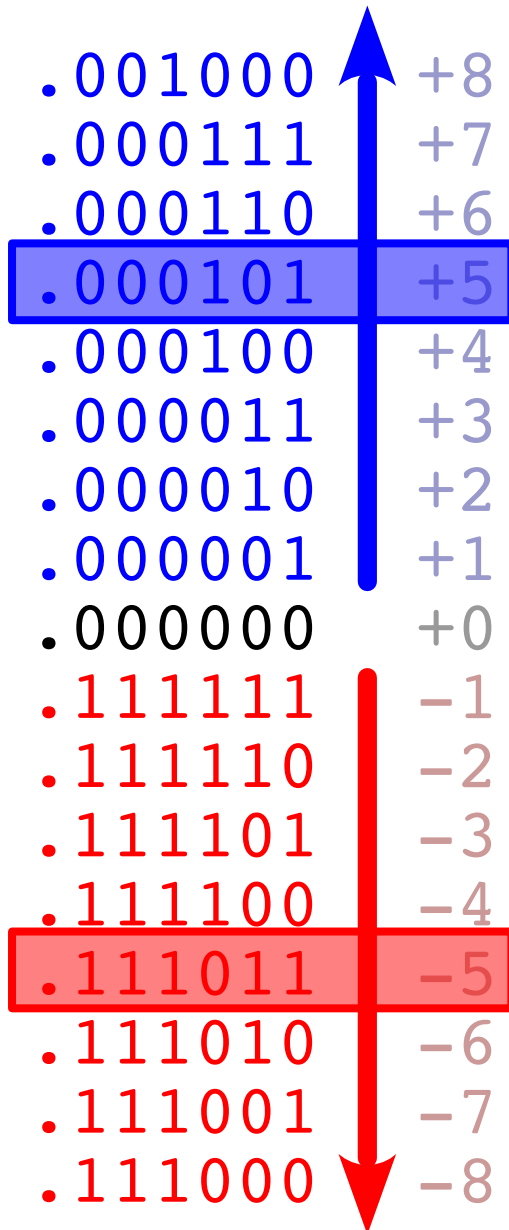

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$


$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011 = \overline{.1011} + 1 = .0100 + 1 = .0101$$

Additive Inverse

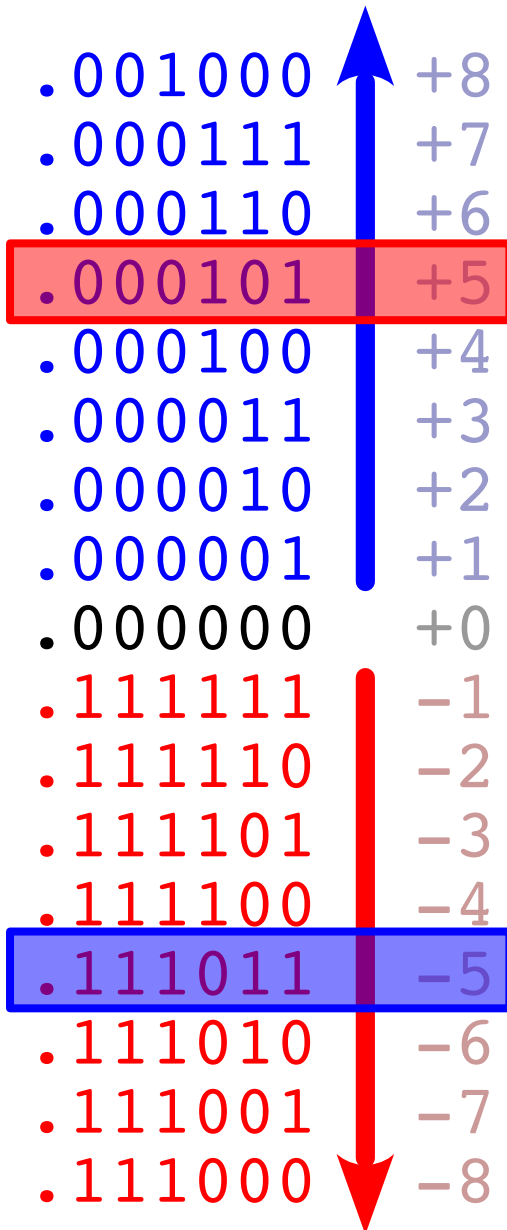

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$- .0101$$


$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011 = \overline{.1011} + 1 = .0100 + 1 = .0101$$

Additive Inverse



.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$- .0101 = \overline{.0101} + 1$$


$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011 = \overline{.1011} + 1 = .0100 + 1 = .0101$$

Additive Inverse

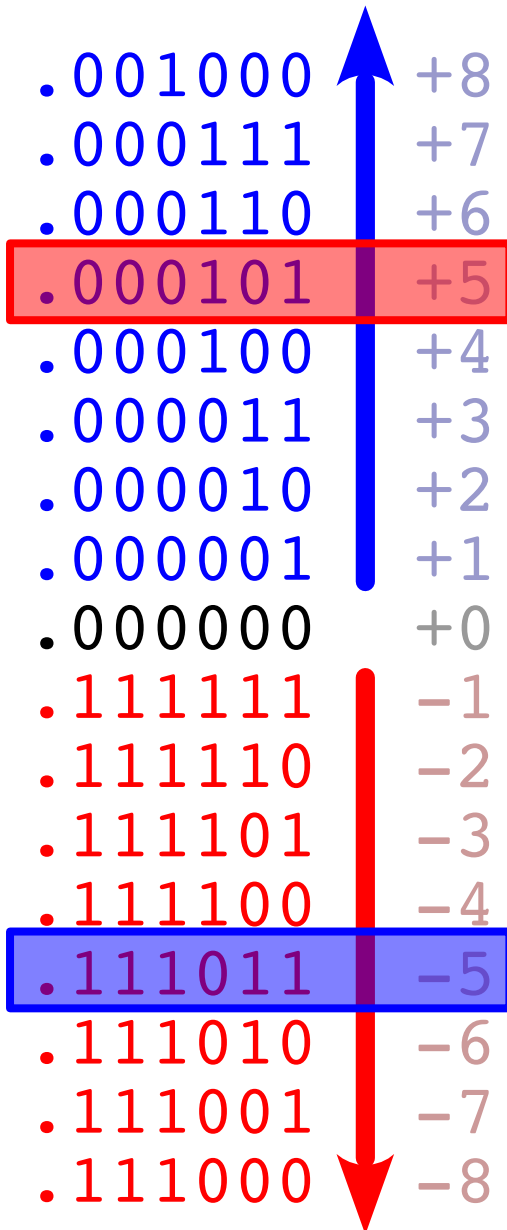

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$X - Y = X + \bar{Y} + 1$$

Corollary:

$$-Y = \bar{Y} + 1$$

$$- .0101 = \overline{.0101} + 1 = .1010 + 1$$


$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011 = \overline{.1011} + 1 = .0100 + 1 = .0101$$

Additive Inverse



.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

THEROEM:

If **X** and **Y** are signed integers then

$$\mathbf{X - Y = X + \bar{Y} + 1}$$

Corollary:

$$\mathbf{-Y = \bar{Y} + 1}$$

$$- .0101 = \overline{.0101} + 1 = .1010 + 1 = .1011$$

$$- .0001 = \overline{.0001} + 1 = .1110 + 1 = .1111$$

$$- .0000 = \overline{.0000} + 1 = .1111 + 1 = .0000$$

$$- .1111 = \overline{.1111} + 1 = .0000 + 1 = .0001$$

$$- .1011 = \overline{.1011} + 1 = .0100 + 1 = .0101$$

n-bit Binary Numbers

Unsigned: $b_{n-1} b_{n-2} \dots b_1 b_0$ ($b_i = 0$ or $b_i = 1$)

value: $b_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_12^1 + b_02^0$

range: $[0 \dots 2^n - 1]$

n-bit sum: $A \overset{\dots}{+} B + \textcolor{violet}{c} \cdot 2^n = A + B$

n-bit diff: $A \overset{\dots}{-} B \equiv A \overset{\dots}{+} (2^n - B) = A \overset{\dots}{+} \overline{B} + 1 = A - B + 2^n - \textcolor{violet}{c} \cdot 2^n$

Signed: $b_{n-1} b_{n-2} \dots b_1 b_0$

value: $-\textcolor{red}{b}_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_12^1 + b_02^0$

range: $[-2^{n-1} \dots 2^{n-1} - 1]$

n-bit sum: $A \overset{\dots}{+} B = A + B$ iff $\textcolor{teal}{v}=0$

n-bit diff: $A \overset{\dots}{-} B \equiv A \overset{\dots}{+} (2^n - B) = A \overset{\dots}{+} \overline{B} + 1 = A - B$ iff $\textcolor{teal}{v}=0$

N-Bit Integers (N = 8)

Unsigned Integers

...	0100000000
...	0011111111
...	0010000000
...	0001111111
...	0000000101
...	0000000100
...	0000000011
...	0000000010
...	0000000001
...	0000000000
...	1111111111
...	1111111110
...	1111111101
...	1111111100
...	1111111011
...	1110000000
...	1101111111
...	1100000000
...	1011111111

$$= 2^N$$

$$= 2^N - 1$$

$$= 2^{N-1}$$

$$= 2^{N-1} - 1$$

$$= 4 = 2^2$$

$$= 3 = 2^2 - 1$$

$$= 2 = 2^1$$

$$= 1 = 2^0 = 2^1 - 1$$

$$= 0 = 2^0 - 1$$

$$= -1 = -2^0$$

$$= -2 = -2^1$$

$$= -3 = -2^1 - 1$$

$$= -4 = -2^2$$

$$= -5 = -2^2 - 1$$

$$= -2^{N-1}$$


$$= -2^{N-1} - 1$$

$$= -2^N$$

$$= -2^N - 1$$

Signed Integers

3-Bit Unsigned Integers (Binary)



0000	1111
0000	1110
0000	1101
0000	1100
0000	1011
0000	1010
0000	1001
0000	1000
0000	111
0000	110
0000	101
0000	100
0000	011
0000	010
0000	001
0000	000

8 supported values: 0 .. 7

Not closed under addition

carry => **incorrect** result: 8 .. 14

Not closed under subtraction

7 undefined (negative) differences

Want: $A - B + C = A + C - B$


$$A - B \equiv A + 2^3 - B$$

$$\bar{B} \equiv 2^3 - B \quad (2^3 - B = \bar{B} + 1)$$

$$A \geq B \Rightarrow A - B + 2^3 > 2^3 \text{ (**carry**)}$$

carry => **correct** result: 0 .. 7

3-Bit Signed Binary Integers

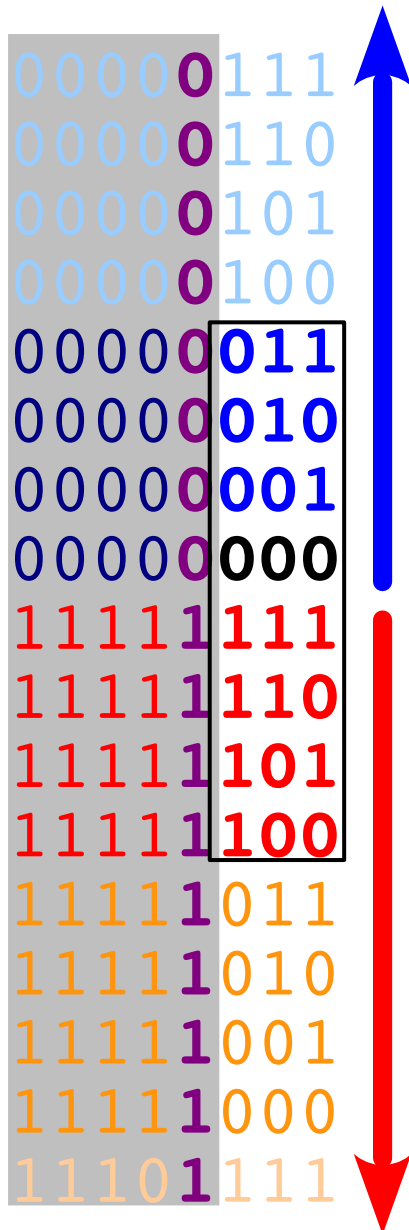

0000	0111
0000	0110
0000	0101
0000	0100
0000	0011
0000	0010
0000	0001
0000	0000
1111	1111
1111	1110
1111	1101
1111	1100
1111	1011
1111	1010
1111	1001
1111	1000
1110	1111

8 supported values: **-4** .. **3**

Sign: high bit: **0** positive, **1** negative

Not closed under addition

incorrect results: **-8** .. **-5**, **4** .. **6**

Not closed under subtraction

incorrect results: **-7** .. **-5**, **4** .. **7**


Correct: $X \oplus Y = Z$, $X \oplus Y = Z$

$X \oplus Y$, $X \oplus Y$ always correct. Why?

Incorrect: $X \oplus Y = Z$, $X \oplus Y = Z$

$X \oplus Y = Z$, $X \oplus Y = Z$

Unsigned Sum and Difference

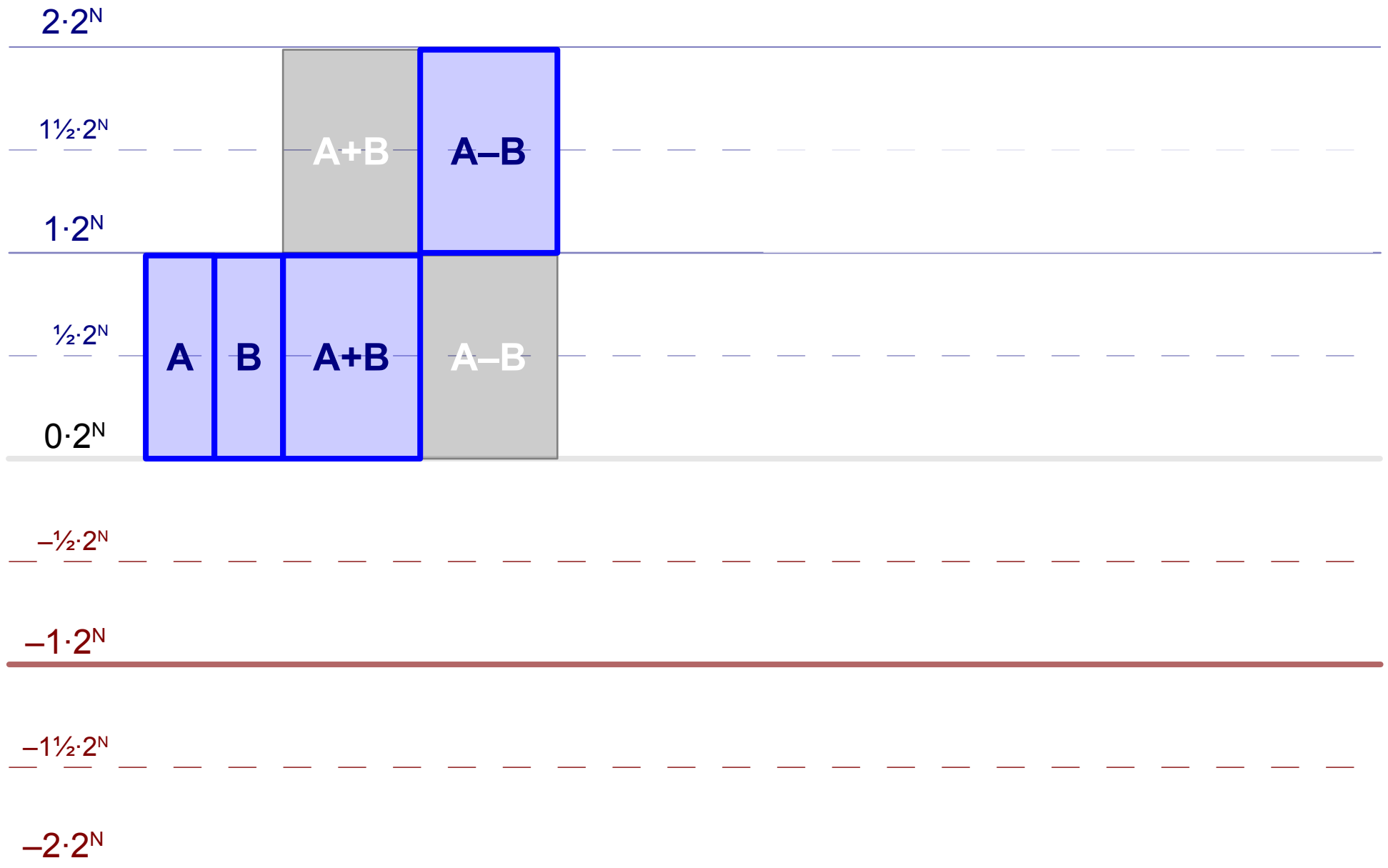

Signed Integers

$2 \cdot 2^N$

$1\frac{1}{2} \cdot 2^N$

$1 \cdot 2^N$

$\frac{1}{2} \cdot 2^N$


$0 \cdot 2^N$

$-\frac{1}{2} \cdot 2^N$

$-1 \cdot 2^N$

$-1\frac{1}{2} \cdot 2^N$

$-2 \cdot 2^N$

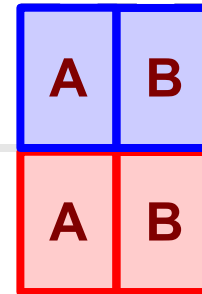

Signed Integer Sum or Difference

$2 \cdot 2^N$

$1\frac{1}{2} \cdot 2^N$

$1 \cdot 2^N$

$\frac{1}{2} \cdot 2^N$


$0 \cdot 2^N$

$-\frac{1}{2} \cdot 2^N$

$-1 \cdot 2^N$

$-1\frac{1}{2} \cdot 2^N$

$-2 \cdot 2^N$

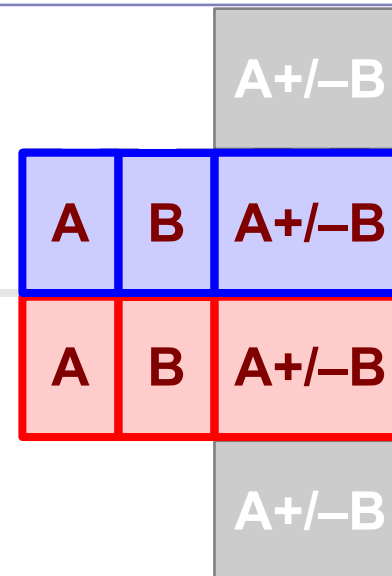

Signed Integer Sum or Difference

$2 \cdot 2^N$

$1\frac{1}{2} \cdot 2^N$

$1 \cdot 2^N$

$\frac{1}{2} \cdot 2^N$


$0 \cdot 2^N$

$-\frac{1}{2} \cdot 2^N$

$-1 \cdot 2^N$

$-1\frac{1}{2} \cdot 2^N$

$-2 \cdot 2^N$

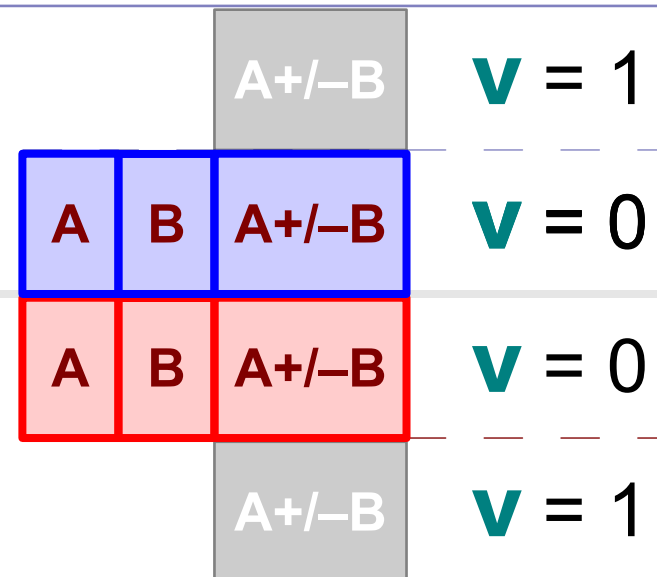

Unsigned Two's Complement

.010000	16
.001111	15
.001110	14
.001101	13
.001100	12
.001011	11
.001010	10
.001001	09
.001000	08
.000111	07
.000110	06
.000101	05
.000100	04
.000011	03
.000010	02
.000001	01
.000000	00



Additive Inverse Theroem:

If X and Y are whole numbers

$$X - Y = X + \bar{Y} + 1$$

$$-Y \equiv \bar{Y} + 1$$

Unsigned N-bit integers: A and B

$$\underline{B} + \underline{\bar{B}} + 1 = 2^N - 1 + 1 = 2^N = \underline{0}$$

$$\underline{A} - \underline{B} \equiv \underline{A} + \underline{\bar{B}} + 1$$

$$= 2^N + \underline{A} - \underline{B} \quad \underline{\text{if } 0 \leq \underline{A} - \underline{B} < 2^N \text{ (} \underline{A} \geq \underline{B} \text{)}}$$

Carry => **correct subtraction**

Signed Two's Complement

.001000	+8
.000111	+7
.000110	+6
.000101	+5
.000100	+4
.000011	+3
.000010	+2
.000001	+1
.000000	+0
.111111	-1
.111110	-2
.111101	-3
.111100	-4
.111011	-5
.111010	-6
.111001	-7
.111000	-8

Additive Inverse Theroem:

If X and Y are whole numbers

$$X - Y = X + \bar{Y} + 1$$

$$-Y \equiv \bar{Y} + 1$$

Signed N-bit integers: C and D

$$D + \bar{D} + 1 = -1 + 1 = 0$$

$$\underline{C - D} = \underline{C + \bar{D} + 1}$$

$$= C - D \text{ if } -2^{N-1} \leq C - D < 2^{N-1}$$

oVerflow => incorrect subtraction

Honesty Criteria

The n-bit result **r** of a binary operation on n-bit values **a** and **b** is **honest** (**deceptive**) if it is *the same as* (*different from*) the whole number result of the same operation on the same values.

(n-bit) unsigned addition is *honest* iff (**c** = 0)

Carry flag is not set

(n-bit) unsigned subtraction is *honest* iff (**c** = 1)

Carry flag is set

(n-bit) signed addition is *honest* iff (**v** = 0)

a and **b** have different signs or **a**, **b**, and **r** have same sign

(n-bit) signed subtraction is *honest* iff (**v** = 0)

a and **b** have same sign or **a** and **r** have same sign

HW 9: Signed Binary Arithmetic

For each of the $\langle X, Y \rangle$ pairs in the table below:

- Convert X and $Y \rightarrow$ binary
- Compute $X + Y$ (the 8-bit **sum**)
- Compute \bar{Y} (the 2's complement of Y)
- Compute $X - Y \equiv X + \bar{Y}$ (the 8-bit **difference**)
- Convert $X + Y$, \bar{Y} , and $X - Y \rightarrow$ hexadecimal
- Indicate condition flag (**z**, **n**, **c**, **v**) values for $X + Y$, $X - Y$
- Indicate the signs of X , Y , $X + Y$, \bar{Y} , and $X - Y$
- Is $X + Y$ honest? is $X - Y$ honest?

Where $\langle X, Y \rangle =$

- | | |
|---------------------------------|---------------------------------|
| 1) $\langle 0x4F, 0x6D \rangle$ | 2) $\langle 0xB3, 0x17 \rangle$ |
| 3) $\langle 0xA3, 0x95 \rangle$ | 4) $\langle 0x6E, 0x3A \rangle$ |

Signed Arithmetic Example

X

0x8C

Y

0x6F

X + **Y**

~**Y**

X - **Y**

Signed Arithmetic Example

X

Y

X + Y

~Y

X - Y

0x8C

0x6F

10001100

01101111

Signed Arithmetic Example

X	Y	X + Y	~Y	X - Y
0x8C	0x6F			
10001100	01101111	10001100 01101111 <u> </u> 011111011		

Signed Arithmetic Example

X	Y	X + Y	~Y	X - Y
0x8C	0x6F			
10001100	01101111	10001100	<u>01101111</u>	
		<u>01101111</u>	10010000	
		011111011	<u>00000001</u>	
			10010001	

Signed Arithmetic Example

X	Y	X + Y	~Y	X - Y
0x8C	0x6F			
10001100	01101111	10001100 <u>01101111</u> 011111011	<u>01101111</u> 10010000 <u>00000001</u> 10010001	10001100 <u>10010001</u> 100011101

Signed Arithmetic Example

X	Y	X + Y	~Y	X - Y
0x8C	0x6F			
10001100	01101111	10001100 <u>01101111</u> 011111011	<u>01101111</u> 10010000 <u>00000001</u> 10010001	10001100 <u>10010001</u> 100011101

Signed Arithmetic Example

X	Y	X + Y	$\sim Y$	X - Y
0x8C	0x6F			
10001100	01101111	10001100 <u>01101111</u> 011111011	<u>01101111</u> 10010000 <u>00000001</u> 10010001	10001100 <u>10010001</u> 100011101
		0xFB	0x91	0x1D

Signed Arithmetic Example

X	Y	X + Y	~Y	X - Y
0x8C	0x6F			
10001100	01101111	<div>10001100 01101111 ----- 01111011</div>	<div>01101111 10010000 00000001 ----- 10010001</div>	<div>10001100 10010001 ----- 10001101</div>
		0xFB	0x91	0x1D
		no oVerflow		oVerflow


Signed Arithmetic Example

X	Y	X + Y	~Y	X - Y
0x8C	0x6F			
10001100	01101111	<div> <div>10001100</div> <div>01101111</div> <hr/> <div>011111011</div> </div>	<div> <div>01101111</div> <div>10010000</div> <hr/> <div>00000001</div> <div>10010001</div> </div>	<div> <div>10001100</div> <div>10010001</div> <hr/> <div>100011101</div> </div>
		0xFB	0x91	0x1D
		zncv		zncv


Signed Arithmetic Example

X	Y	X + Y	~Y	X - Y
0x8C	0x6F			
10001100	01101111	<div> <div>10001100</div> <div>01101111</div> <hr/> <div>011111011</div> </div>	<div> <div>01101111</div> <hr/> <div>10010000</div> <hr/> <div>00000001</div> <hr/> <div>10010001</div> </div>	<div> <div>10001100</div> <div>10010001</div> <hr/> <div>100011101</div> </div>
		0xFB	0x91	0x1D
		<div> <div>zncv</div> <div>honest</div> </div>		<div> <div>zncv</div> <div>deceptive</div> </div>


z — Zero condition flag

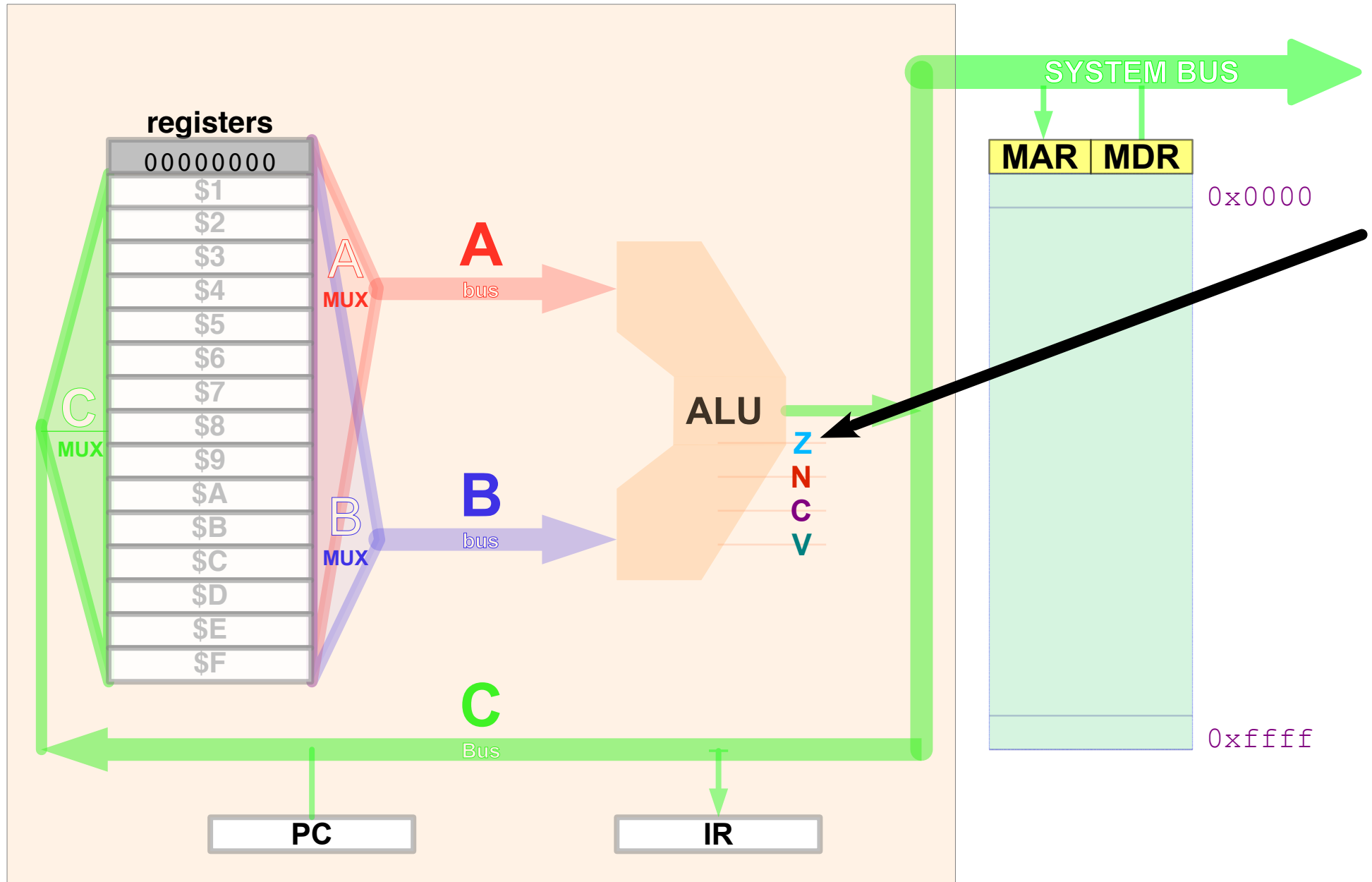


n — Negative condition flag

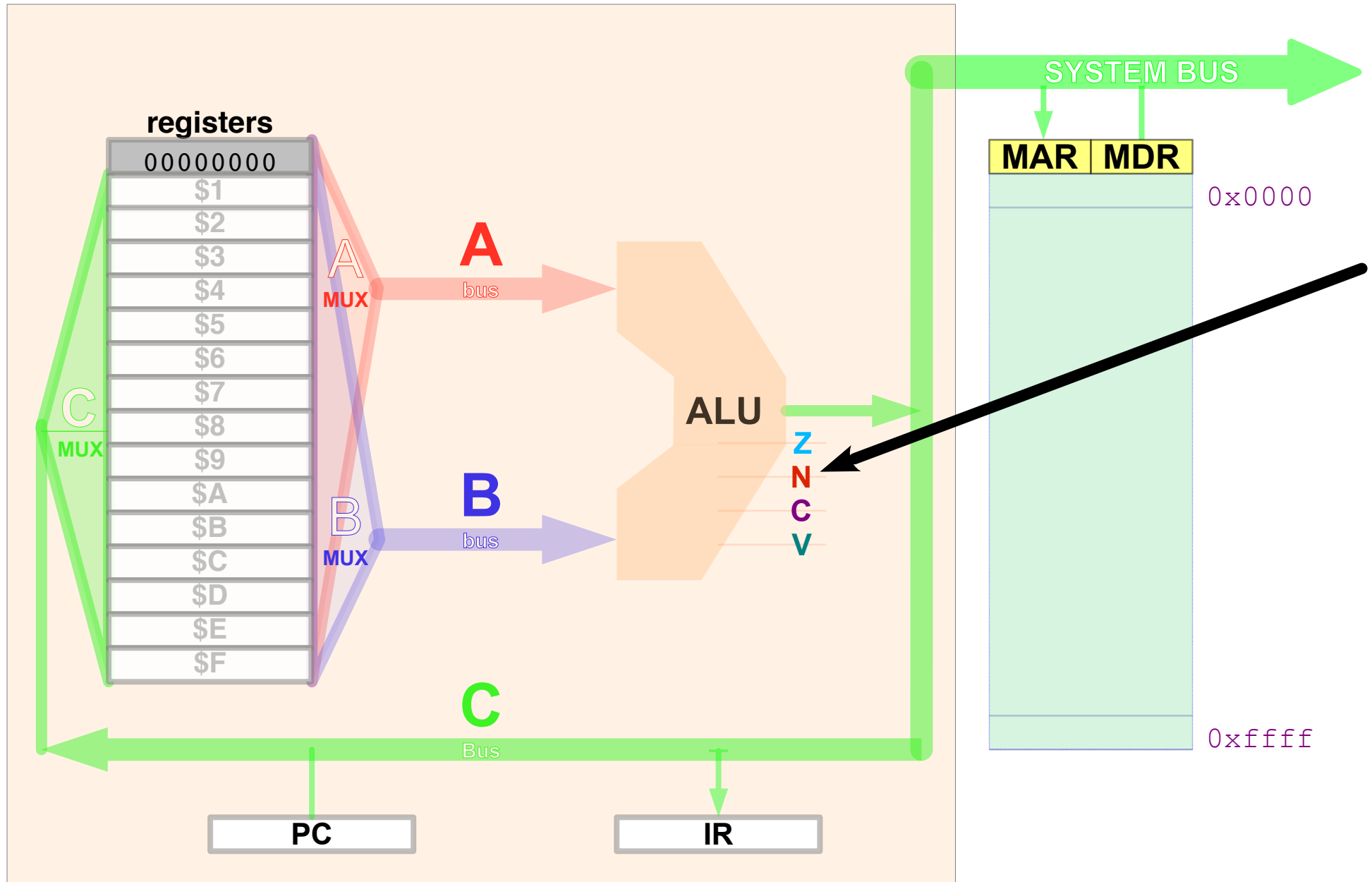


c — Carry condition flag

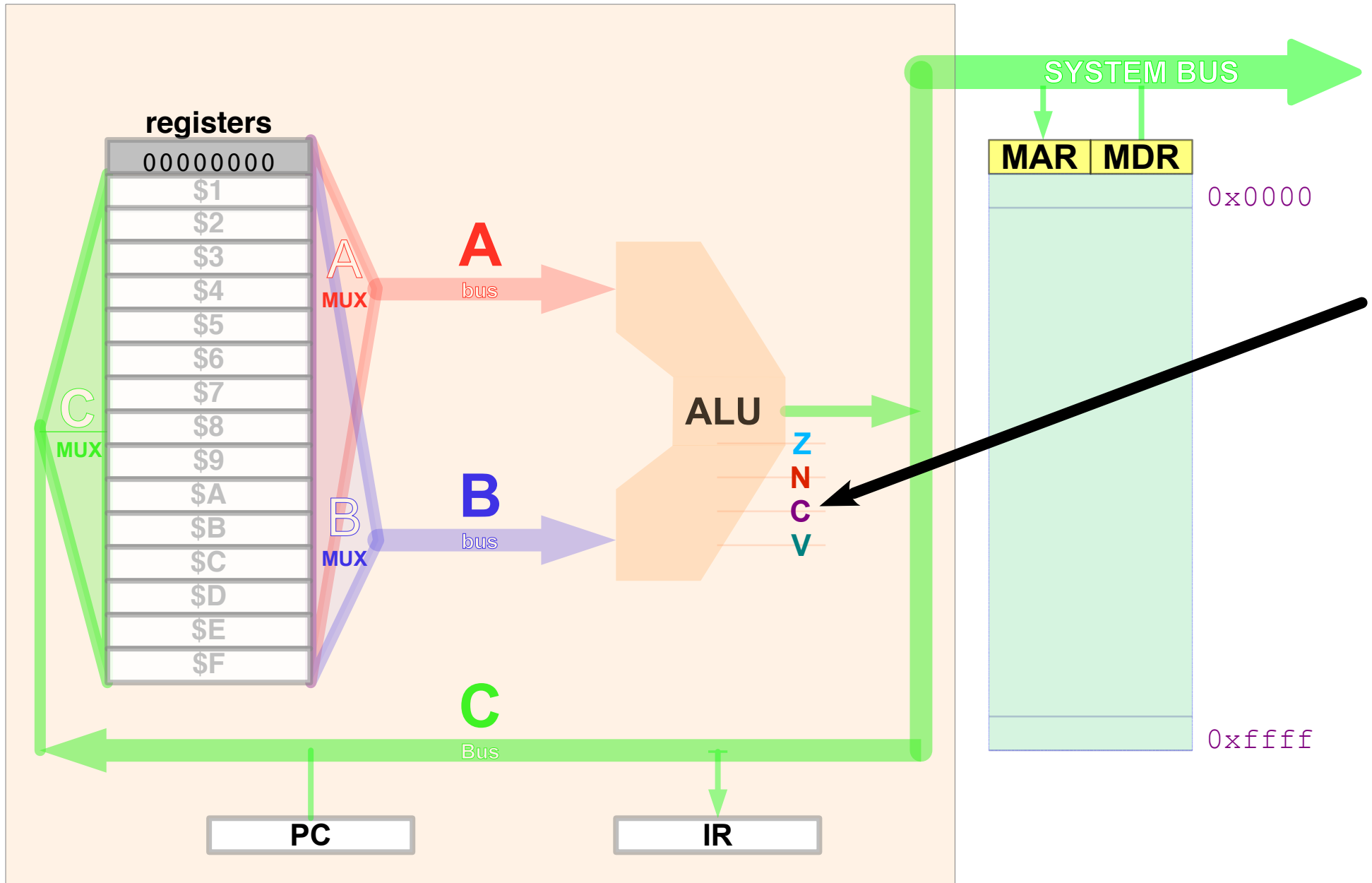

v — oVerflow condition flag

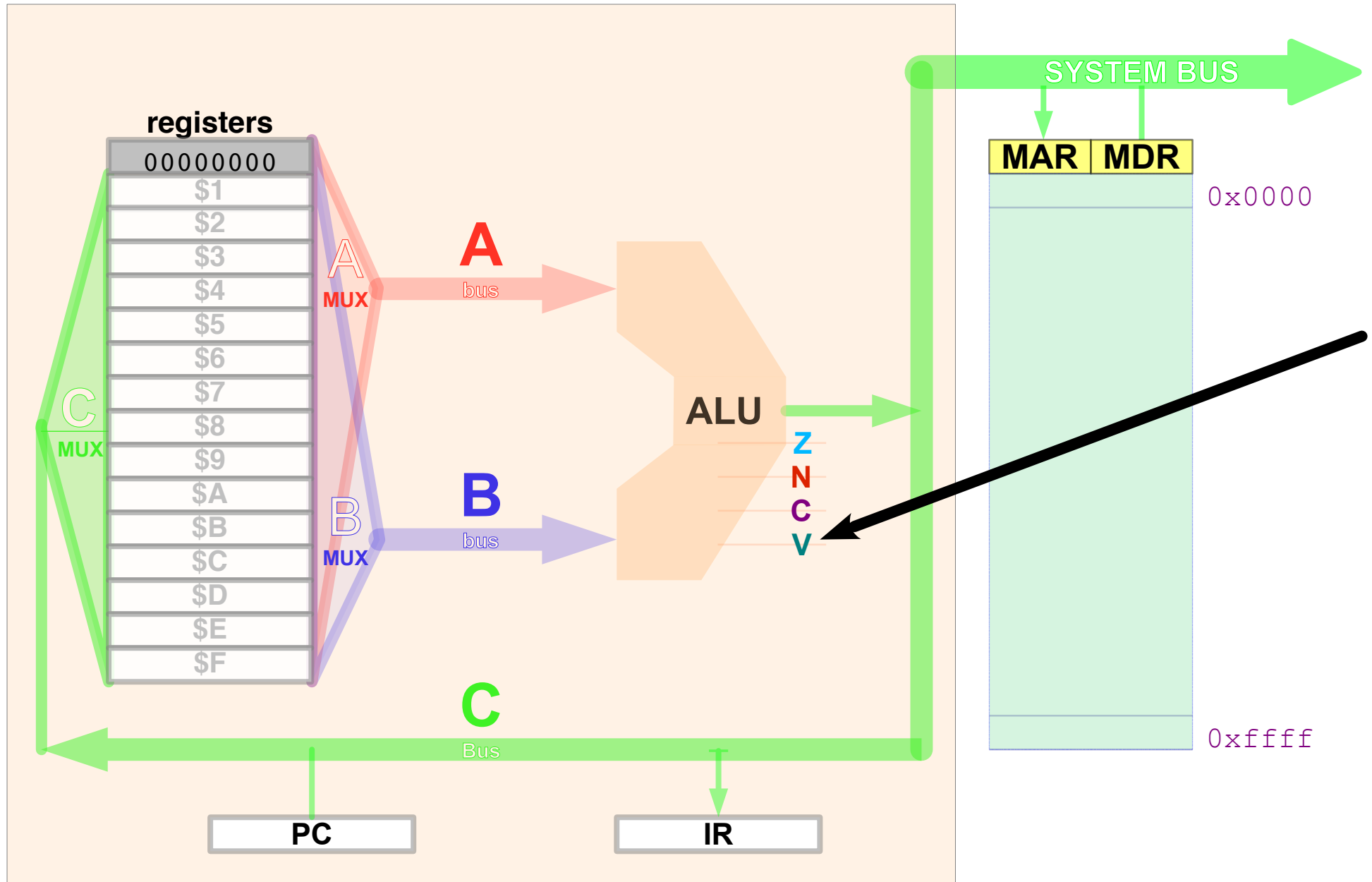

Core Combinational Circuit

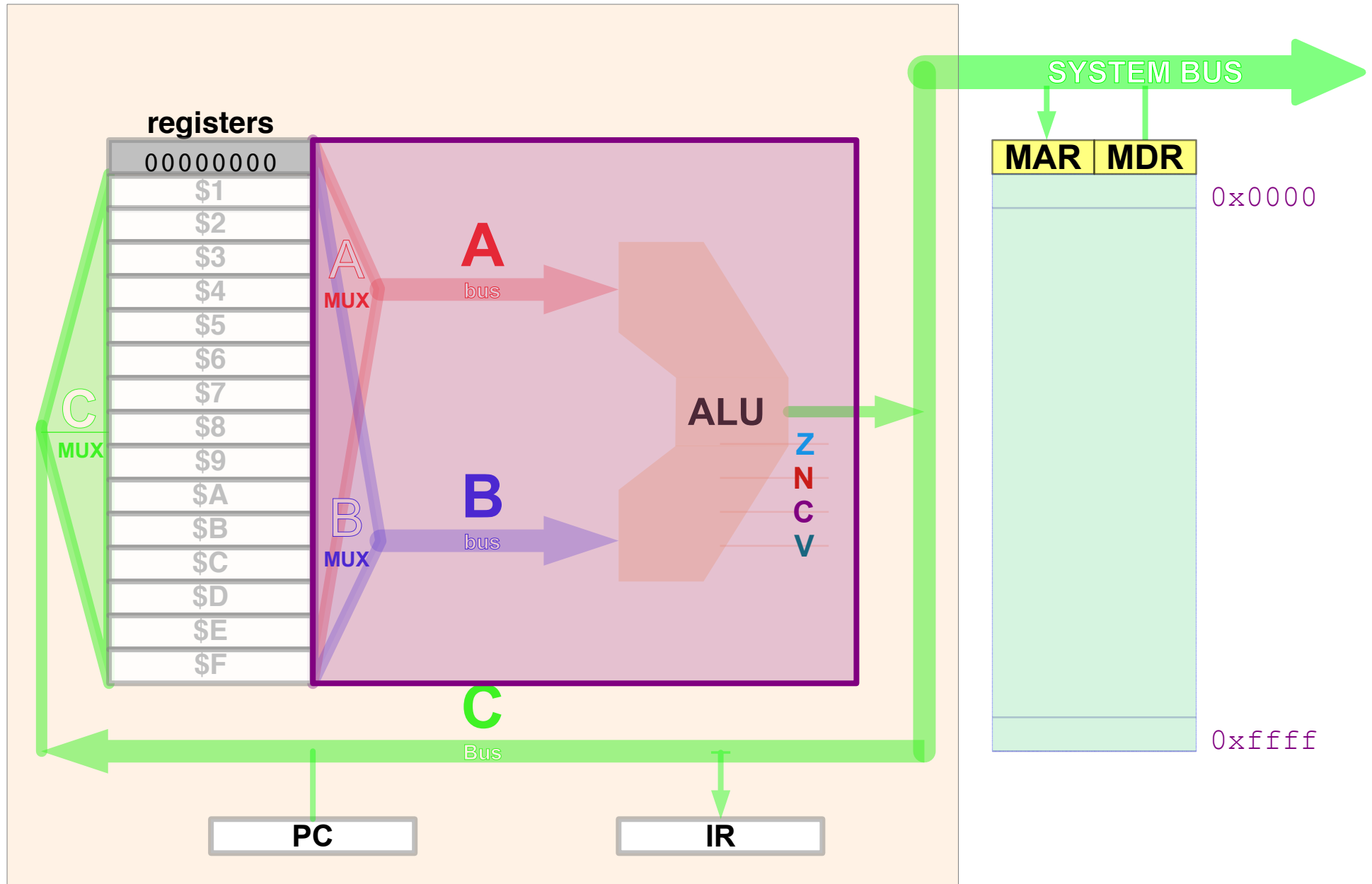

HW 7: $\mathbf{W} = \mathbf{X} + \mathbf{Y} + \mathbf{Z}$

Assignment: Write a **TOY** assembly language program to add the values of 3 variables, **X**, **Y**, and **Z**, in memory and store the sum in a fourth, **W**.

Details: The variables occupy consecutive words of memory starting with **W**. The address of **W** is in register **\$3**. *Do not change* the values in registers **\$0** through **\$3**. You can use registers **\$4** through **\$F** as you please.


Your program should consist entirely of addition (**add**), load (**l**), and store (**st**) instructions.

add	\$7, \$5, \$6	means	\$7	←	[\$5] + [\$6]
l	\$4, \$C, 8	means	\$4	←	MEM[[\$C]+8]
st	\$4, \$C, 8	means	[\$4]	→	MEM[[\$C]+8]

fetch

add \$7, \$5, \$6


execute

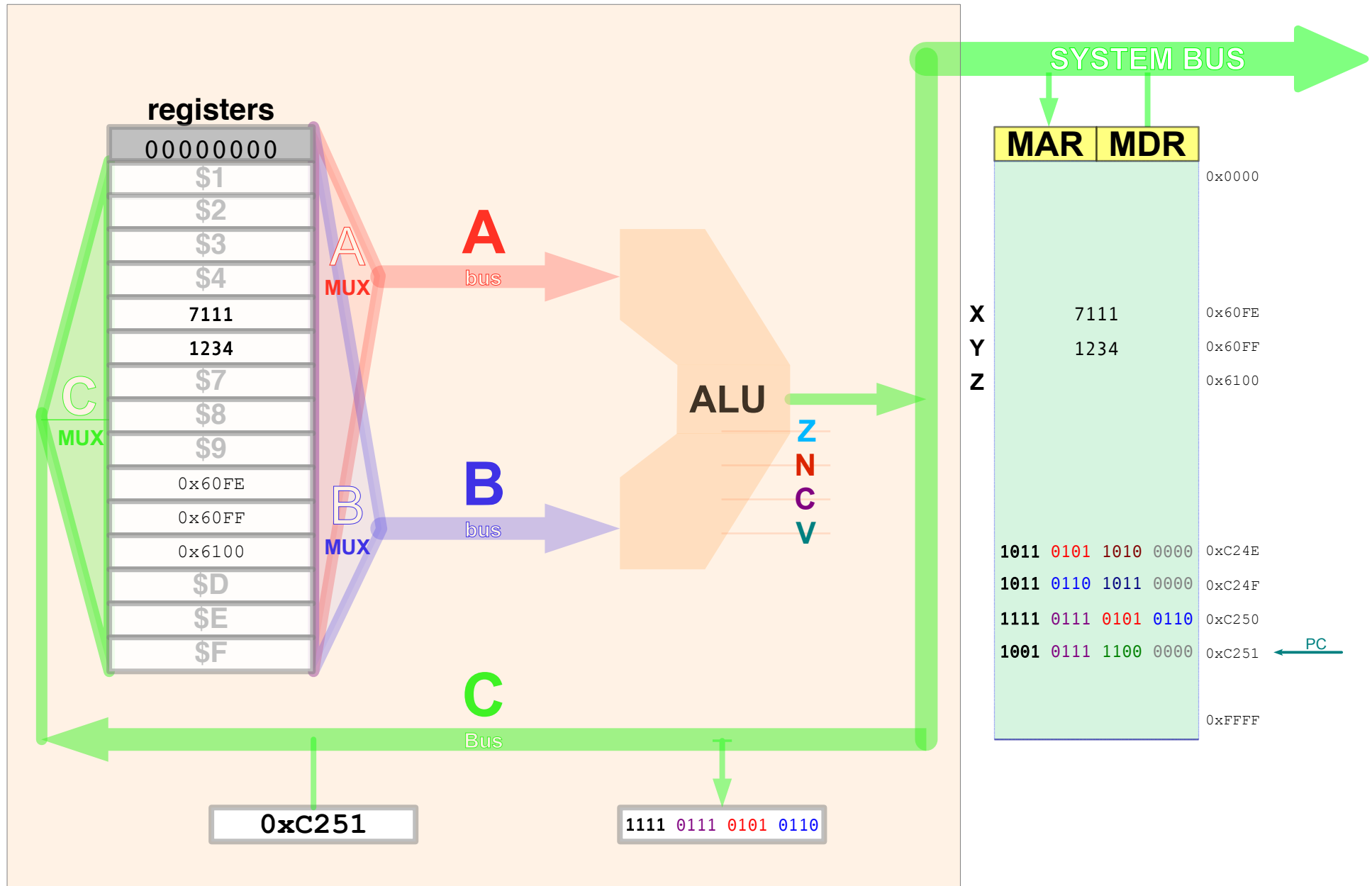

execute

The T₀Y Computer

fetch

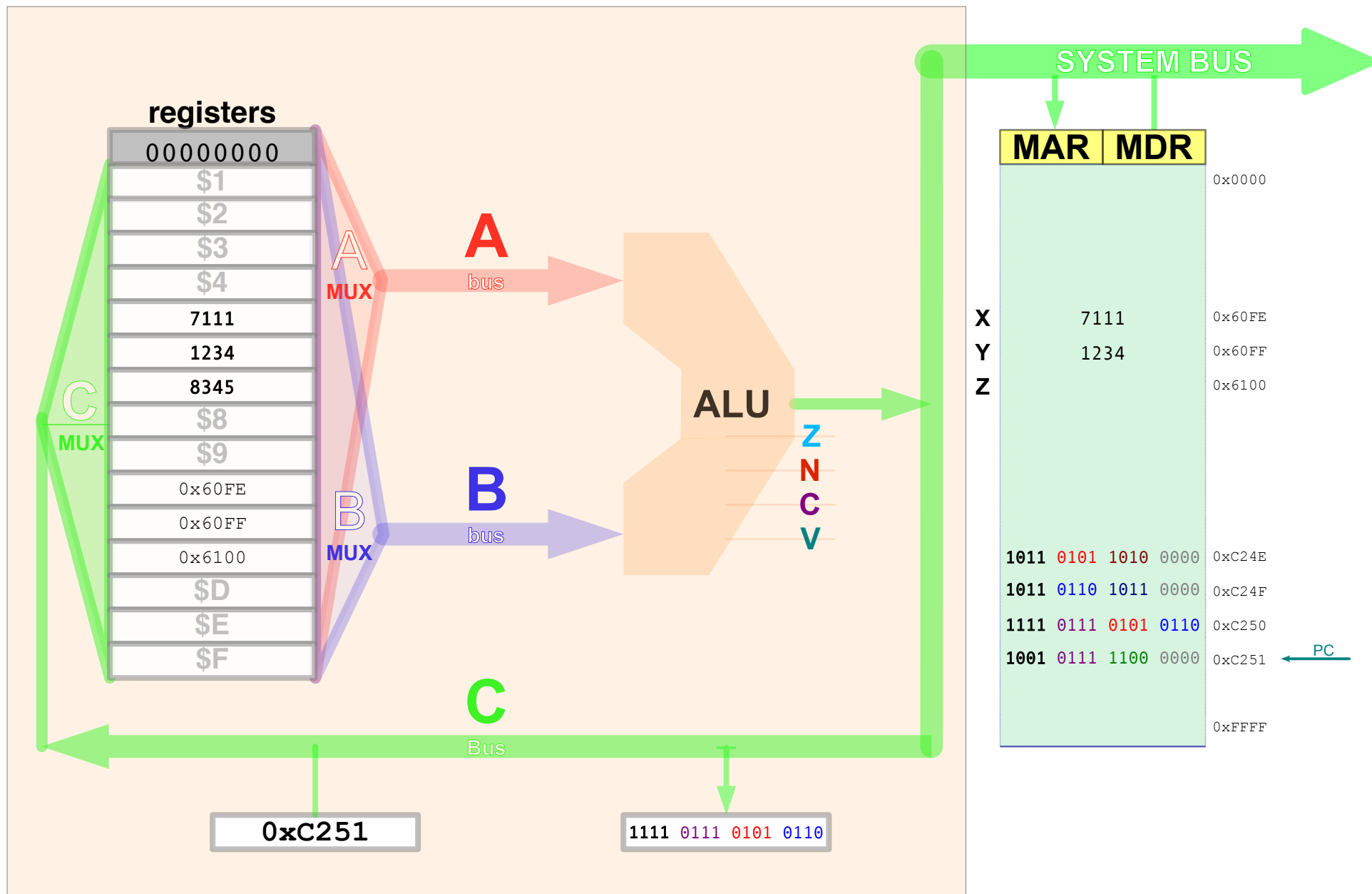

Immediate values

- s8 — 8-bit signed immediate
- u4 — 4-bit unsigned immediate
- cc — 4-bit condition code

Register File 16 16-bit “registers”

- 15 real registers: \$1 ... \$F
- 1 pseudo-register: \$0 [\$0] = 0

Main Memory 65536 16-bit words

- M[n] – nth memory address
- ^M[n] – content of M[n]

Instructions⁰

- add \$T ← [\$A] + [\$B]¹
- and \$T ← [\$A] & [\$B]¹
- bc PC ← [PC] + s8 *iff* cc
- bcl \$L ← [PC], PC ← [\$A]¹ *iff* cc
- l \$T ← ^M[[\$A] + u4]¹
- lwr \$T ← ^M[[\$A] + u4]¹ *set* rsvn
- lih \$T_{15..8} ← s8¹
- lis \$T ← s8¹ (sign extended)
- nor \$T ← $\overline{[\$A] \mid [\$B]}^1$
- sl \$T ← [\$A] << u4¹
- srs \$T ← [\$A] >> u4¹
- sru \$T ← [\$A] >>> u4¹
- st M[[\$A] + u4] ← [\$S]
- stc M[[\$A] + u4] ← [\$S]⁴ *iff* rsvn
- sub \$T ← [\$A] - [\$B]^{1,2}
- sys system call

Arithmetic / Logical				
1111	add	\$T	\$A	\$B
1110	sub	\$T	\$A	\$B
1101	and	\$T	\$A	\$B
1100	nor	\$T	\$A	\$B

Load /Store				
1011	l	\$T	\$A	u4
1010	lwr	\$T	\$A	u4
1001	st	\$S	\$A	u4
1000	stc	\$S	\$A	u4

Shift / Branch & Link				
0111	sru	\$T	\$A	u4
0110	srs	\$T	\$A	u4
0101	bcl	cc	\$A	\$L
0100	sl	\$T	\$A	u4

Immediate				
0011	lih	\$T		s8
0010	lis	\$T		s8
0001	bc	cc		s8
0000	sys	\$X		s8

Condition Codes		
1111	$\overline{znv} + nv$	SGT
1110	$n\overline{v} + \overline{nv}$	SLT
1101	n	NEG
1100	v	OVF
1011	\overline{zc}	UGT
1010	\overline{c}	ULT
1001	\overline{z}	NE
1000	0	NOP
0111	$z + n\overline{v} + \overline{nv}$	SLE
0110	$nv + \overline{nv}$	SGE
0101	\overline{n}	POS
0100	\overline{v}	NVF
0011	$z + \overline{c}$	ULE
0010	c	UGE
0001	z	EQ
0000	1	ALL

Notes

⁰ PC ← PC+1 *before* instruction execution

¹ \$0 *not* changed ([\$0] = 0 always)

² Determines flags: z, n, c, v

⁴ Determines flag: v

TOY ALU Instructions

Addition

add \$9, \$6, \$5 **1111** 1001 0110 0101
 $\$9 = [\$6] + [\$5]$

Subtraction

sub \$9, \$6, \$5 **1110** 1001 0110 0101
 $\$9 = [\$6] - [\$5] = [\$6] + \overline{[\$5]} + 1$

And

and \$9, \$6, \$5 **1101** 1001 0110 0101
 $\$9 = [\$6] \& [\$5]$

Not-Or **[De Morgan's law: $\sim(A \mid B) = (\sim A) \& (\sim B)$]**

nor \$9, \$6, \$5 **1100** 1001 0110 0101
 $\$9 = \overline{[\$6]} \& \overline{[\$5]}$

(1-bit) Full Adder Circuit Design

Combinational circuit

Output determined by input

Design process

1. Specify semantics

Black Box: *input* and *output* (informal semantics)

Truth Table (formal semantics)

2. Truth table \rightarrow Boolean formula

3. Minimize boolean formula (optional)

Boolean algebra

Karnaugh maps

4. Boolean formula \rightarrow combinational circuit

(1-bit) Full Adder Circuit Design

Combinational circuit

Output determined by input

Design process

1. Specify semantics

Black Box: *input* and *output* (informal semantics)

Truth Table (formal semantics)

2. Truth table \rightarrow Boolean formula

3. Minimize boolean formula (optional)

Boolean algebra

Karnaugh maps

4. Boolean formula \rightarrow combinational circuit

(1-bit) Full Adder Circuit Design

Combinational circuit

Output determined by input

Design process

1. Specify semantics

Black Box: *input and output* (informal semantics)

Truth Table

(formal semantics)

2. Truth table \rightarrow Boolean formula


3. Minimize boolean formula (optional)

Boolean algebra

Karnaugh maps

4. Boolean formula \rightarrow combinational circuit

Full Adder Black Box

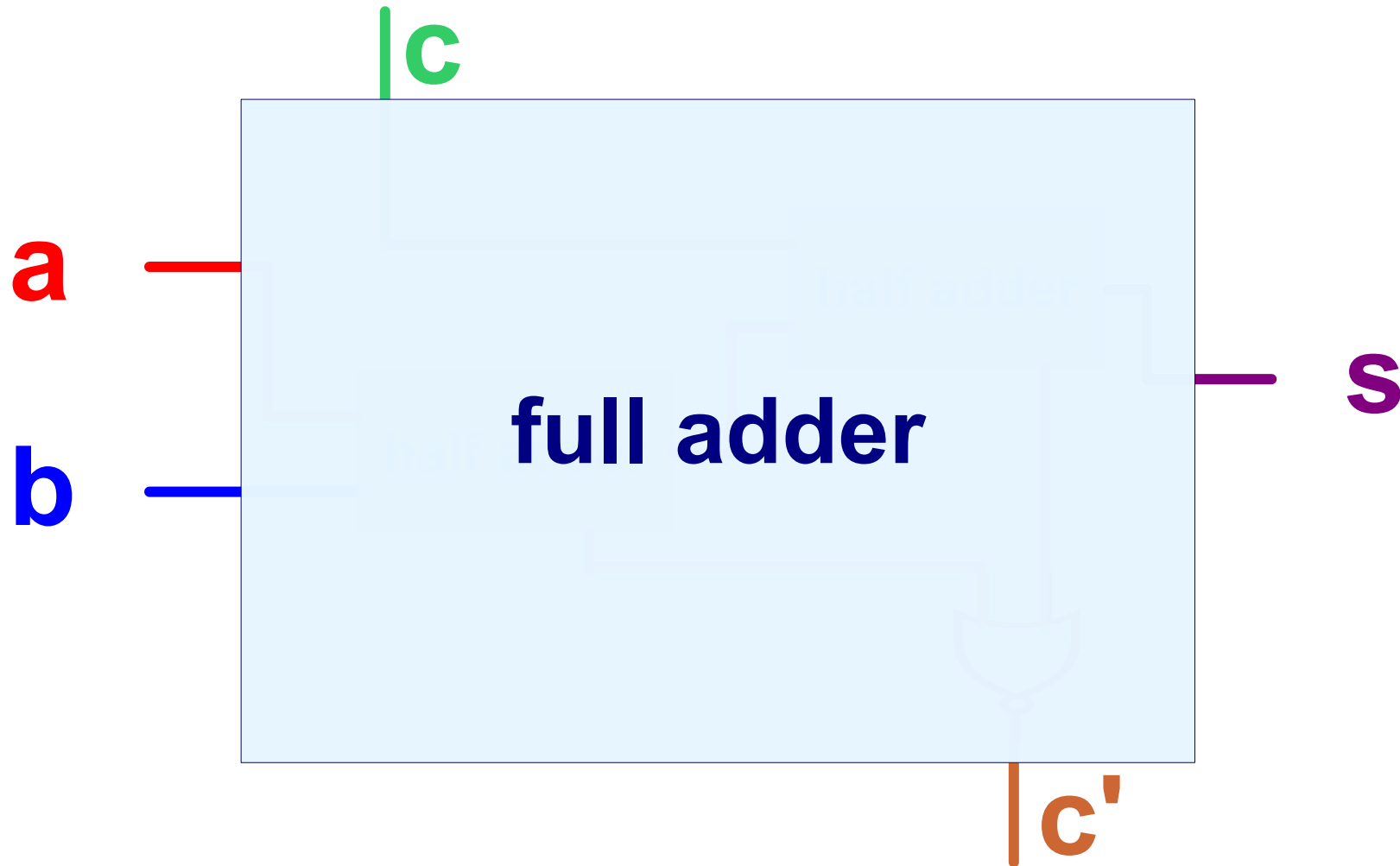

Sum 3 1-bit inputs to give a 2-bit output

(1-bit) Full Adder Circuit Design

Combinational circuit

Output determined by input

Design process

1. Specify semantics

Black Box: *input* and *output* (informal semantics)

Truth Table (formal semantics)

2. Truth table \rightarrow Boolean formula

3. Minimize boolean formula (optional)

Boolean algebra

Karnaugh maps

4. Boolean formula \rightarrow combinational circuit

Full Adder Truth Table

The diagram illustrates the eight possible input combinations for a full adder, arranged in two rows of four. Each combination is shown as a vertical addition problem. The top row shows the first four combinations, and the bottom row shows the next four. The inputs are the two numbers being added, and the result is shown below a horizontal line. The carry-in is indicated by a green arrow pointing to the top-right input, and the carry-out is indicated by a black arrow pointing from the top-right input to the top-left input of the next combination.

Carry In	A	B	Sum	Carry Out
0	1	0	1	0
0	1	1	0	1
0	0	1	1	0
0	0	0	0	0
1	1	0	0	1
1	1	1	1	1
1	0	1	1	1
1	0	0	1	0

Full Adder Truth Table

#	a	b	c	c'	s
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

(1-bit) Full Adder Circuit Design

Combinational circuit

Output determined by input

Design process

1. Specify semantics

Black Box: *input* and *output* (informal semantics)

Truth Table (formal semantics)

2. Truth table \rightarrow Boolean formula

3. Minimize boolean formula (optional)

Boolean algebra

Karnaugh maps

4. Boolean formula \rightarrow combinational circuit

Full Adder Truth Table

#	a	b	c	c'	s
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

Full Adder Boolean Formulas

#	a b c	c'	c'	s	s
0	0 0 0	0		0	
1	0 0 1	0		1	$\overline{a}bc$
2	0 1 0	0		1	$a\overline{b}c$
3	0 1 1	1	$\overline{a}bc$	0	
4	1 0 0	0		1	$a\overline{b}\overline{c}$
5	1 0 1	1	$a\overline{b}c$	0	
6	1 1 0	1	$ab\overline{c}$	0	
7	1 1 1	1	abc	1	abc

Full Adder Boolean Formulas

#	a	b	c	c'	c'	s	s
0	0	0	0	0		0	
1	0	0	1	0		1	$\overline{a}bc$
2	0	1	0	0		1	$a\overline{b}c$
3	0	1	1	1	$\overline{a}bc$	0	
4	1	0	0	0		1	$a\overline{b}c$
5	1	0	1	1	$a\overline{b}c$	0	
6	1	1	0	1	$ab\overline{c}$	0	
7	1	1	1	1	abc	1	abc

$$s = \overline{a}bc + \overline{a}b\overline{c} + a\overline{b}c + abc$$

$$c' = \overline{a}bc + a\overline{b}c + ab\overline{c} + abc$$

(1-bit) Full Adder Circuit Design

Combinational circuit

Output determined by input

Design process

1. Specify semantics

Black Box: *input* and *output* (informal semantics)

Truth Table (formal semantics)

2. Truth table \rightarrow Boolean formula

3. Minimize boolean formula (optional)

Boolean algebra

Karnaugh maps

4. Boolean formula \rightarrow combinational circuit

Full Adder Boolean Formulas

#	a	b	c	c'	s
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

$$s = \overline{a}bc + \overline{a}b\overline{c} + a\overline{b}c + a\overline{b}\overline{c}$$

$$c' = \overline{a}bc + a\overline{b}c + ab\overline{c} + abc$$

Full Adder Boolean Formulas

#	a	b	c	c'	s
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

$$s = \overline{a}\overline{b}c + \overline{a}b\overline{c} + a\overline{b}\overline{c} + abc$$

$$c' = \overline{a}bc + a\overline{b}c + ab\overline{c} + abc$$

$$= \overline{a}bc + a\overline{b}c + ab\overline{c} + abc + abc + abc$$

Full Adder Boolean Formulas

#	a	b	c	c'	s
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

$$s = \overline{a}bc + a\overline{b}c + ab\overline{c} + abc$$

$$c' = \overline{a}bc + a\overline{b}c + ab\overline{c} + abc$$

$$= \boxed{\overline{a}bc} + \boxed{a\overline{b}c} + \boxed{ab\overline{c}} + \boxed{abc}$$

Full Adder Boolean Formulas

#	a	b	c	c'	s
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

$$s = \overline{a}bc + a\overline{b}c + ab\overline{c} + abc$$

$$c' = \overline{a}bc + a\overline{b}c + ab\overline{c} + abc$$

$$= \boxed{\overline{a}bc} + \boxed{a\overline{b}c} + \boxed{ab\overline{c}} + \boxed{abc}$$

$$= bc + ac + ab$$

Full Adder Boolean Formulas

#	a	b	c	c'	s
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

$$s = \overline{a}b\overline{c} + \overline{a}b\overline{c} + a\overline{b}\overline{c} + abc$$

$$c' = bc + ac + ab$$

(1-bit) Full Adder Circuit Design

Combinational circuit

Output determined by input

Design process

1. Specify semantics

Black Box: *input* and *output* (informal semantics)

Truth Table (formal semantics)

2. Truth table → Boolean formula

3. Minimize boolean formula (optional)


Boolean algebra

Karnaugh maps

4. Boolean formula → combinational circuit


$$s = abc + \overline{a}b\overline{c} + \overline{a}\overline{b}c + a\overline{b}\overline{c}$$

$$c' = ab + ac + bc$$

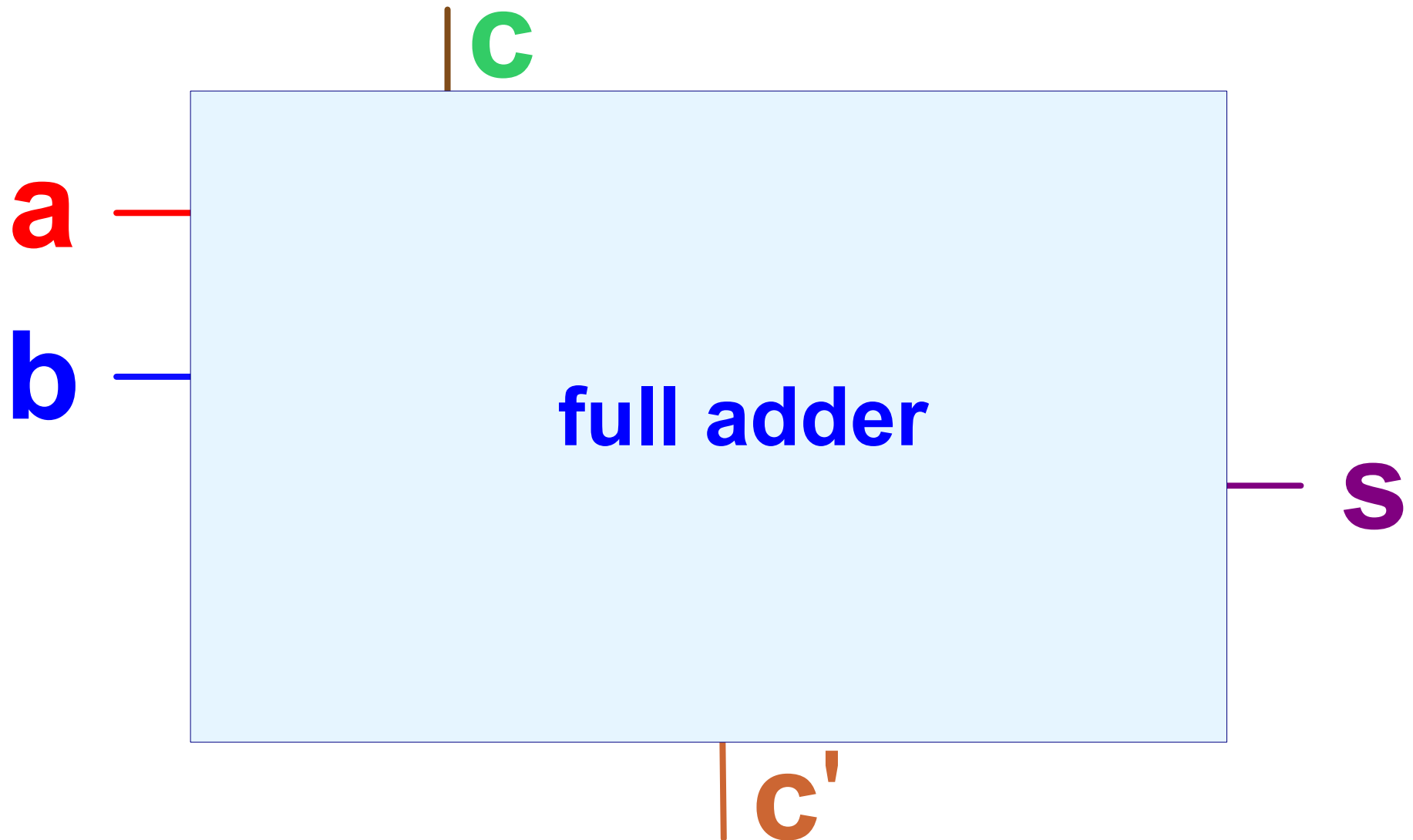


$$s = abc + \overline{a}b\overline{c} + \overline{a}\overline{b}c + a\overline{b}\overline{c}$$

$$c' = ab + ac + bc$$

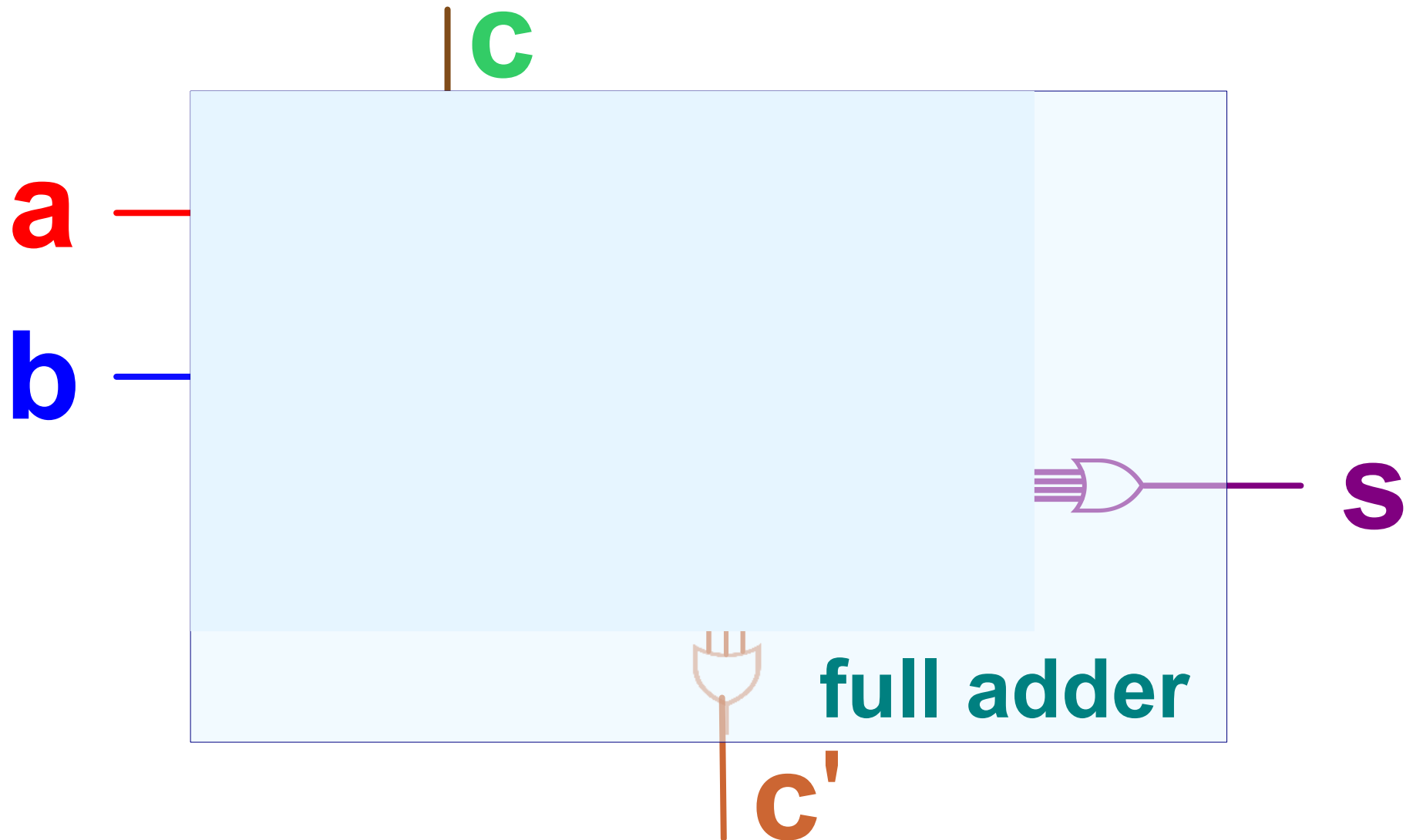


$$s = abc + \overline{a}bc + \overline{a}\overline{b}c + a\overline{b}c$$

$$c' = ab + ac + bc$$

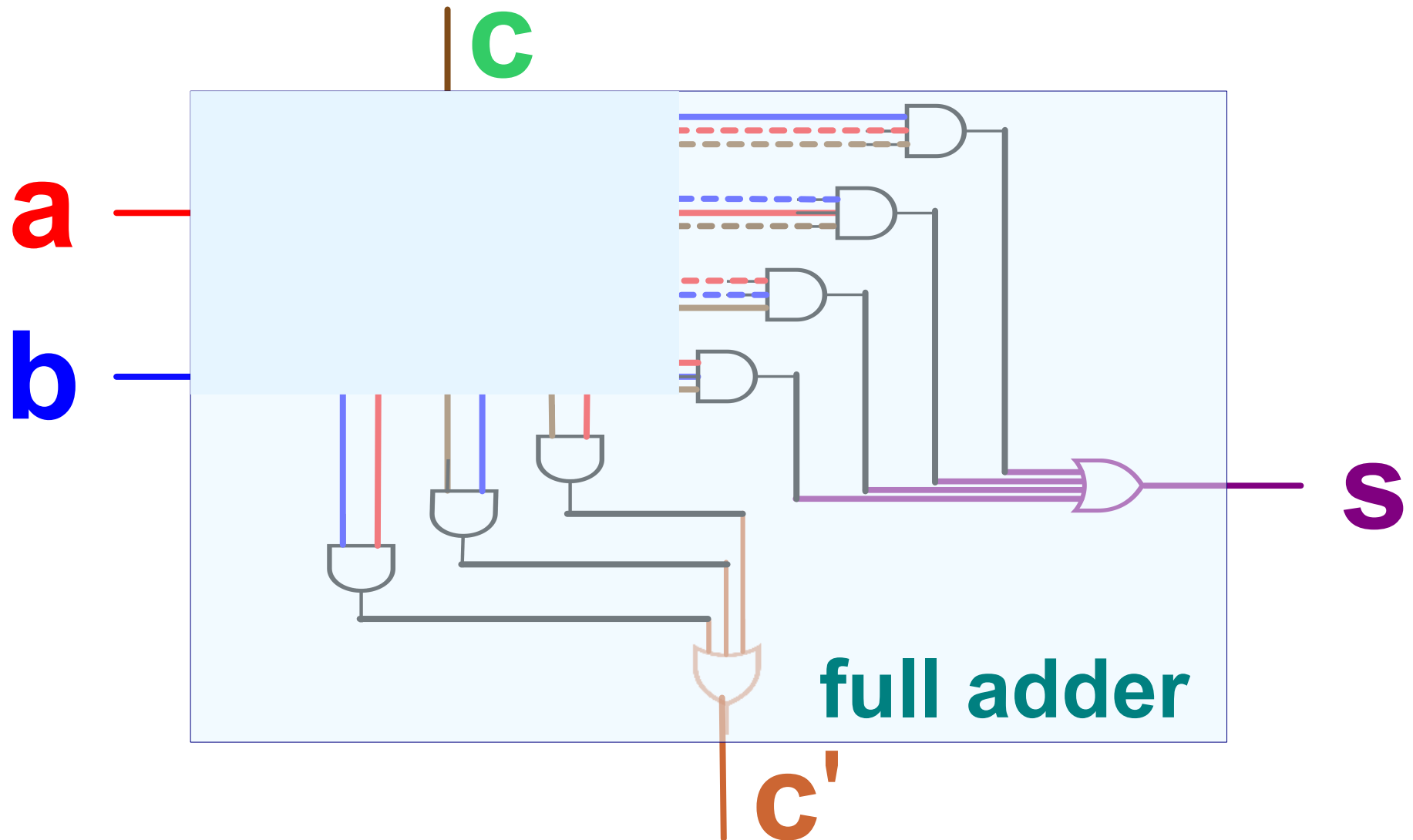


$$s = abc + \overline{a}b\overline{c} + \overline{a}\overline{b}c + a\overline{b}\overline{c}$$

$$c' = ab + ac + bc$$

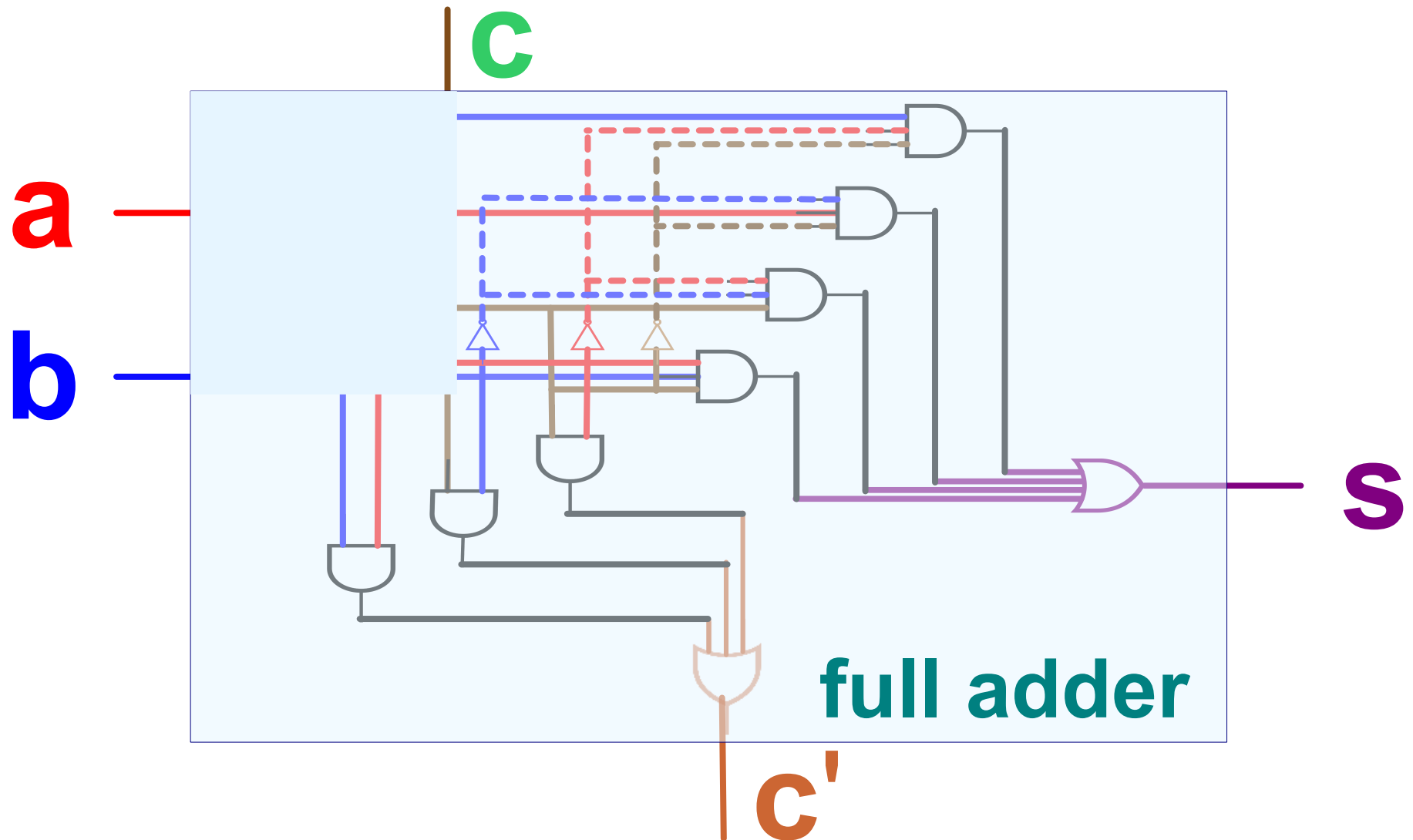

$$s = abc + \overline{a}bc + \overline{a}\overline{b}\overline{c} + a\overline{b}c$$

$$c' = ab + ac + bc$$

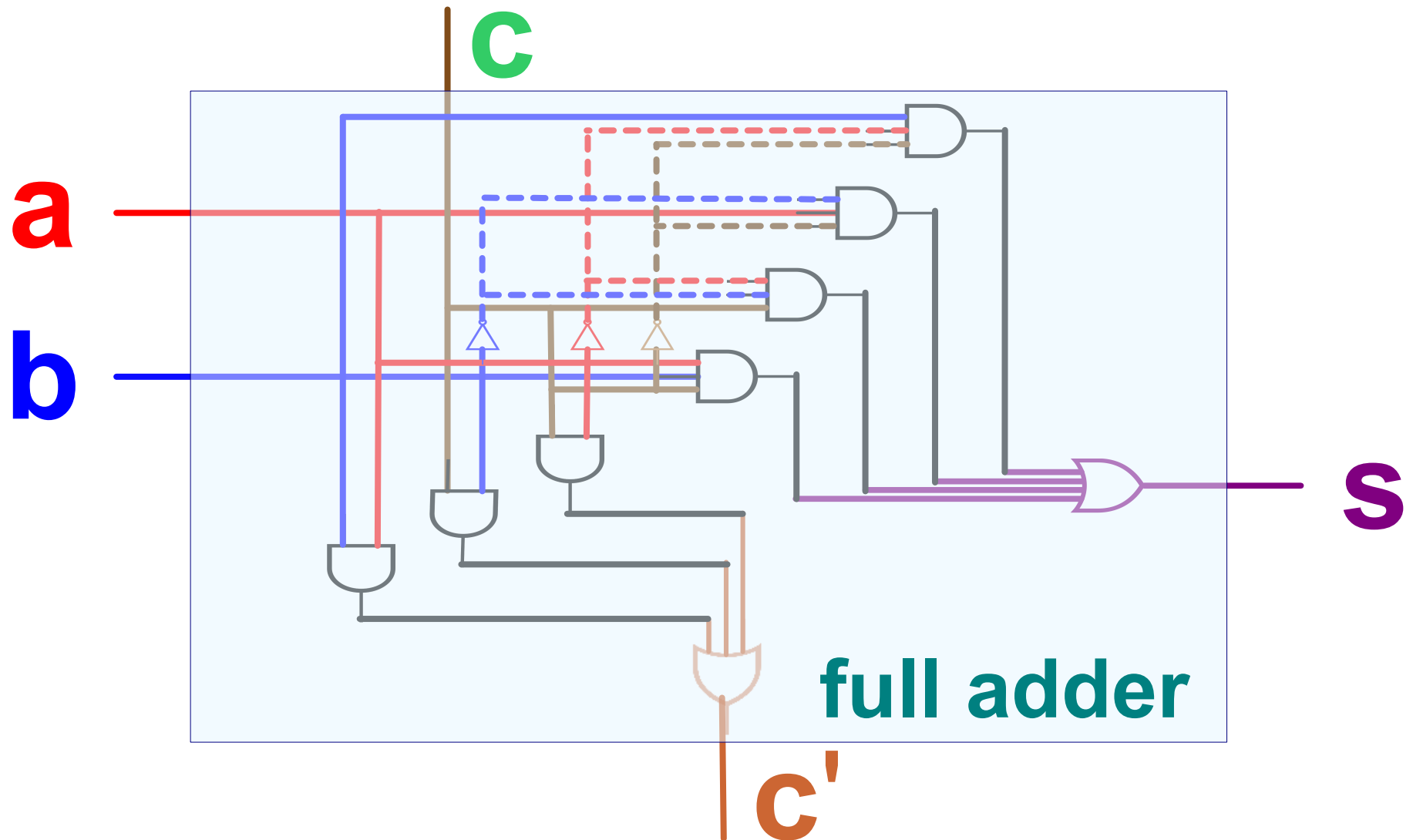

Inverters, Decoders, Multiplexer

Inverter: select data input or its negation

1 data input

1 selector input

1 output

Decoder: select unique output to be 1 (true)

N selector inputs

2^N outputs


Multiplexer: select unique data input to be output

2^N data inputs

N selector inputs


1 output

Inverter Black Box

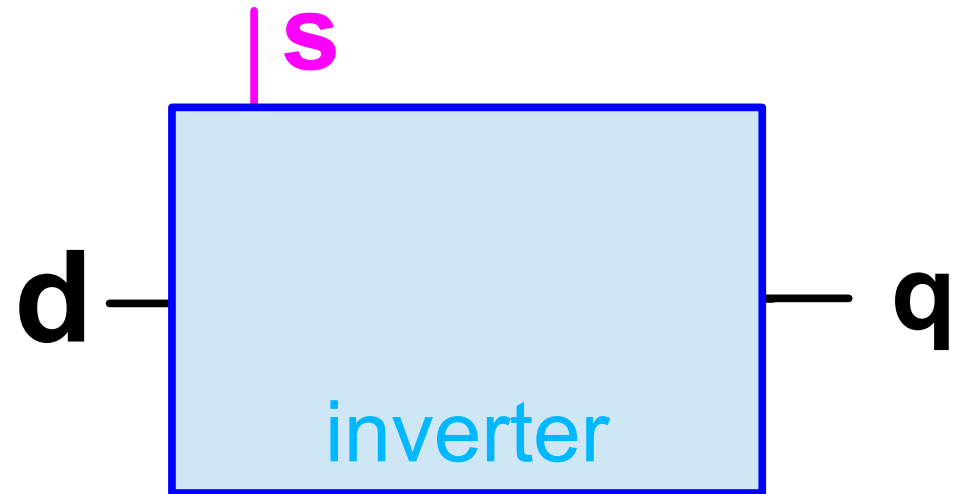


Inverter Truth Table

s	d	q
0	0	0
0	1	1
1	0	1
1	1	0

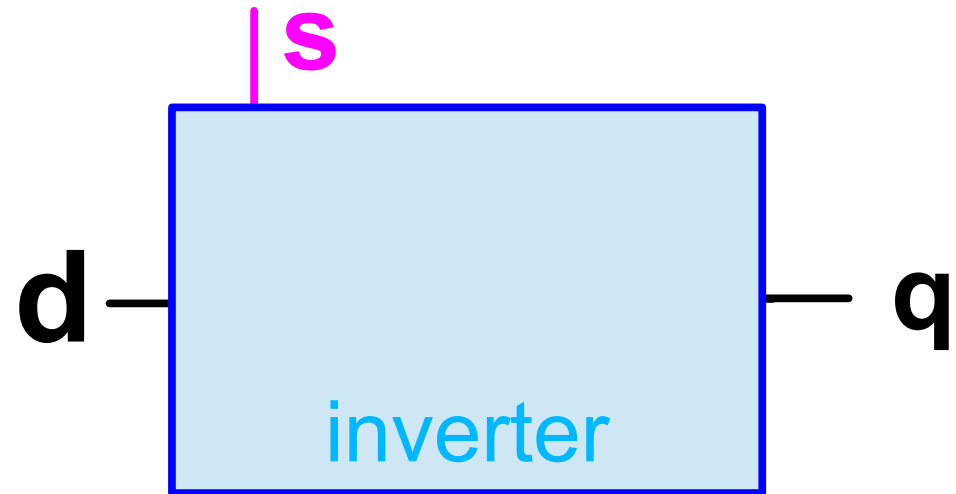

Inverter Formula


s	d	q
0	0	0
0	1	1
1	0	1
1	1	0

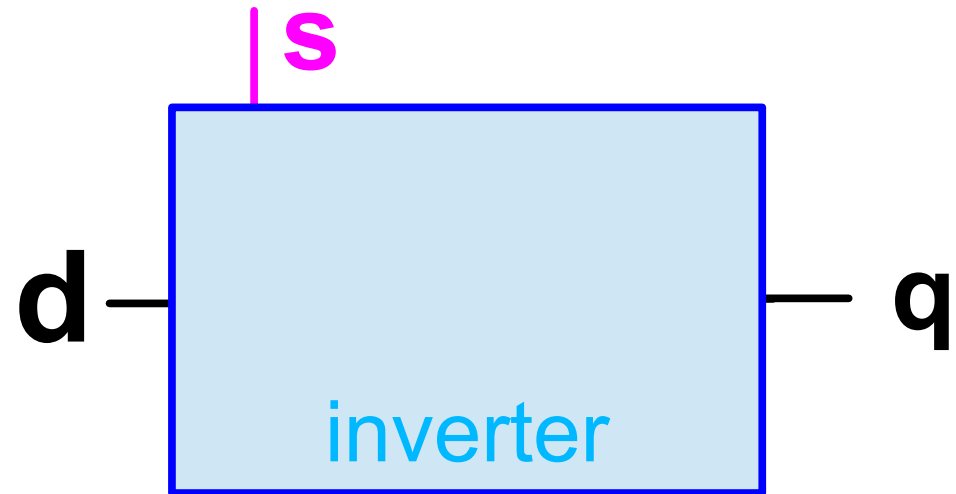

$$q = \bar{s}d + s\bar{d}$$

Inverter Circuit


s	d	q
0	0	0
0	1	1
1	0	1
1	1	0

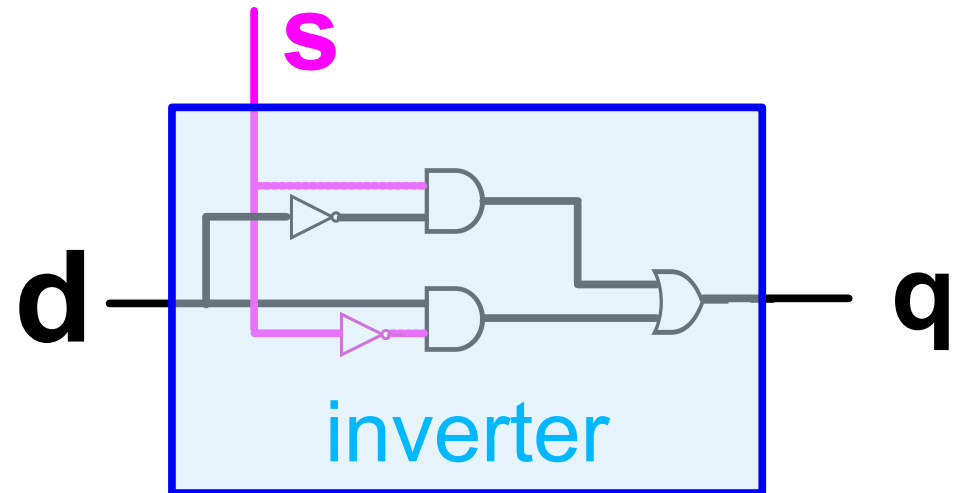


$$q = \bar{s}d + s\bar{d}$$

Inverter Component Icon

s	d	q
0	0	0
0	1	1
1	0	1
1	1	0

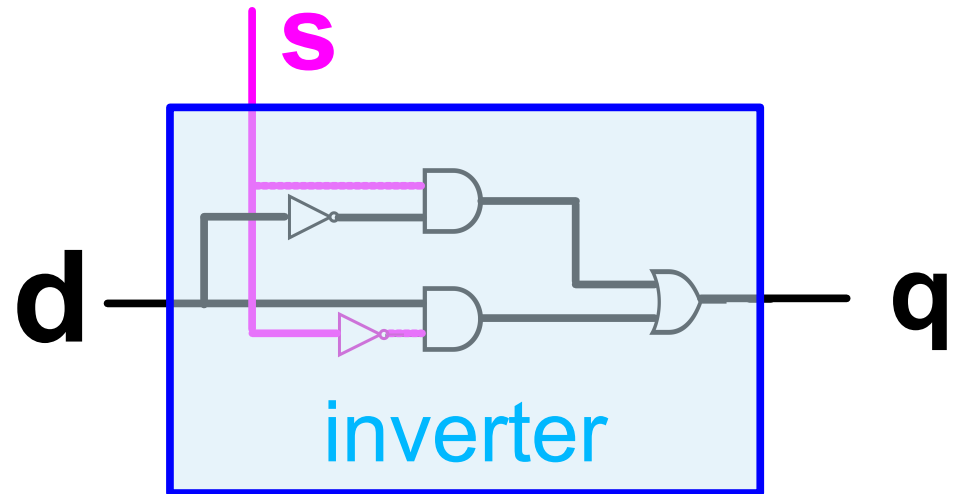

$$q = \bar{s}d + s\bar{d}$$

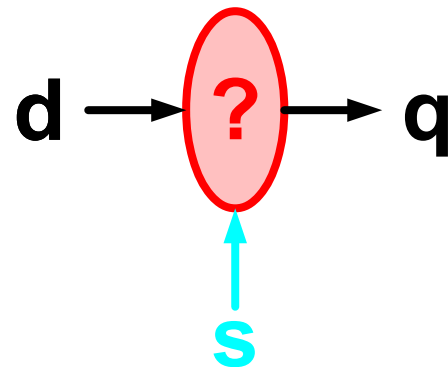



Inverter Summary

Inverter: select data input or its negation

1 data input

1 selector input

1 output

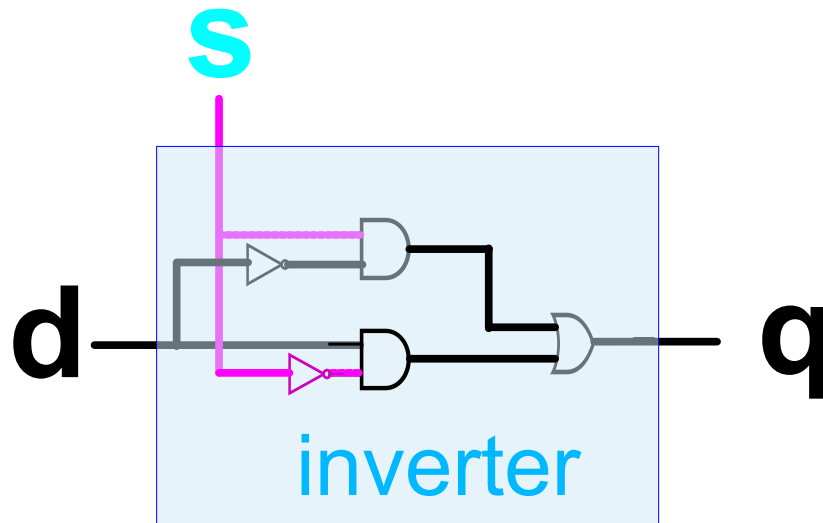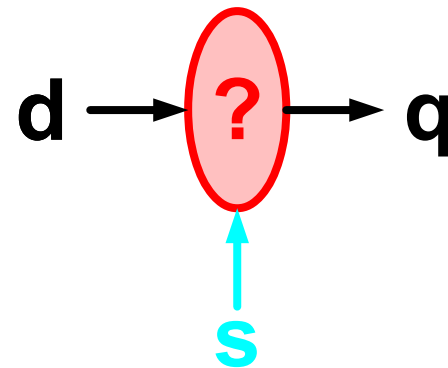

N-Bit Decoder

Each different combination of N input bits uniquely specifies one of 2^N outputs. An output is **1** if and only if the corresponding input combination is active (true). For any input, exactly one output is **1**.

N-Bit Decoder Truth Table:

- N input (**selector**) columns


- 2^N output columns

- 2^N rows

- Exactly one 1 in each output column


- Exactly one 1 in each output row

1-Bit Decoder Black Box

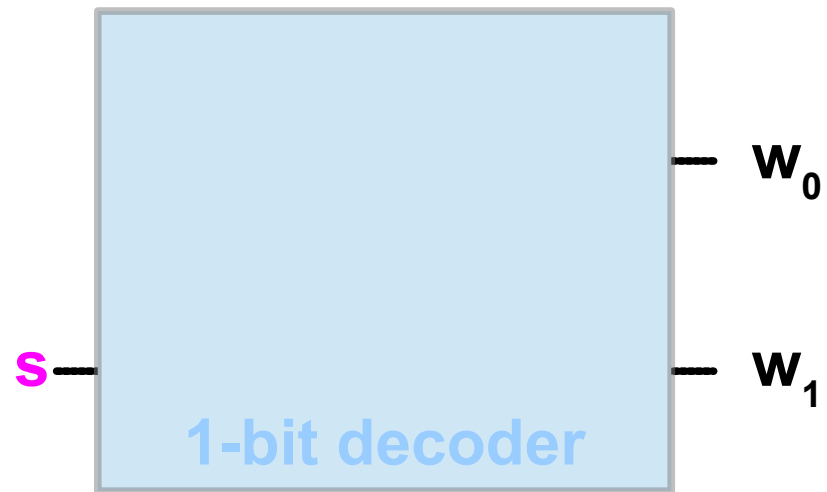


1-Bit Decoder Truth Table

s	w₀	w₁
0	1	0
1	0	1

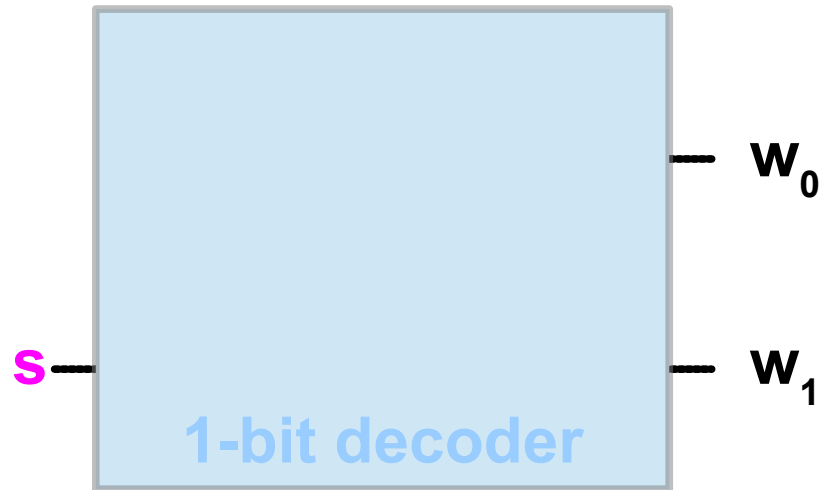

1-Bit Decoder Formulas

s	w₀	w₁
0	1	0
1	0	1

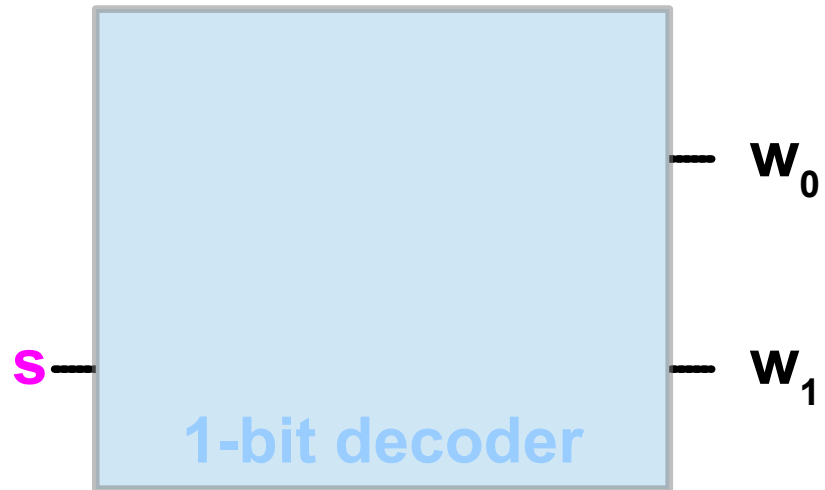


$$w_0 = \overline{s}$$

$$w_1 = s$$

1-Bit Decoder Circuit

s	w_0	w_1
0	1	0
1	0	1

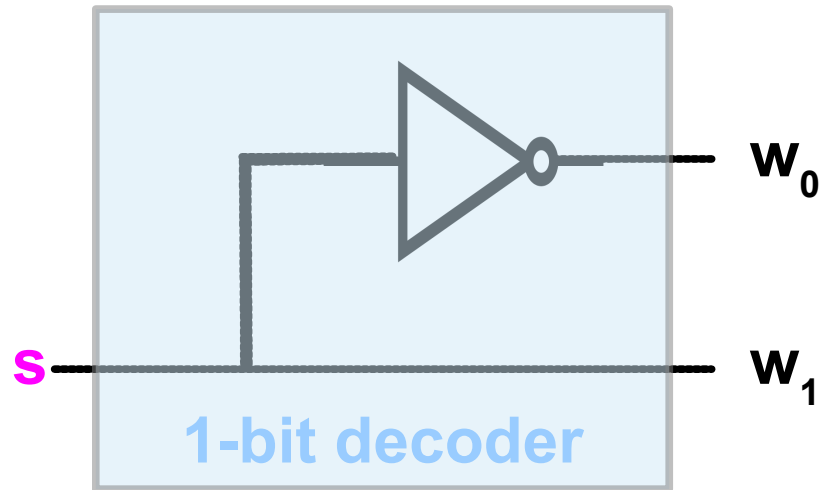


$$w_0 = \overline{s}$$

$$w_1 = s$$


1-Bit Decoder Component Icon

s	w₀	w₁
0	1	0
1	0	1

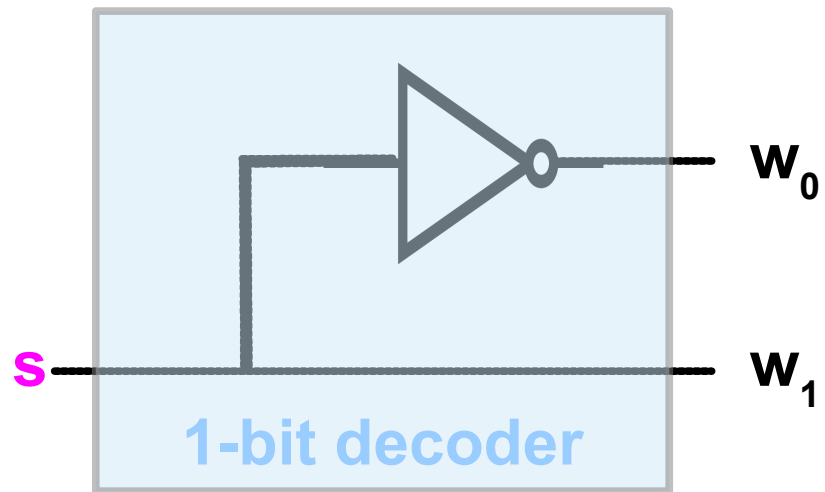


$$w_0 = \overline{s}$$

$$w_1 = s$$

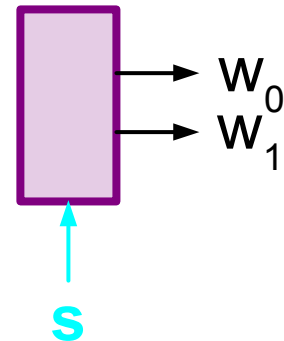

2-Bit Decoder

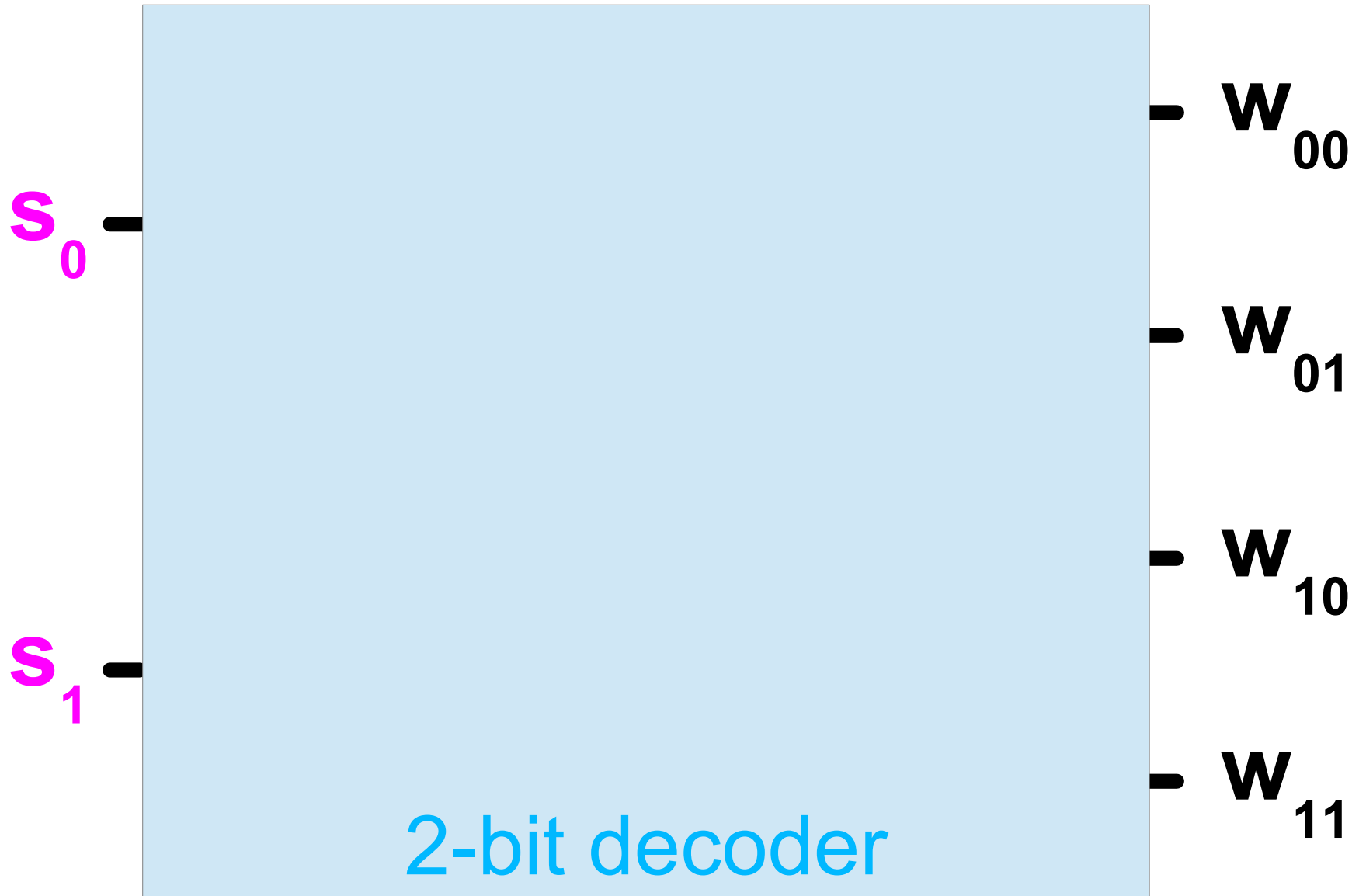

2-bit Decoder Truth Table

#	s_1	s_0	w_{00}	w_{01}	w_{10}	w_{11}
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1

2-bit Decoder Formulas

#	s_1	s_0	w_{00}	w_{01}	w_{10}	w_{11}
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1


$$w_{11} = s_1 \overline{s_0}$$

$$w_{10} = \overline{s_1} s_0$$


$$w_{01} = \overline{s_1} \overline{s_0}$$

$$w_{00} = s_1 s_0$$


2-Bit Decoder Circuit

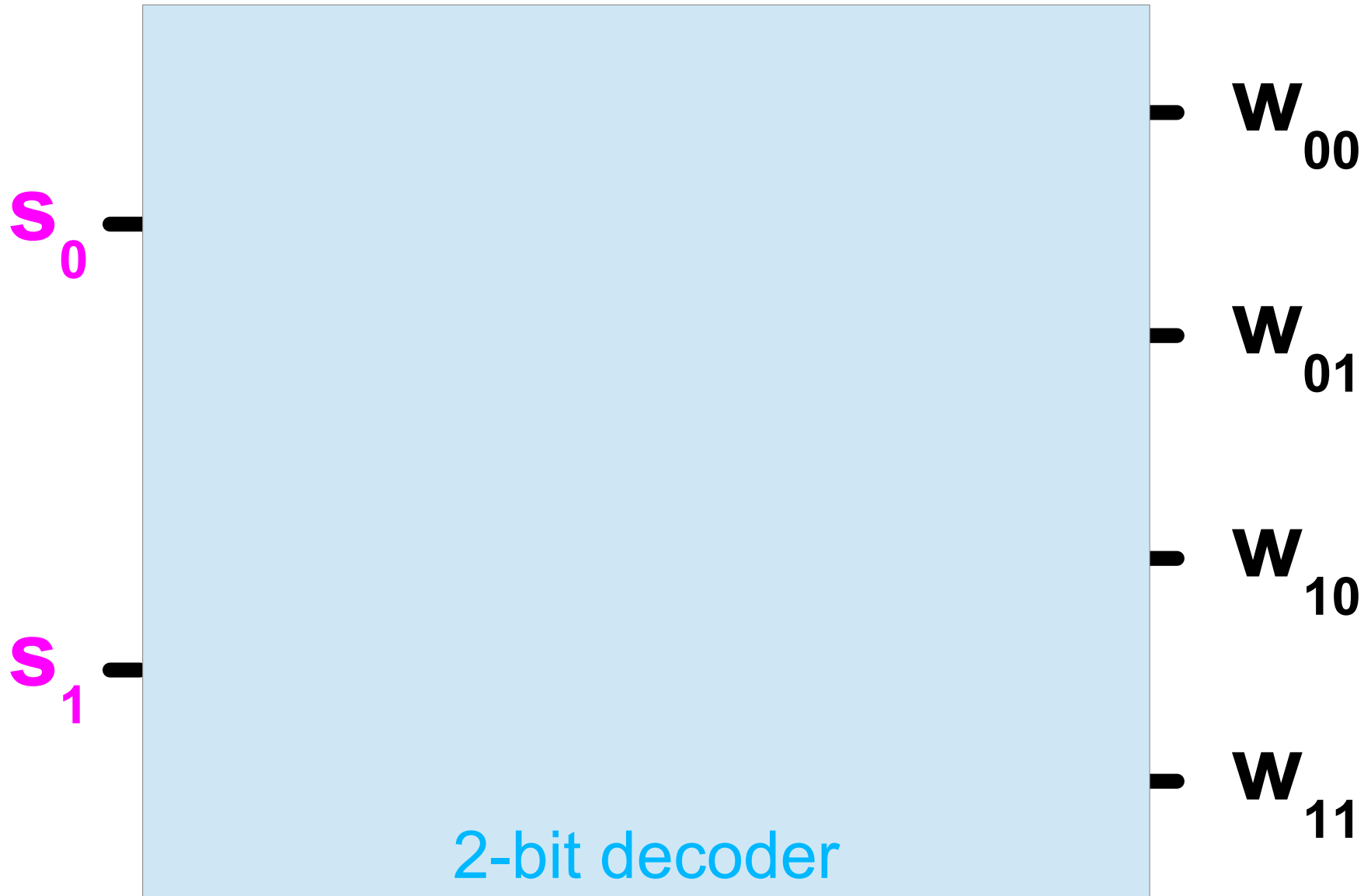


2-Bit Decoder Circuit

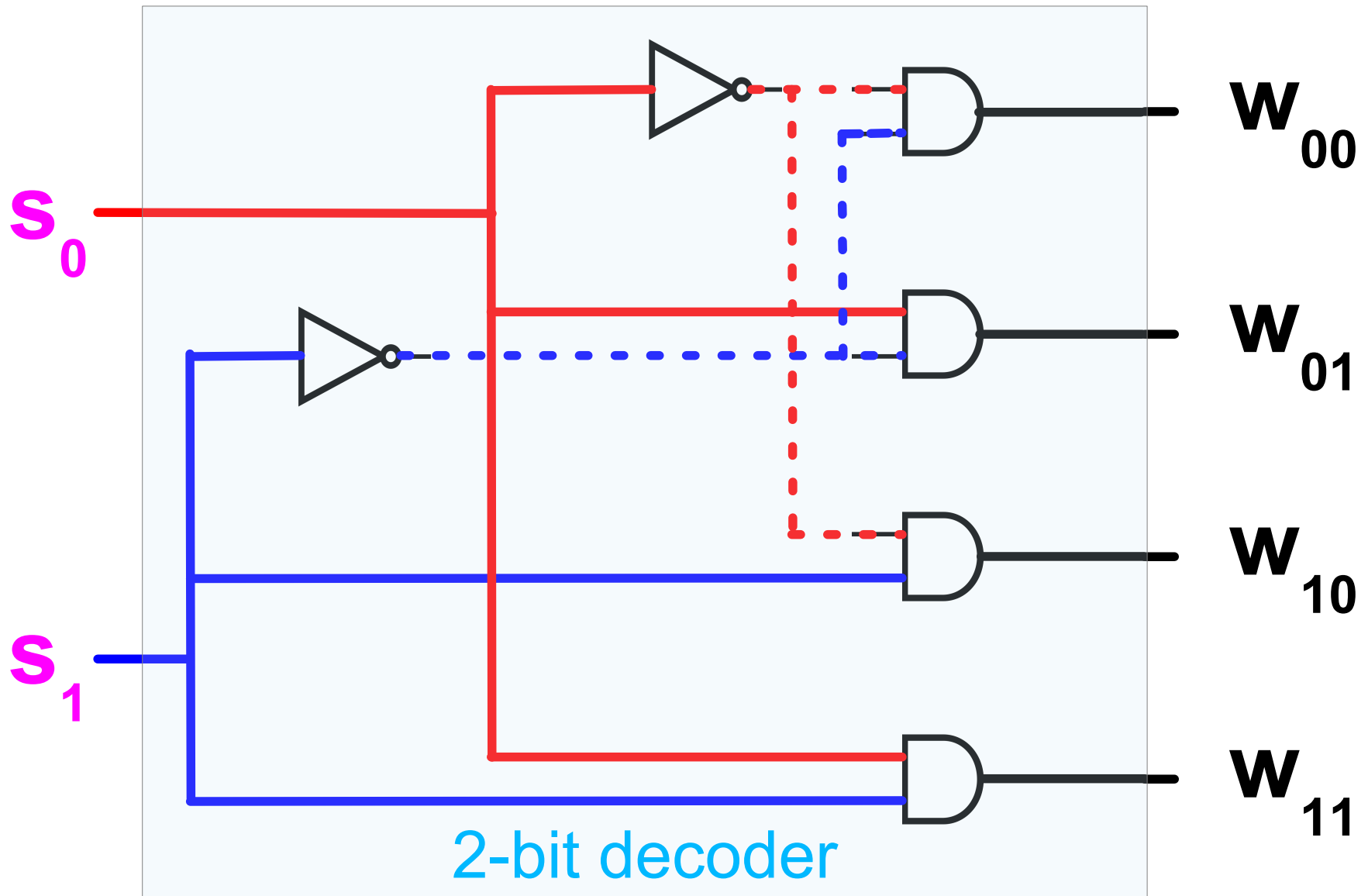

2-Bit Decoder Circuit

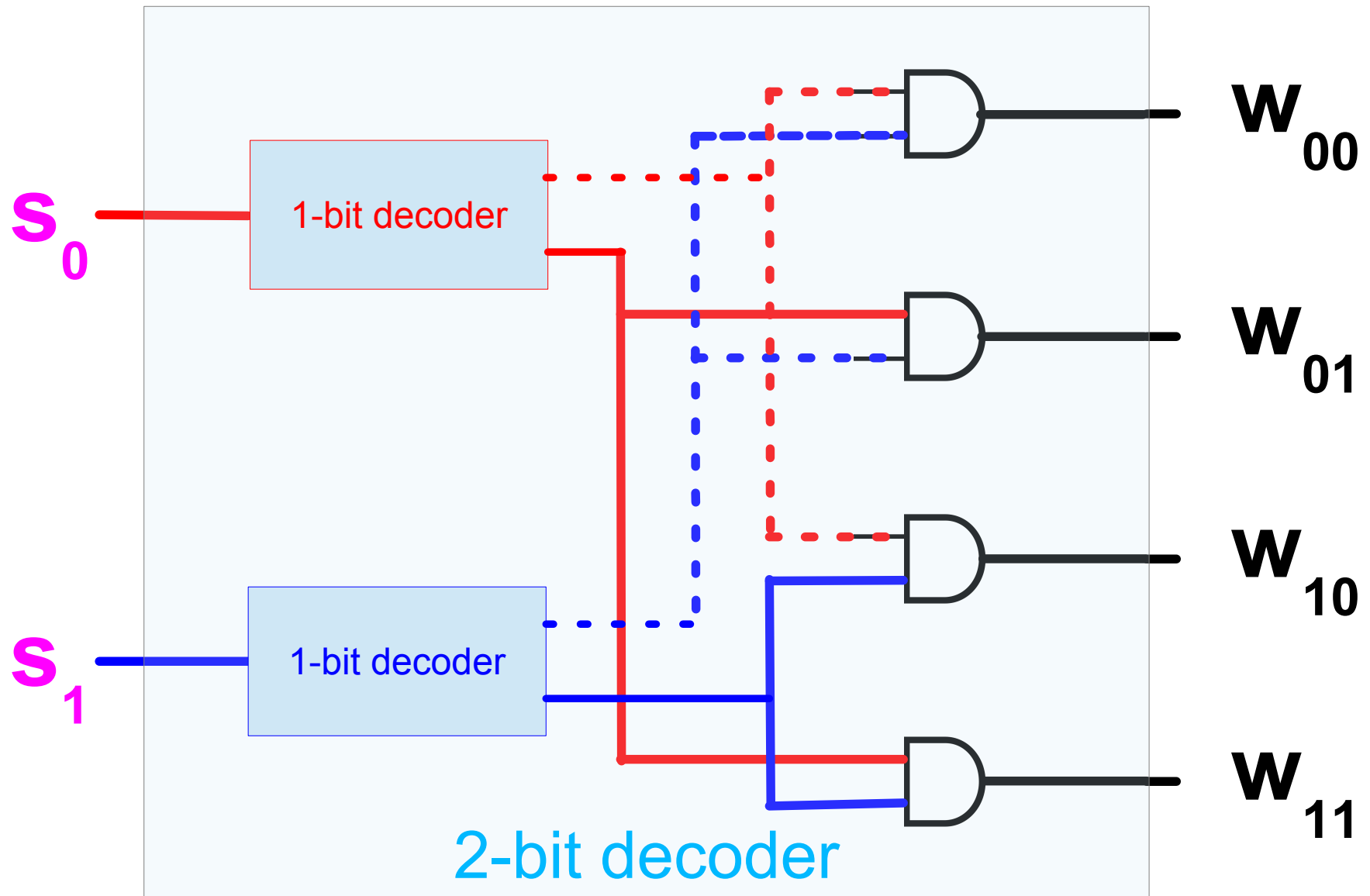

3-Bit Decoder Black Box

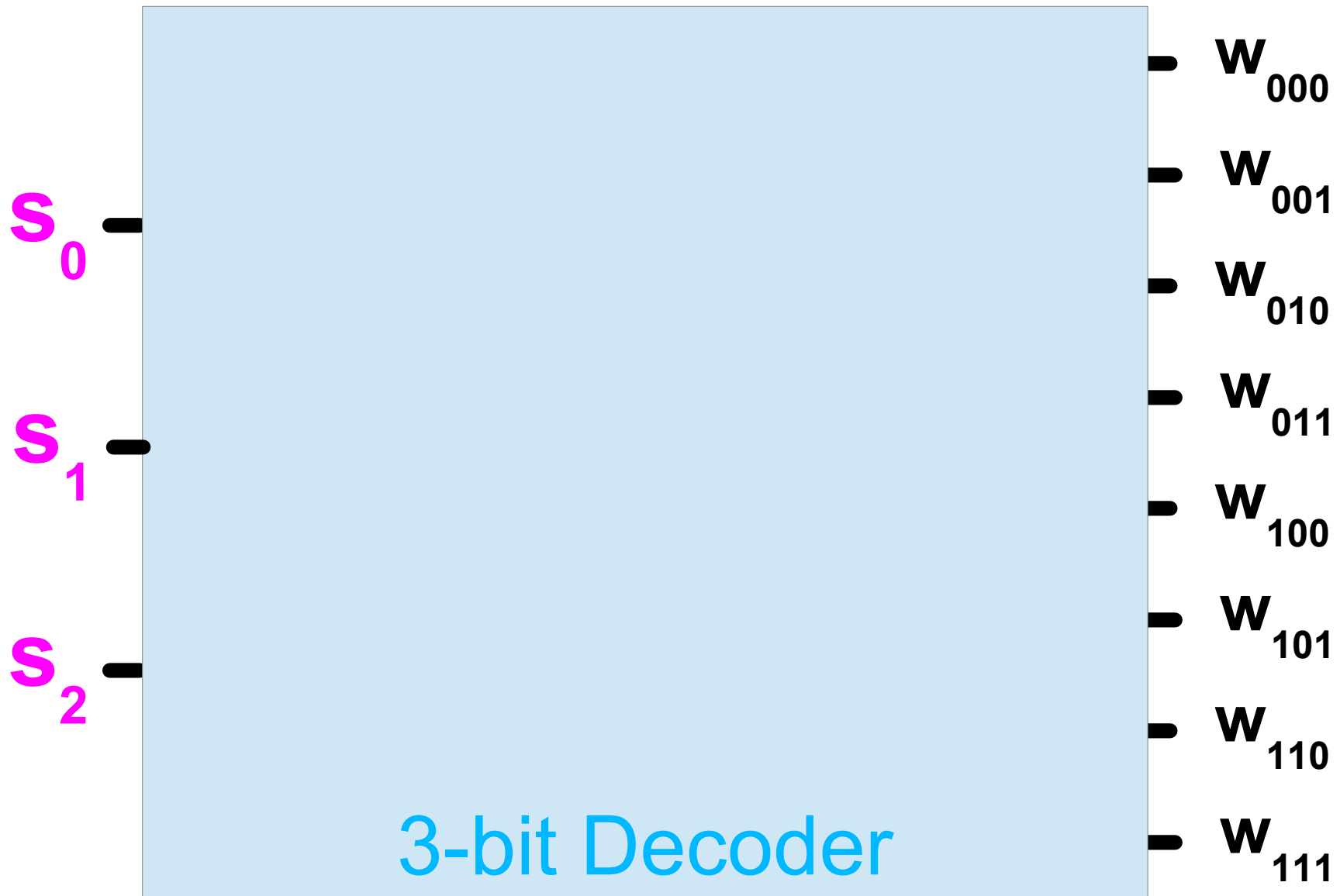

3-bit Decoder Truth Table


s_2	s_1	s_0	w_{000}	w_{010}	w_{010}	w_{011}	w_{100}	w_{111}	w_{110}	w_{111}
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Decoder Summary

Decoder: *select* unique output to be 1 (true)

N **selector** inputs

2^N outputs

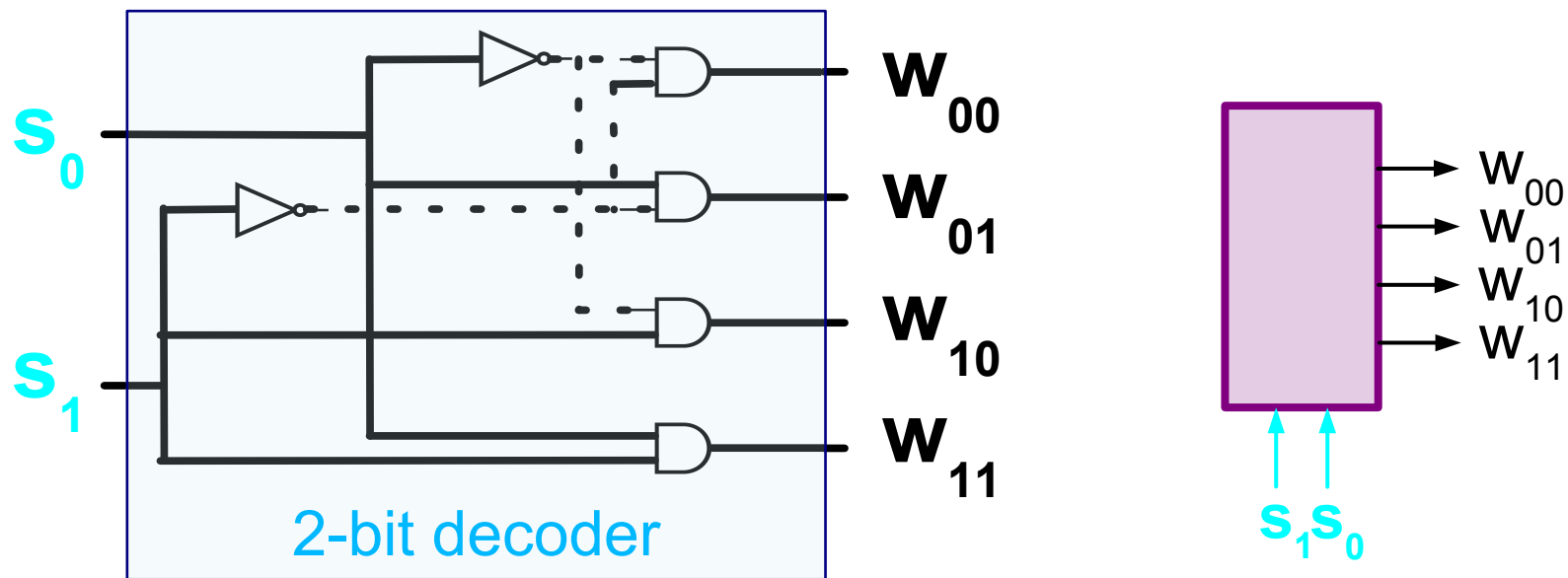

M-way Multiplexer ($M \equiv 2^N$)

N ($\lg M$) *selector* inputs

choose one of 2^N (M) data inputs to output


2^N -way multiplexer truth table:

2^N data input columns (\mathbf{d}_i $0 \leq i < 2^N$)

N selector input columns (\mathbf{s}_j $0 \leq j < N$, $0 \leq \mathbf{s} < 2^N$)

1 output column ($\mathbf{x} = \mathbf{d}_s$)


2-Way Multiplexer

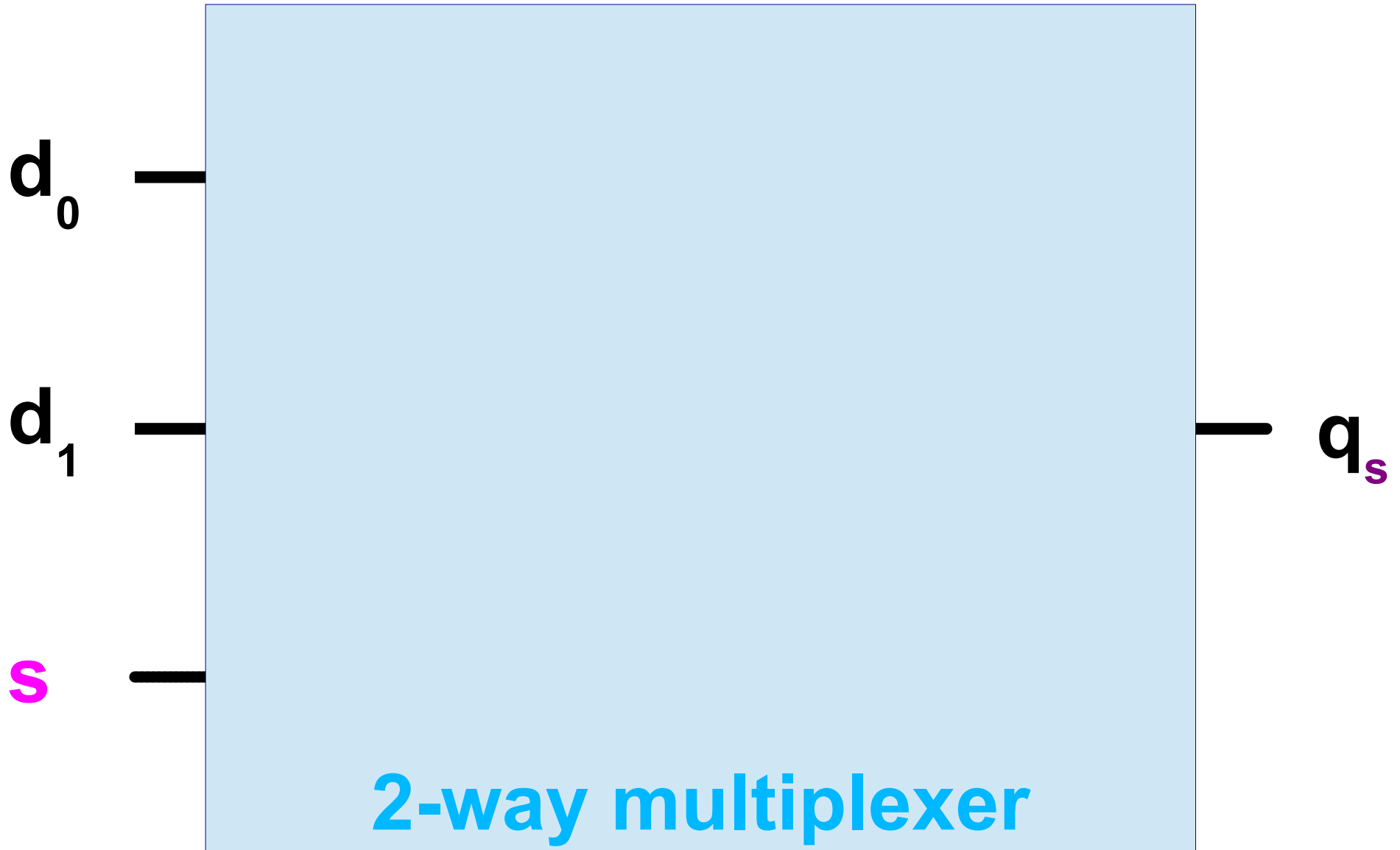


2-Way Multiplexer

#	s	d ₁	d ₀	q
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1


2-Way Multiplexer

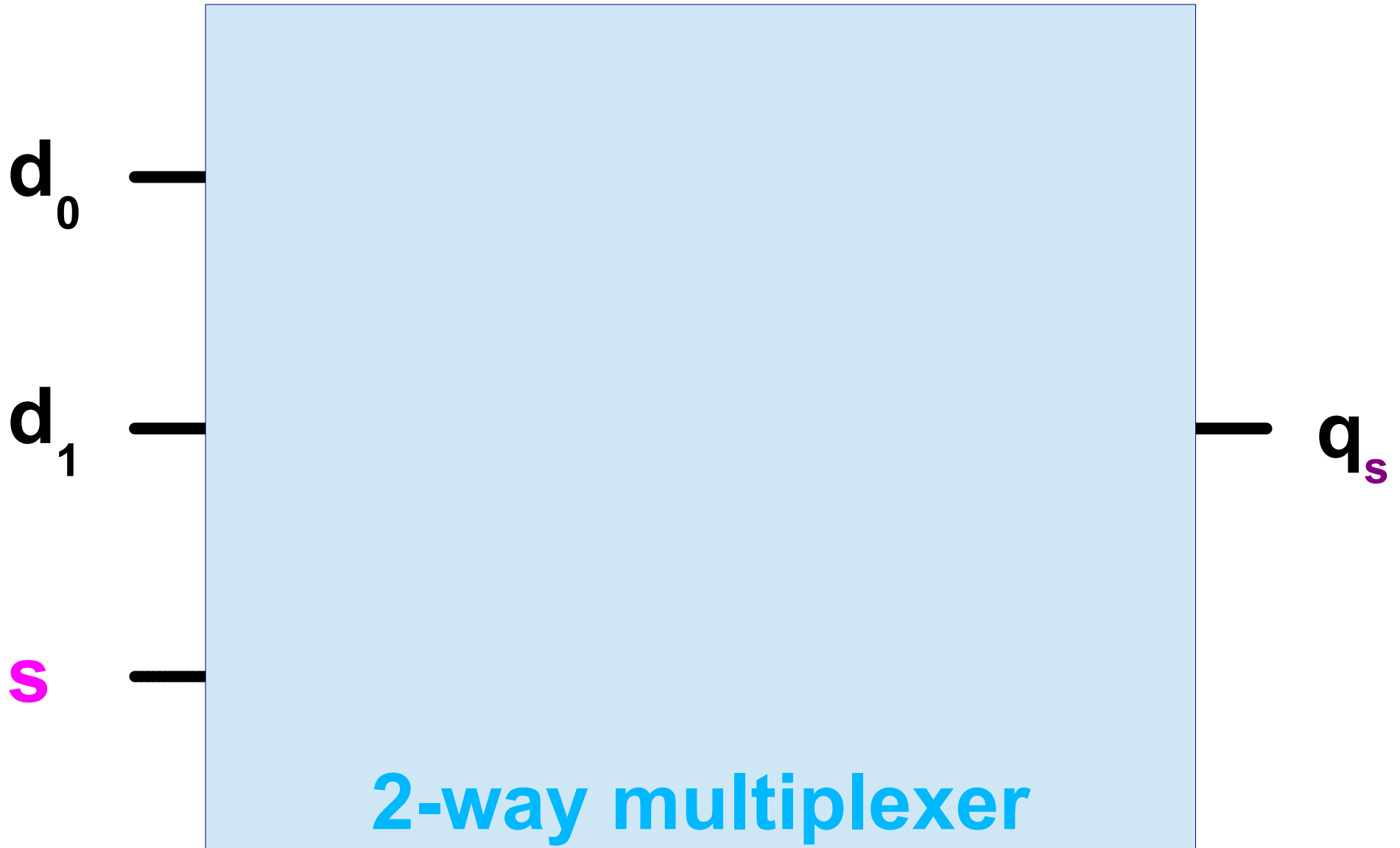


2-Way Multiplexer

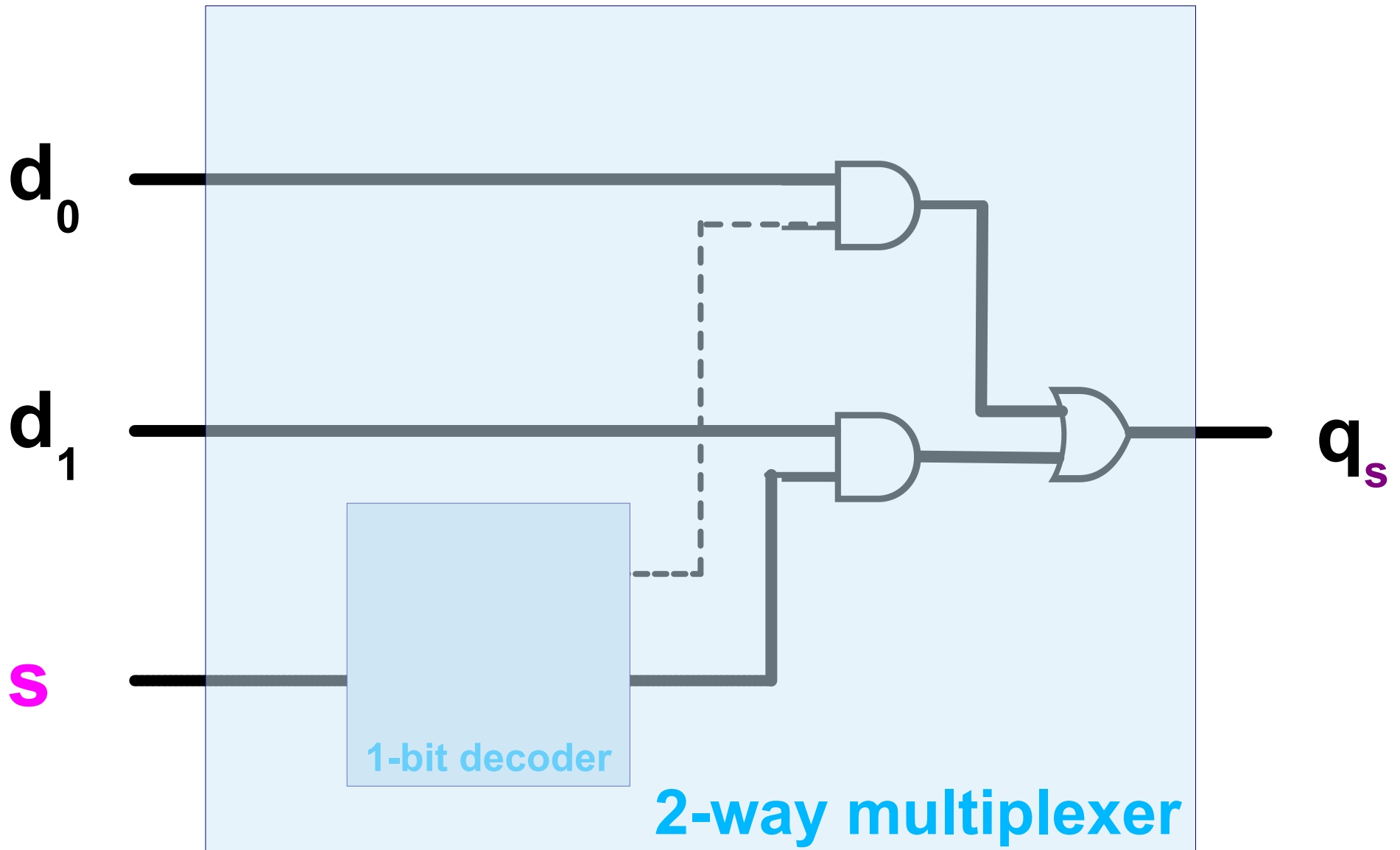


1-Bit Decoder

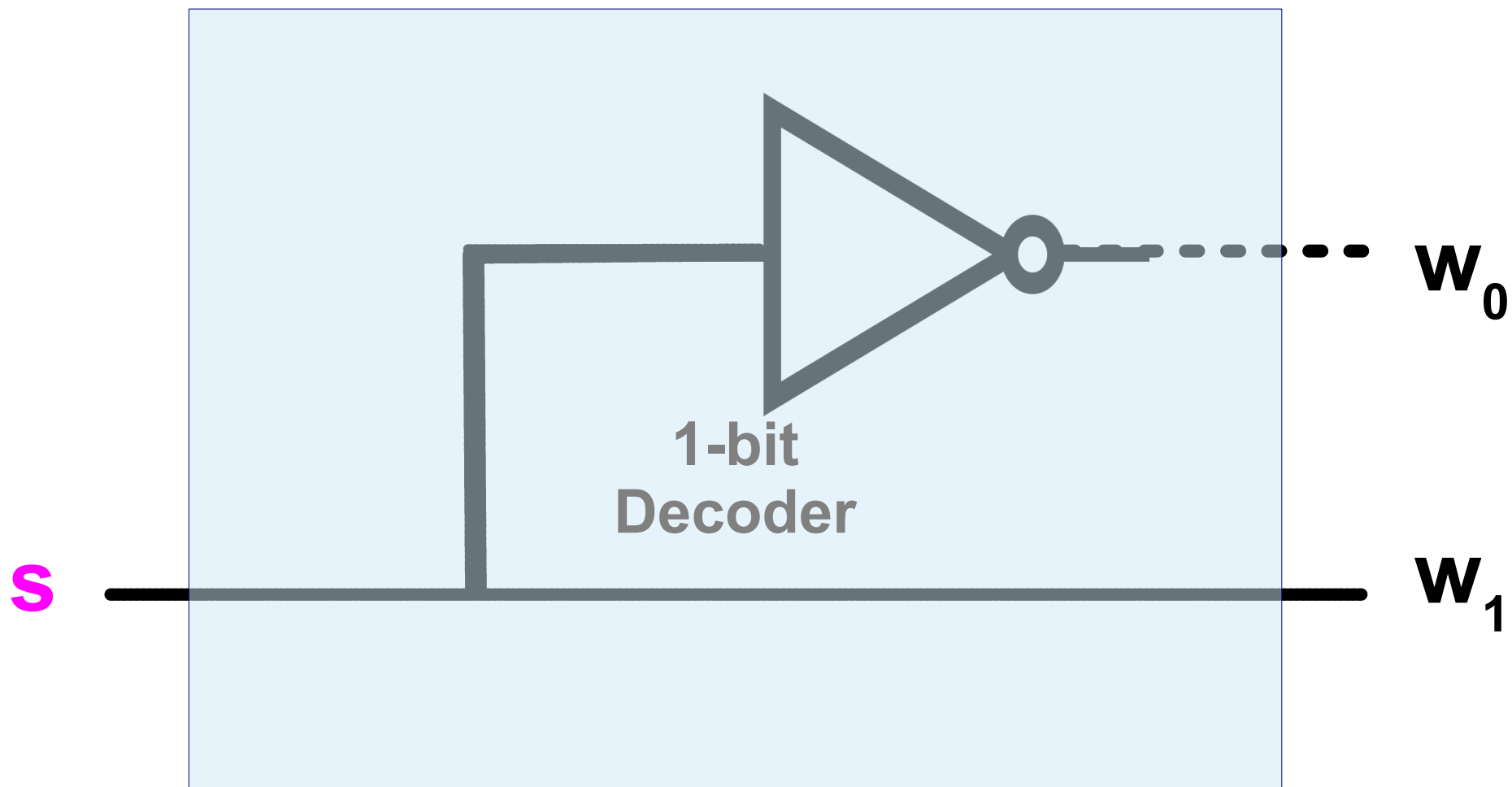


2-Way Multiplexer

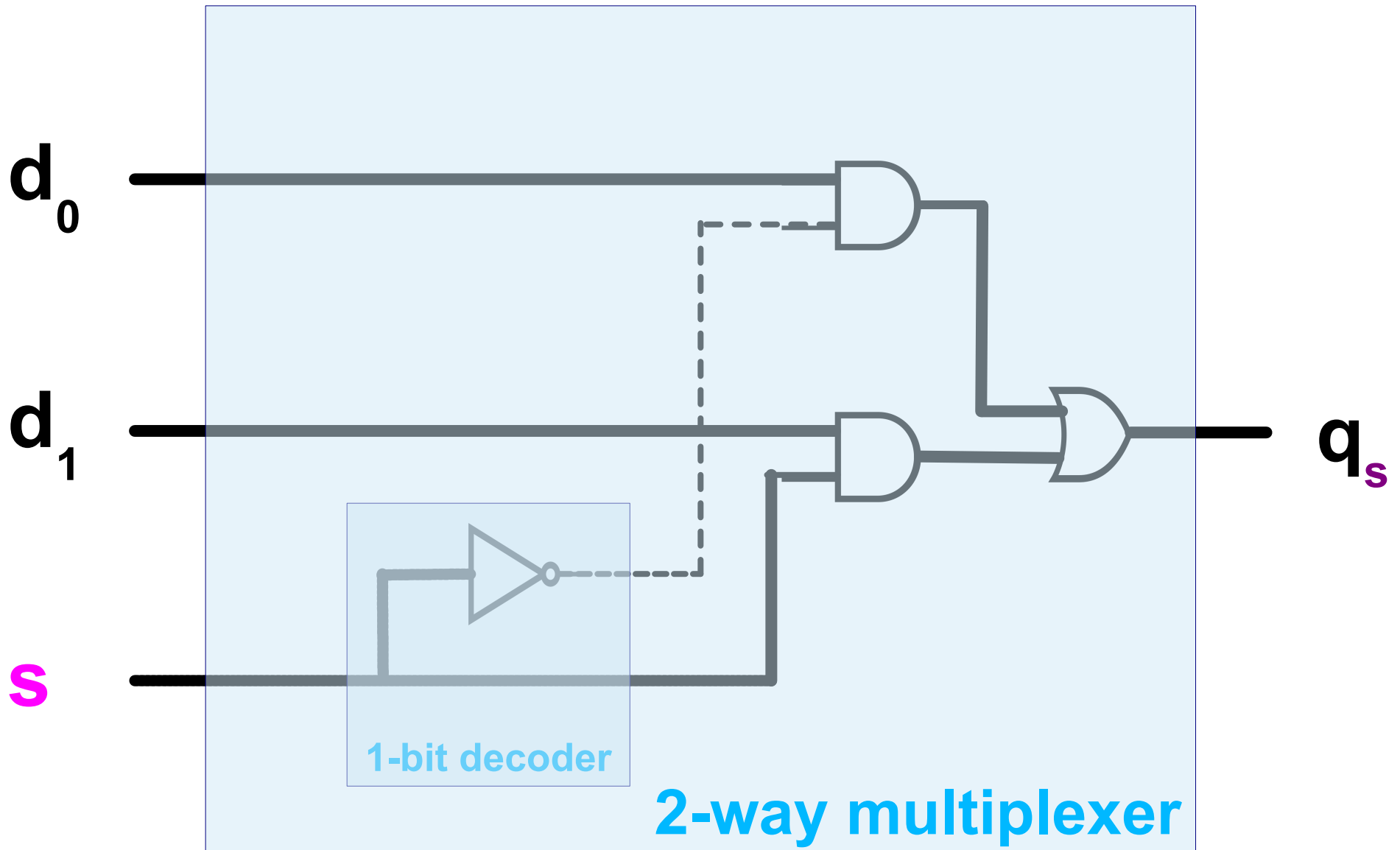


2-Way Multiplexer

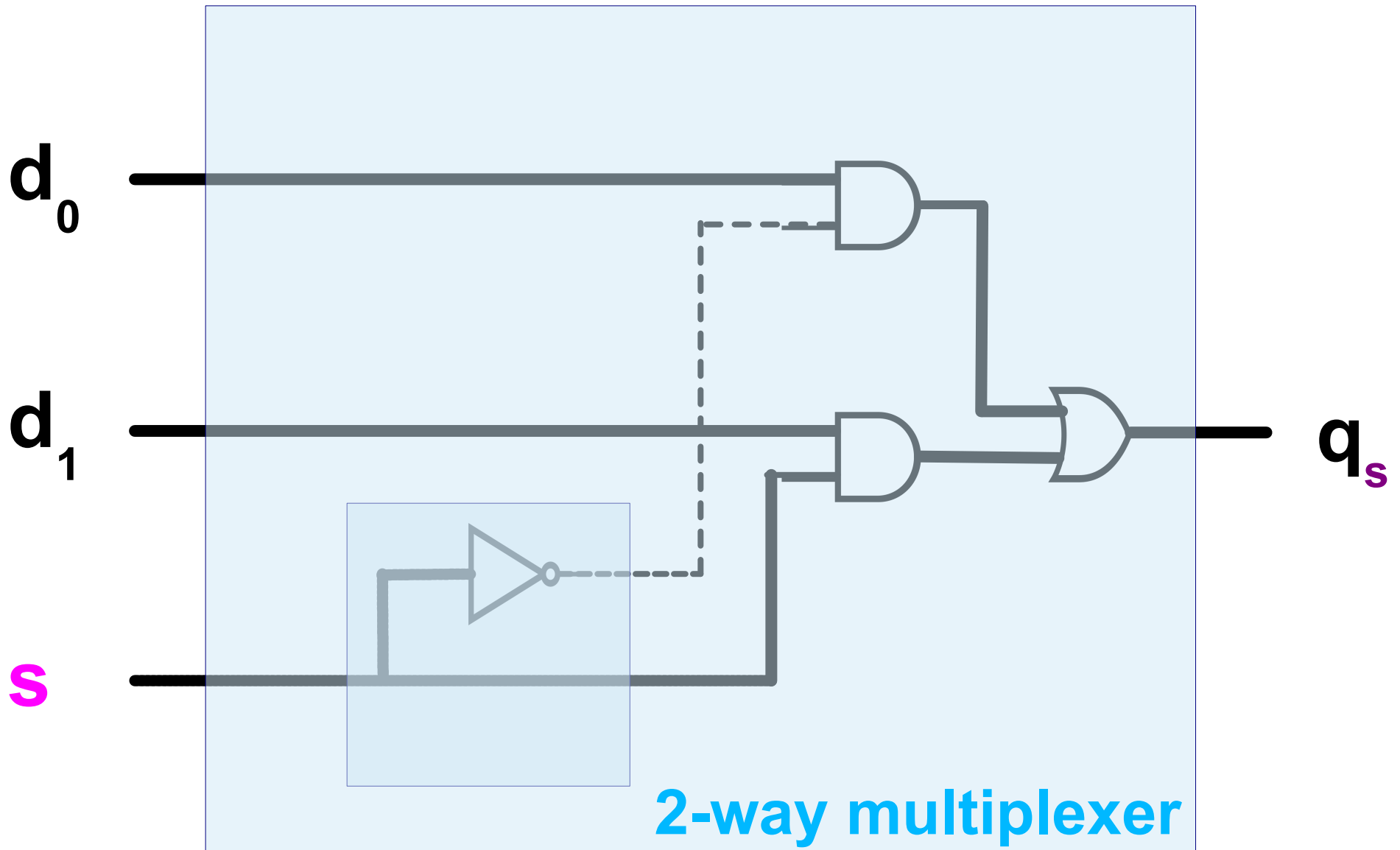

2-Way Multiplexer

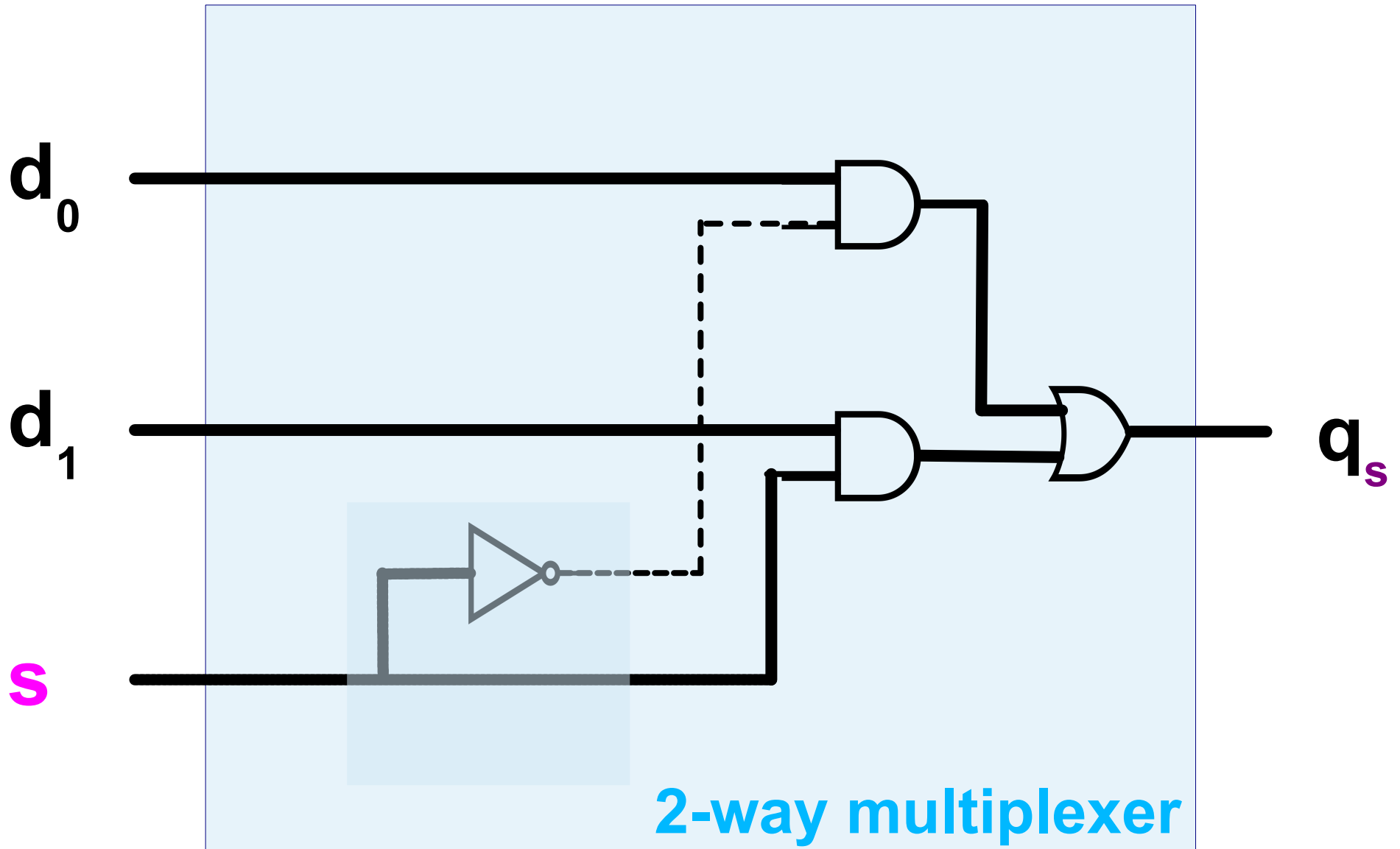

Two Way Multiplexer Circuit

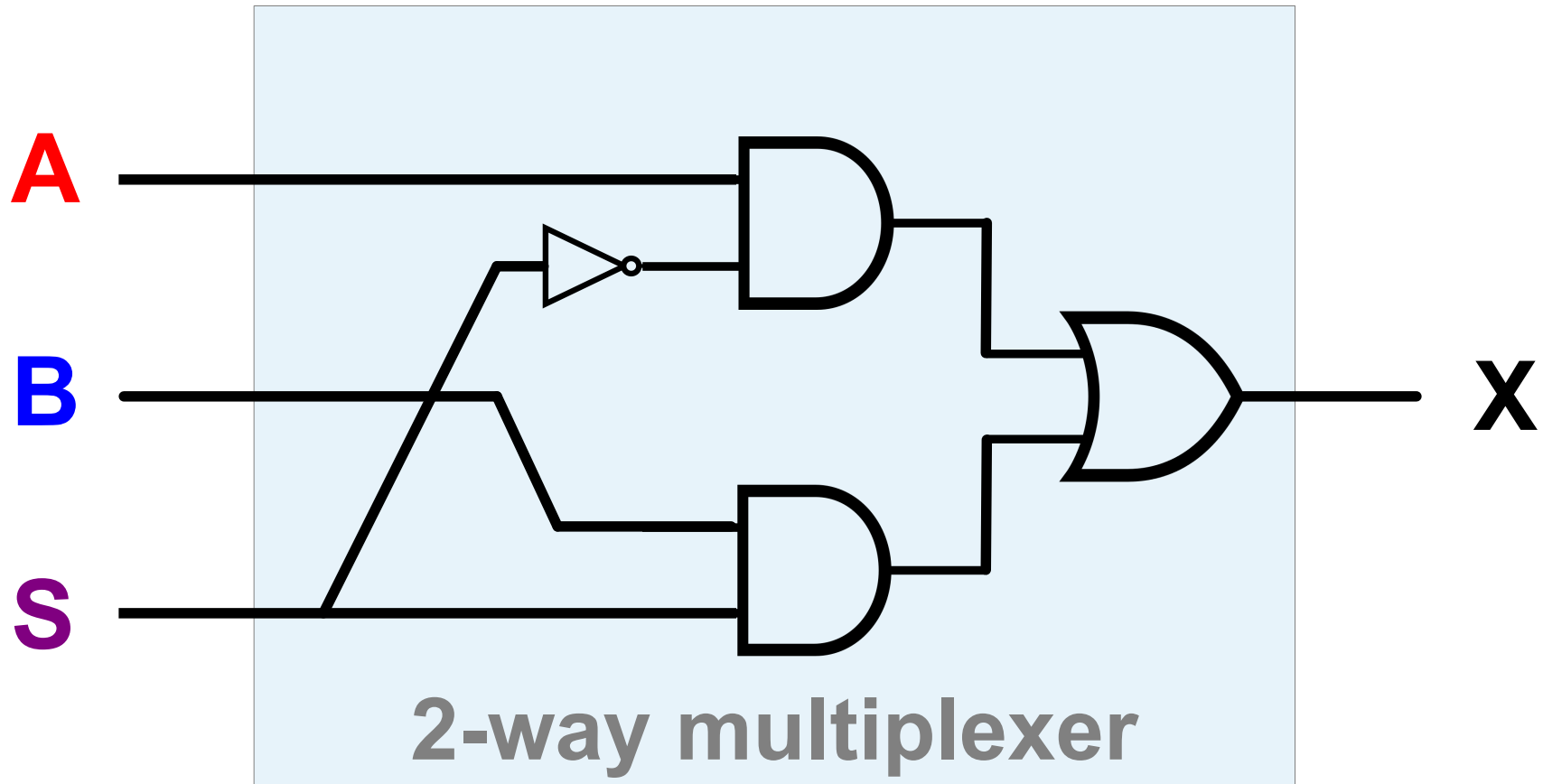

$$X = \bar{S}A + SB$$

4-Way Multiplexer Black Box



4-Way Multiplexer

s_1	s_0	d_{11}	d_{10}	d_{01}	d_{00}	q
0	0	✓	✓	✓	0	0
0	0	✓	✓	✓	1	1
0	1	✓	✓	0	✓	0
0	1	✓	✓	1	✓	1
1	0	✓	0	✓	✓	0
1	0	✓	1	✓	✓	1
1	1	0	✓	✓	✓	0
1	1	1	✓	✓	✓	1

4-Way Multiplexer

s_1	s_0	d_{11}	d_{10}	d_{01}	d_{00}	q
0	0	✓	✓	✓	0	0
0	0	✓	✓	✓	1	1
0	1	✓	✓	0	✓	0
0	1	✓	✓	1	✓	1
1	0	✓	0	✓	✓	0
1	0	✓	1	✓	✓	1
1	1	0	✓	✓	✓	0
1	1	1	✓	✓	✓	1


$$\bar{s}_1 \bar{s}_0 d_{00}$$

$$+ \bar{s}_1 s_0 d_{01}$$

$$+ s_1 \bar{s}_0 d_{10}$$

$$+ s_1 s_0 d_{11}$$


4-Way Multiplexer

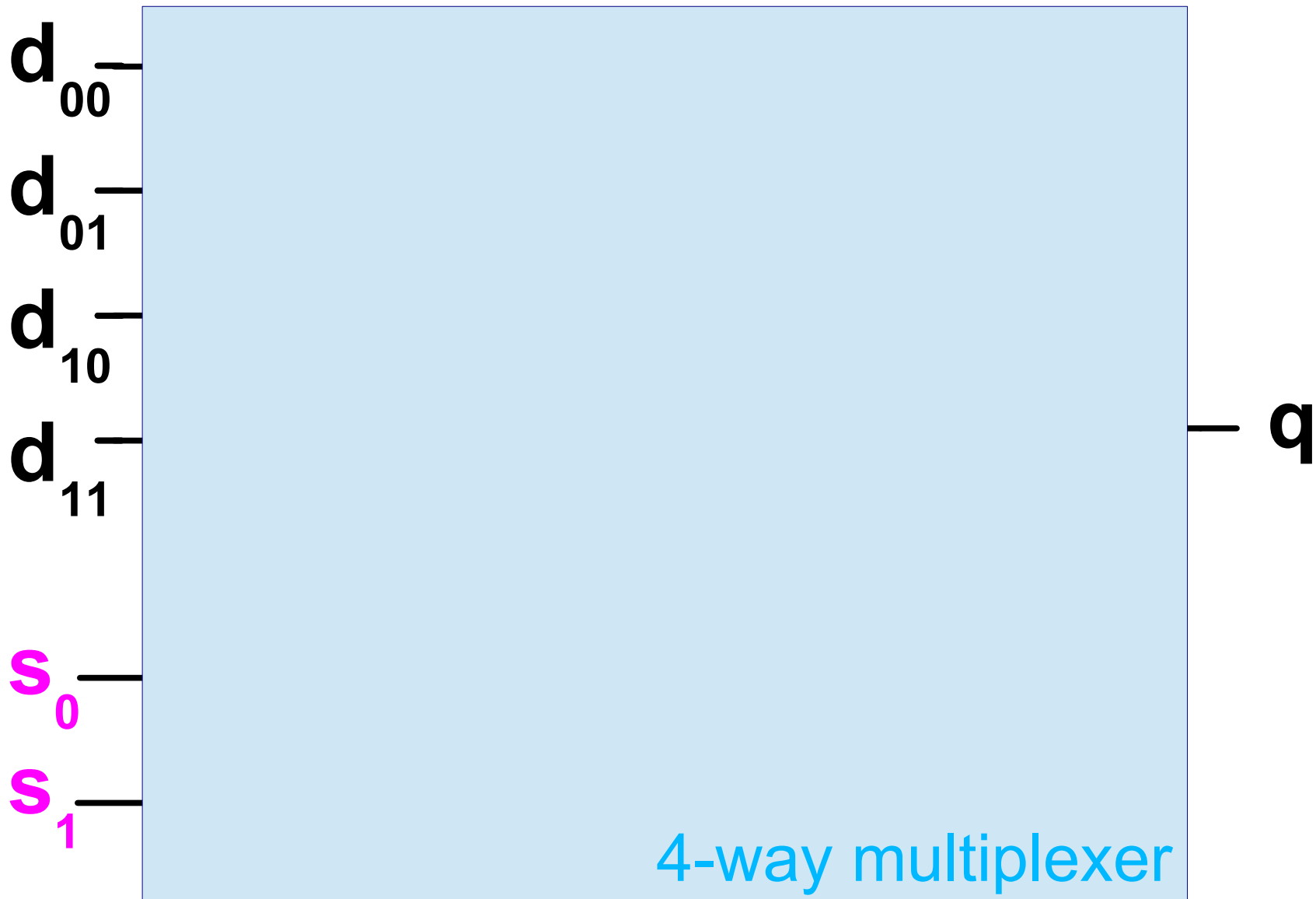


16-Way Multiplexer



16-Way Multiplexer

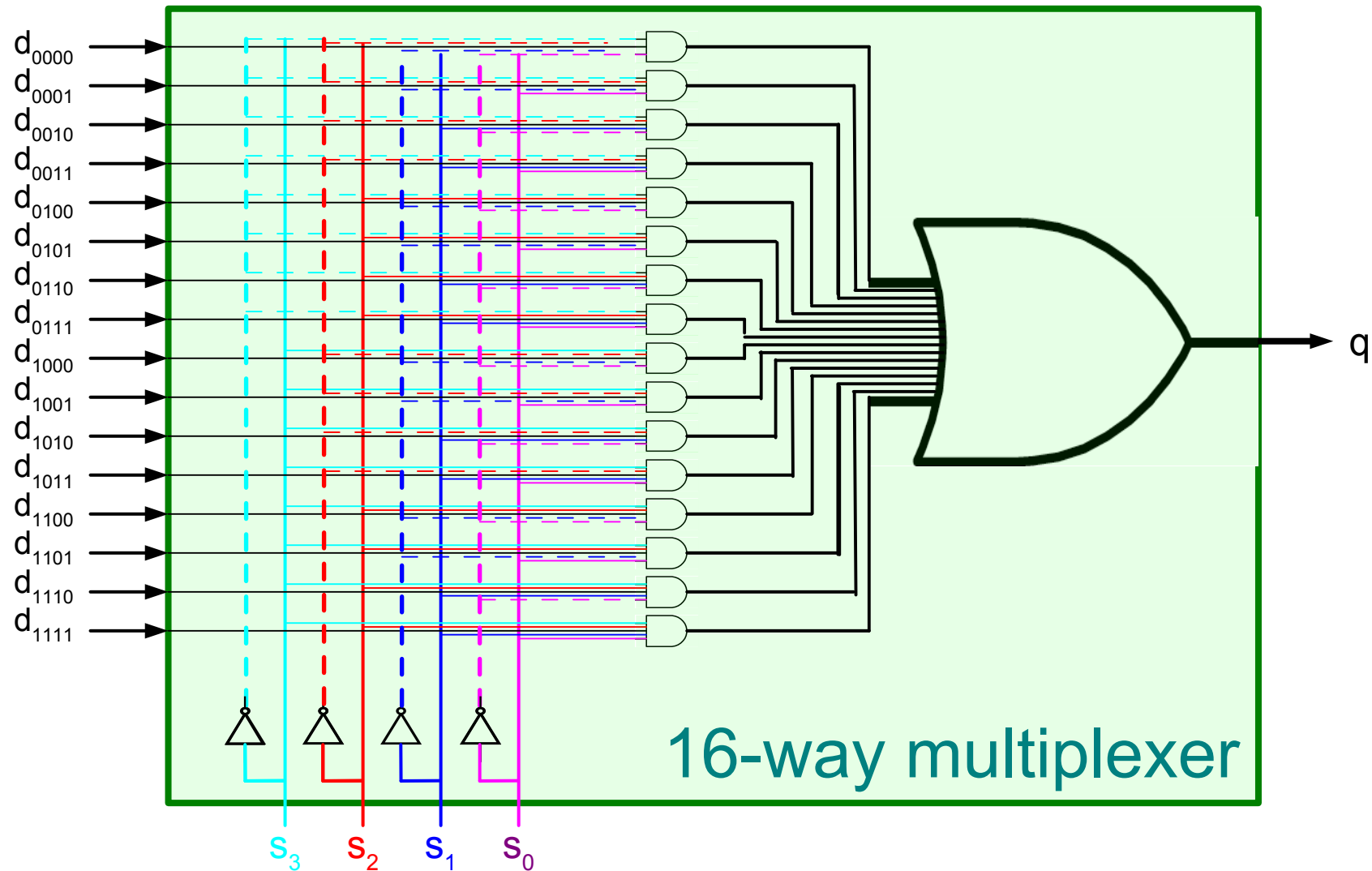

4-Way Multiplexer

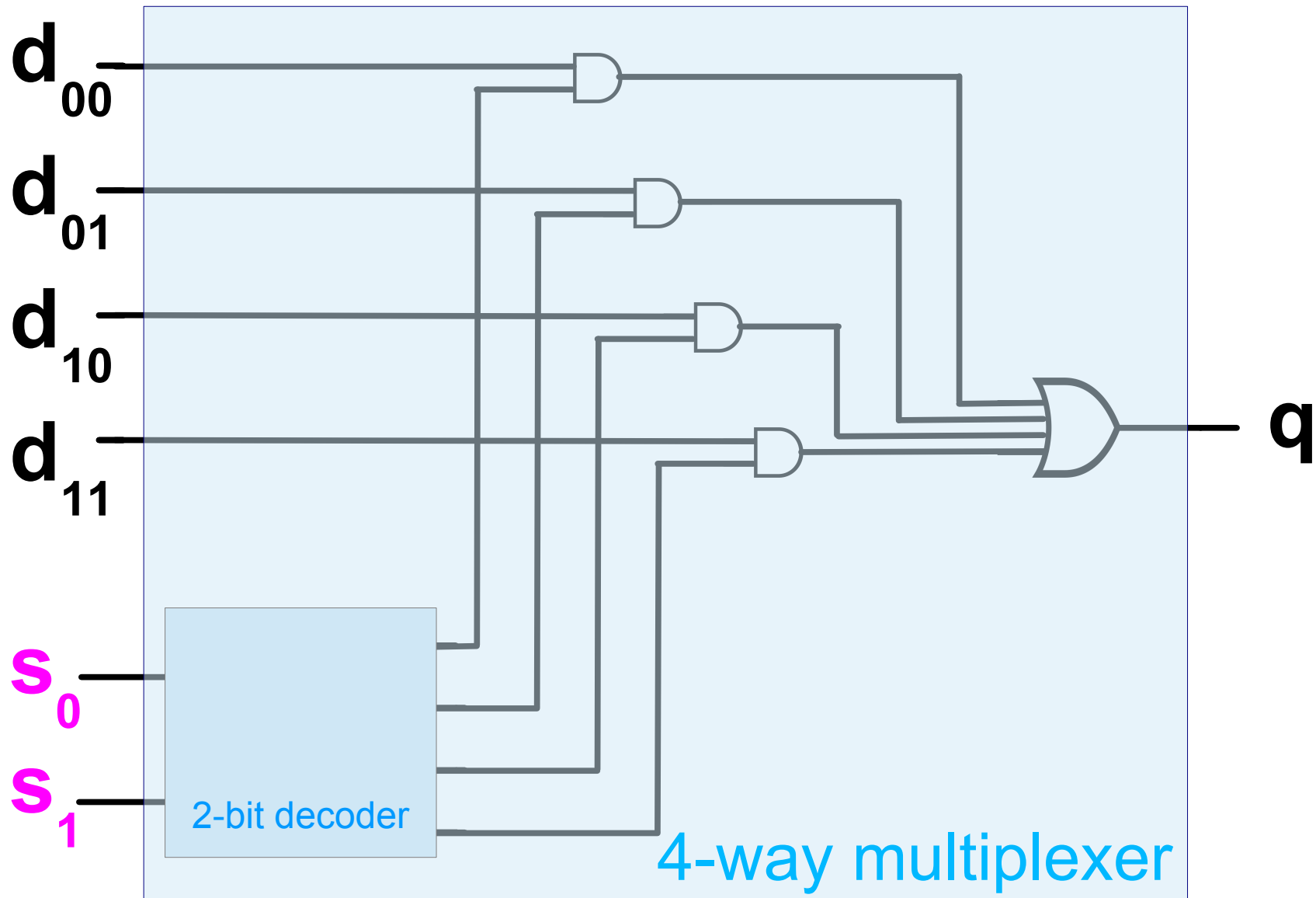

2^N -Way Multiplexer Summary

N **selector** inputs specify one of 2^N data inputs to output

