

# CMP 334 (2/13/19)

Review Quiz 1 (base conversion)

Unsigned binary subtraction (example)

High Level Language program compilation

**TOY** assembly language (introduction)

**TOY** AL program execution

Representing numbers in circuits

$N < 4$  circuit

Circuit  $\rightarrow$  formula  $\rightarrow$  truth table  $\rightarrow$  circuit

Combinational circuit design process

# Quiz 1 Review

1. Convert **0x8D39** to binary.

1000 1101 0011 1001

2. Convert **0x14A** to decimal.

0x14A represents

$$\begin{aligned} 1 \cdot 16^2 + 4 \cdot 16^1 + 10 \cdot 16^0 &= 256 + 4 \cdot 16 + 10 \\ &= 256 + 64 + 10 \\ &= 330 \end{aligned}$$

# Quiz 1 Review (continued)

2. Convert **187**<sub>10</sub> to binary.

$$187 \cdot 2^0 = 93 \cdot 2^1 + 1 \cdot 2^0$$

$$93 \cdot 2^1 = 46 \cdot 2^2 + 1 \cdot 2^1$$

$$46 \cdot 2^2 = 23 \cdot 2^3 + 0 \cdot 2^2$$

$$23 \cdot 2^3 = 11 \cdot 2^4 + 1 \cdot 2^3$$

$$11 \cdot 2^4 = 5 \cdot 2^5 + 1 \cdot 2^4$$

$$5 \cdot 2^5 = 2 \cdot 2^6 + 1 \cdot 2^5$$

$$2 \cdot 2^6 = 1 \cdot 2^7 + 0 \cdot 2^6$$

$$1 \cdot 2^7 = \textcolor{red}{0} \cdot 2^8 + 1 \cdot 2^7$$

$$187_{10} = 1 \cdot 2^7 + 0 \cdot 2^6 + 1 \cdot 2^5 + 1 \cdot 2^4 + 1 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0$$

$$= 10111011_2$$

**Immediate values**

s8 — 8-bit signed immediate  
 u4 — 4-bit unsigned immediate  
 CC — 4-bit condition code

**Register File** 16 16-bit “registers”

15 real registers: \$1 ... \$F  
 1 pseudo-register: \$0 [\$0] = 0

**Main Memory** 65536 16-bit words

$M[n]$  —  $n^{\text{th}}$  memory address  
 $\wedge M[n]$  — content of  $M[n]$

**Instructions<sup>0</sup>**

**add**  $\$T \leftarrow [\$A] + [\$B]^1$   
**and**  $\$T \leftarrow [\$A] \& [\$B]^1$   
**bc**  $PC \leftarrow [PC] + S8 \ll CC$   
**bcl**  $\$L \leftarrow [PC], PC \leftarrow [\$A]^1 \ll CC$   
**l**  $\$T \leftarrow \wedge M[[\$A] + [\$B]]^1$   
**lwr**  $\$T \leftarrow \wedge M[[\$A] + [\$B]]^1 \text{ set rsvn}$   
**lih**  $\$T_{15..8} \leftarrow I8^1$   
**lis**  $\$T \leftarrow I8^1$  (sign extended)  
**nor**  $\$T \leftarrow \overline{[\$A] \mid [\$B]}^1$   
**sl**  $\$T \leftarrow [\$A] \ll U4^1$   
**srs**  $\$T \leftarrow [\$A] \gg U4^1$   
**sru**  $\$T \leftarrow [\$A] \ggg U4^1$   
**st**  $M[[\$A] + [\$B]] \leftarrow [\$S]$   
**stc**  $M[[\$A] + [\$B]] \leftarrow [\$S]^4 \ll \text{rsvn}$   
**sub**  $\$T \leftarrow [\$A] - [\$B]^{1,2}$   
**sys** system call

## Arithmetic / Logical

1111	<b>add</b>	\$T	\$A	\$B
1110	<b>sub</b>	\$T	\$A	\$B
1101	<b>and</b>	\$T	\$A	\$B
1100	<b>nor</b>	\$T	\$A	\$B

## Load /Store

1011	<b>l</b>	\$T	\$A	\$B
1010	<b>lwr</b>	\$T	\$A	\$B
1001	<b>st</b>	\$S	\$A	\$B
1000	<b>stc</b>	\$S	\$A	\$B

## Shift / Branch &amp; Link

0111	<b>sru</b>	\$T	\$A	U4
0110	<b>srs</b>	\$T	\$A	U4
0101	<b>bcl</b>	CC	\$A	\$L
0100	<b>sl</b>	\$T	\$A	U4

## Immediate

0011	<b>lih</b>	\$T	S8
0010	<b>lis</b>	\$T	S8
0001	<b>bc</b>	CC	S8
0000	<b>sys</b>	\$X	S8

## Condition Codes

1111	$\overline{znv} + nv$	SGT
1110	v	OVF
1101	$n\overline{v} + \overline{nv}$	SLT
1100	n	NEG
1011	$\overline{zc}$	UGT
1010	$\overline{z}$	NE
1001	$\overline{c}$	ULT
1000	0	NOP
0111	$z + n\overline{v} + \overline{nv}$	SLE
0110	$\overline{v}$	NVF
0101	$nv + \overline{nv}$	SGE
0100	$\overline{n}$	POS
0011	$z + \overline{c}$	ULE
0010	z	EQ
0001	c	UGE
0000	1	ALL

**Notes**

<sup>0</sup>  $PC \leftarrow PC+1$  *before* instruction execution


<sup>1</sup> \$0 *not* changed

<sup>2</sup> Determines flags: **z**, **n**, **c**, **v**


<sup>4</sup> Determines flag: **v**

# Assignment Compilation

$$Z = X + Y$$

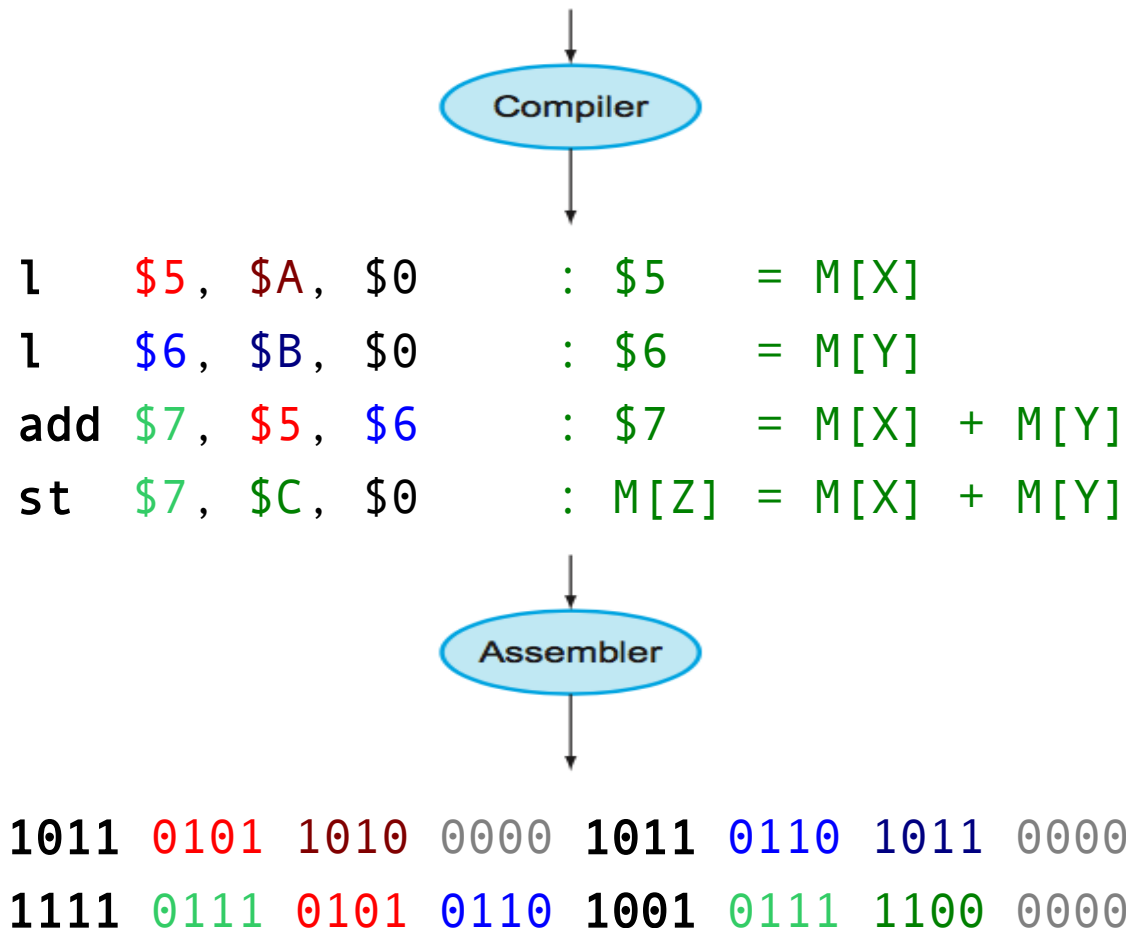


# TOY Processor & RAM

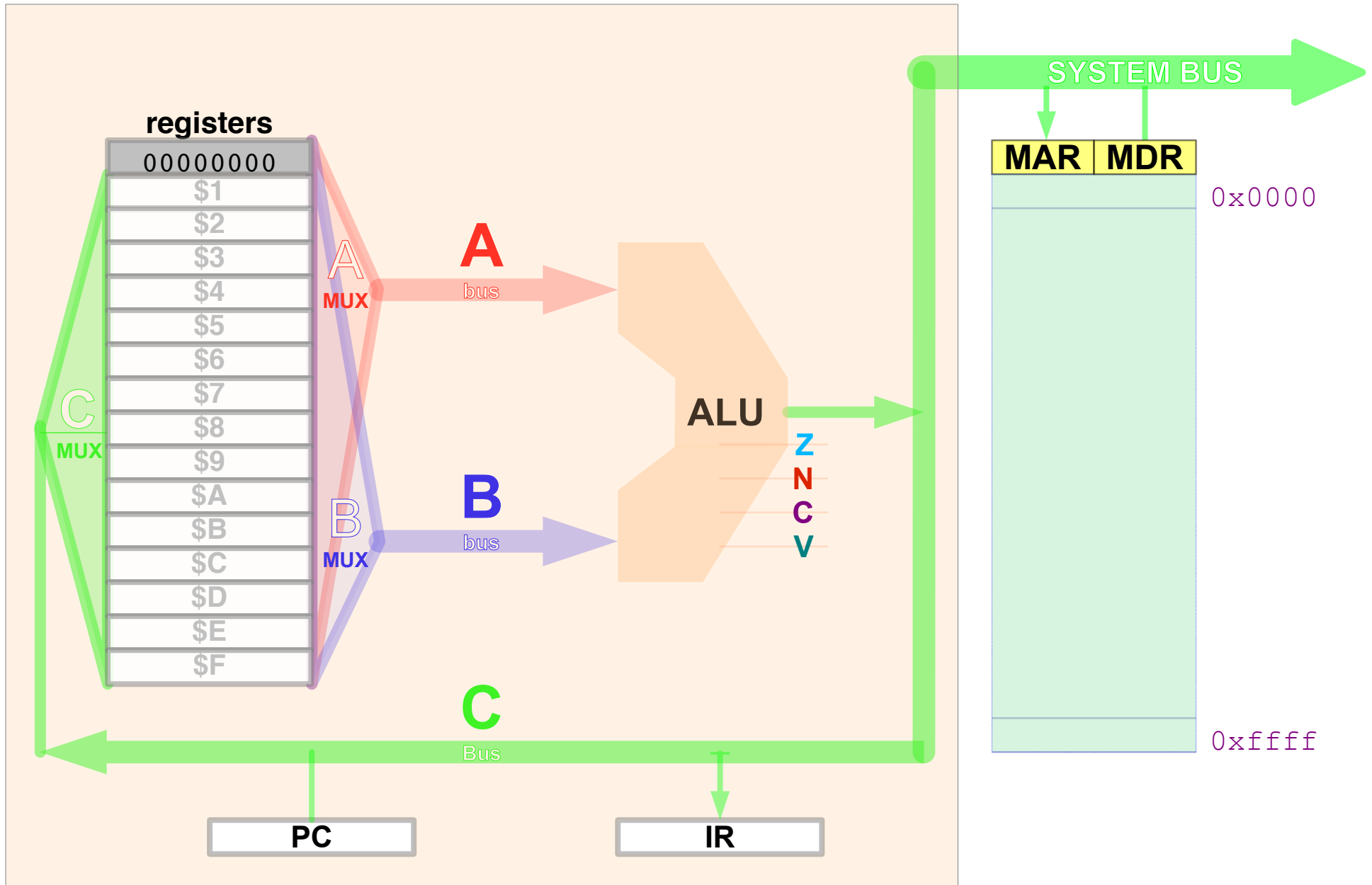

# The T<sup>o</sup>Y Computer


fetch

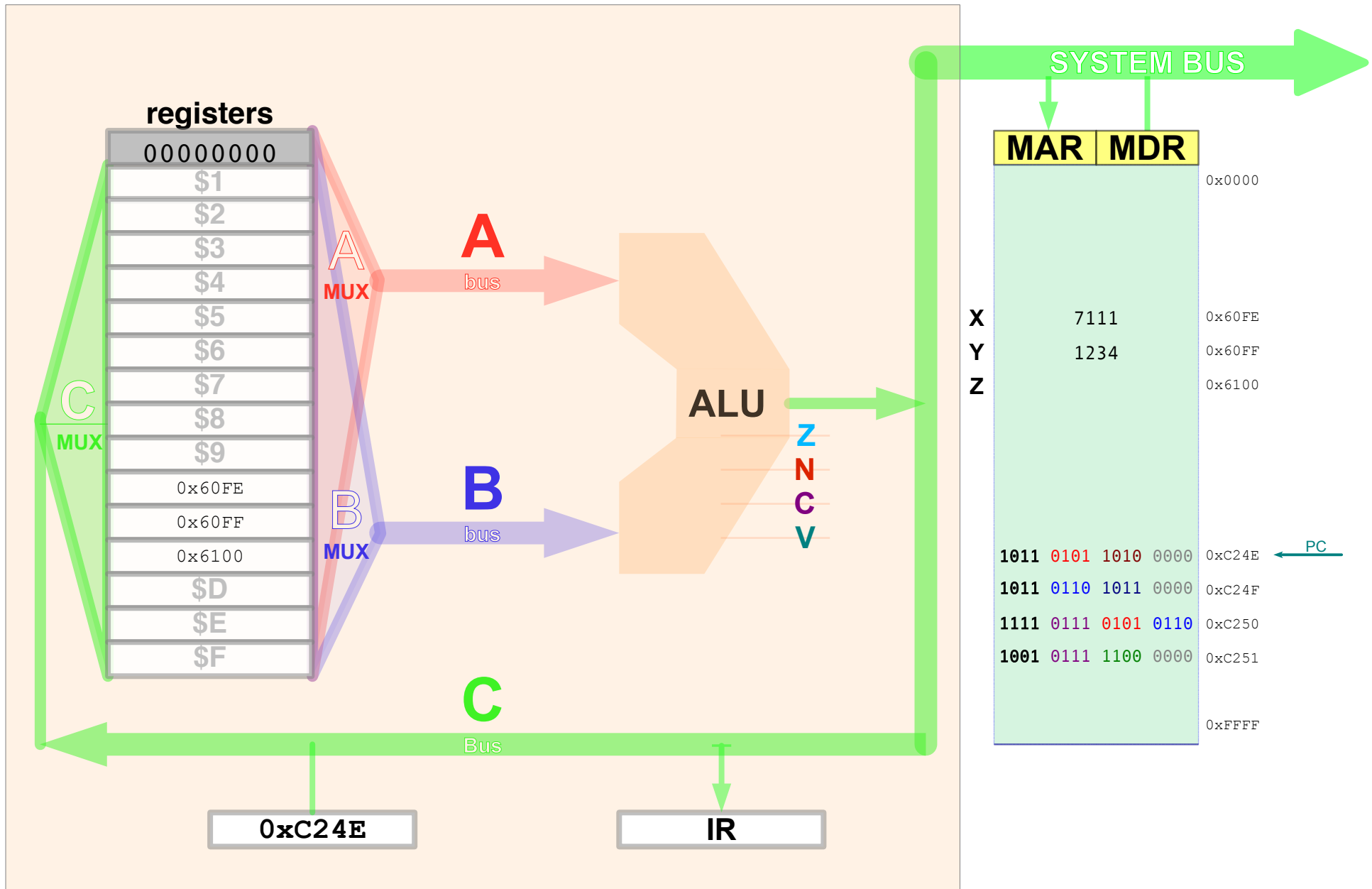

fetch

# The T<sup>©</sup>Y Computer

execute

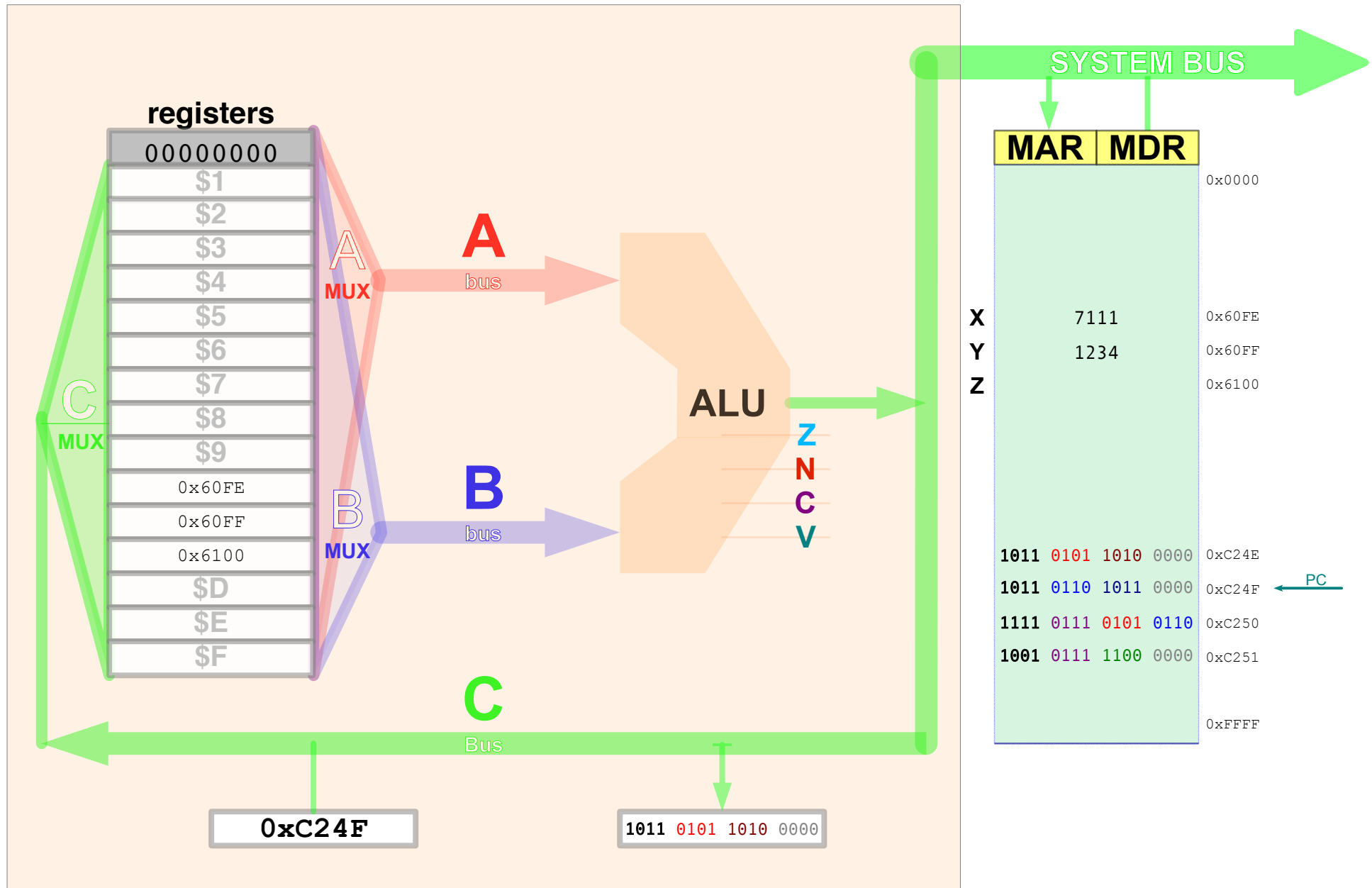




execute

# The T<sup>©</sup>Y Computer


fetch

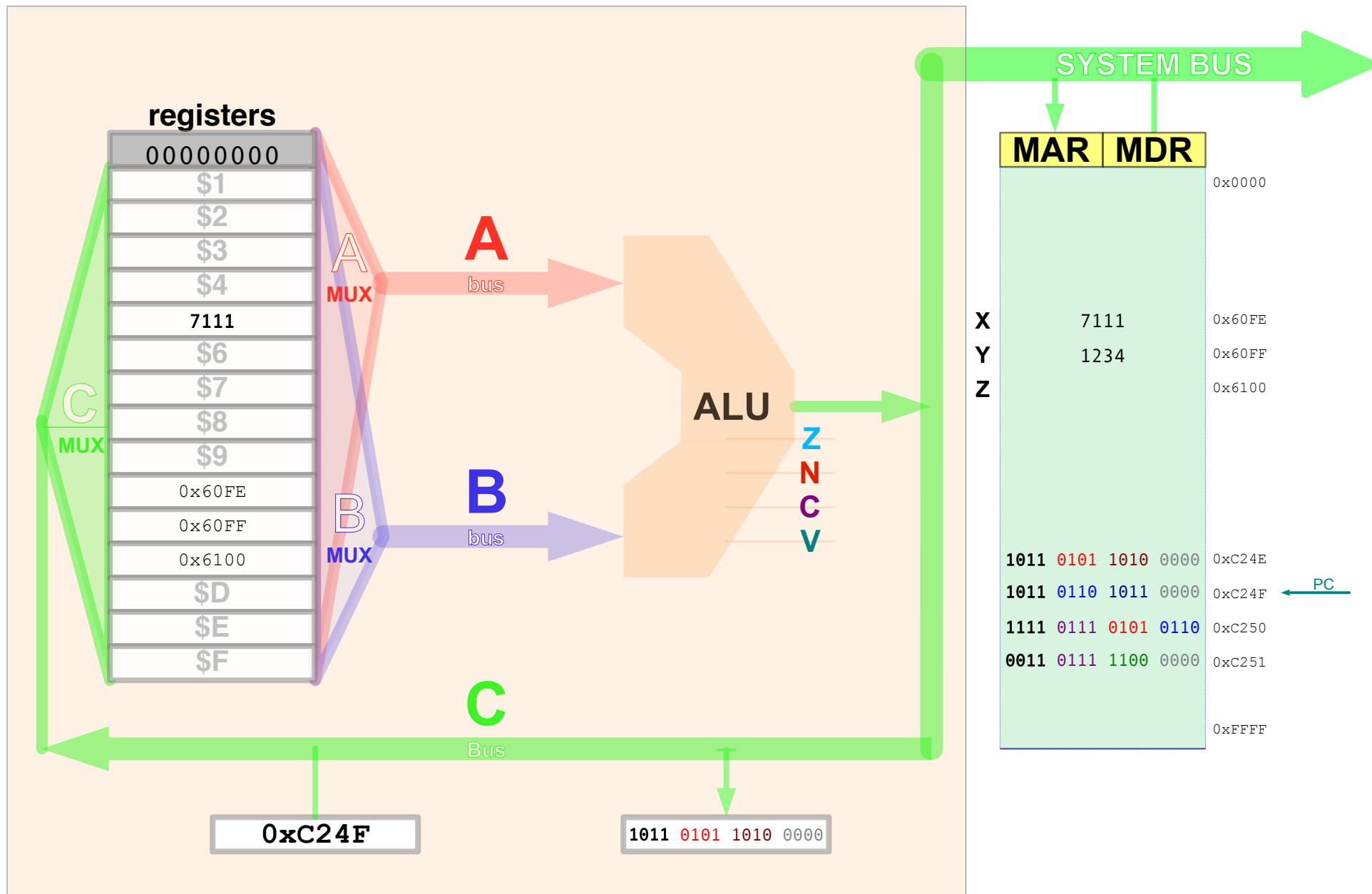

fetch

# The T<sup>©</sup>Y Computer


execute

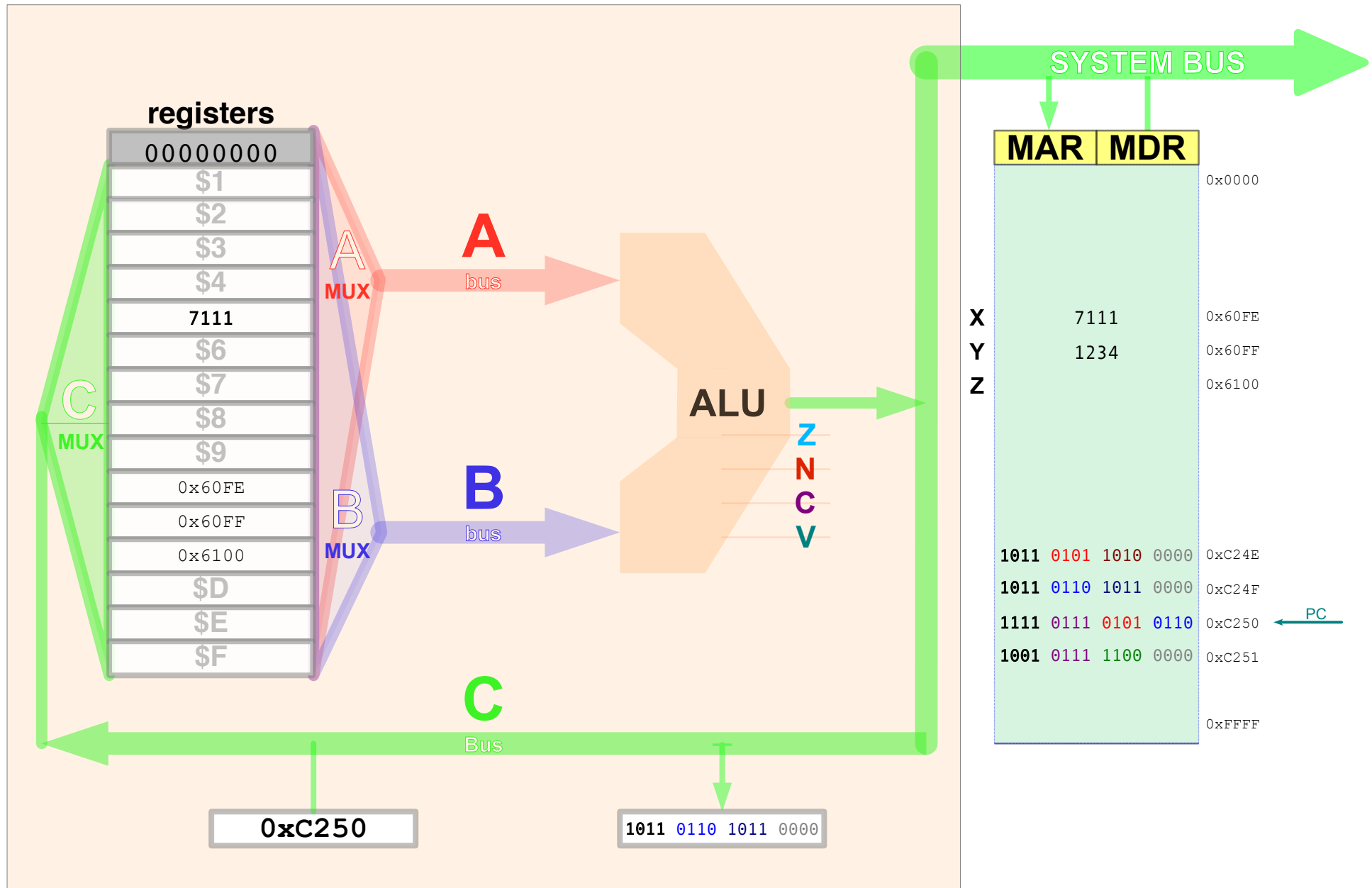

execute

# The T<sub>0</sub>Y Computer


fetch

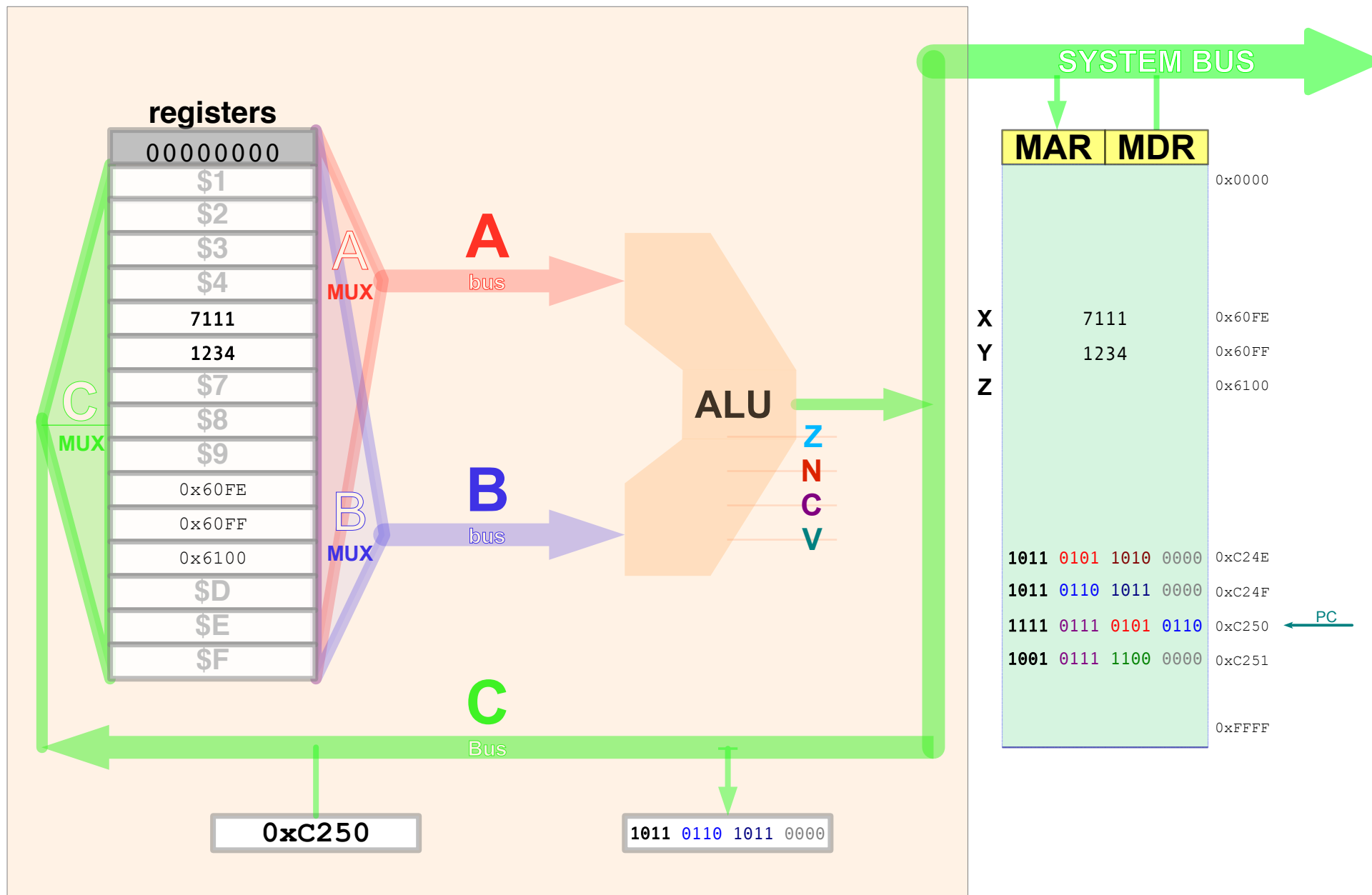

fetch

# The T<sub>0</sub>Y Computer


execute

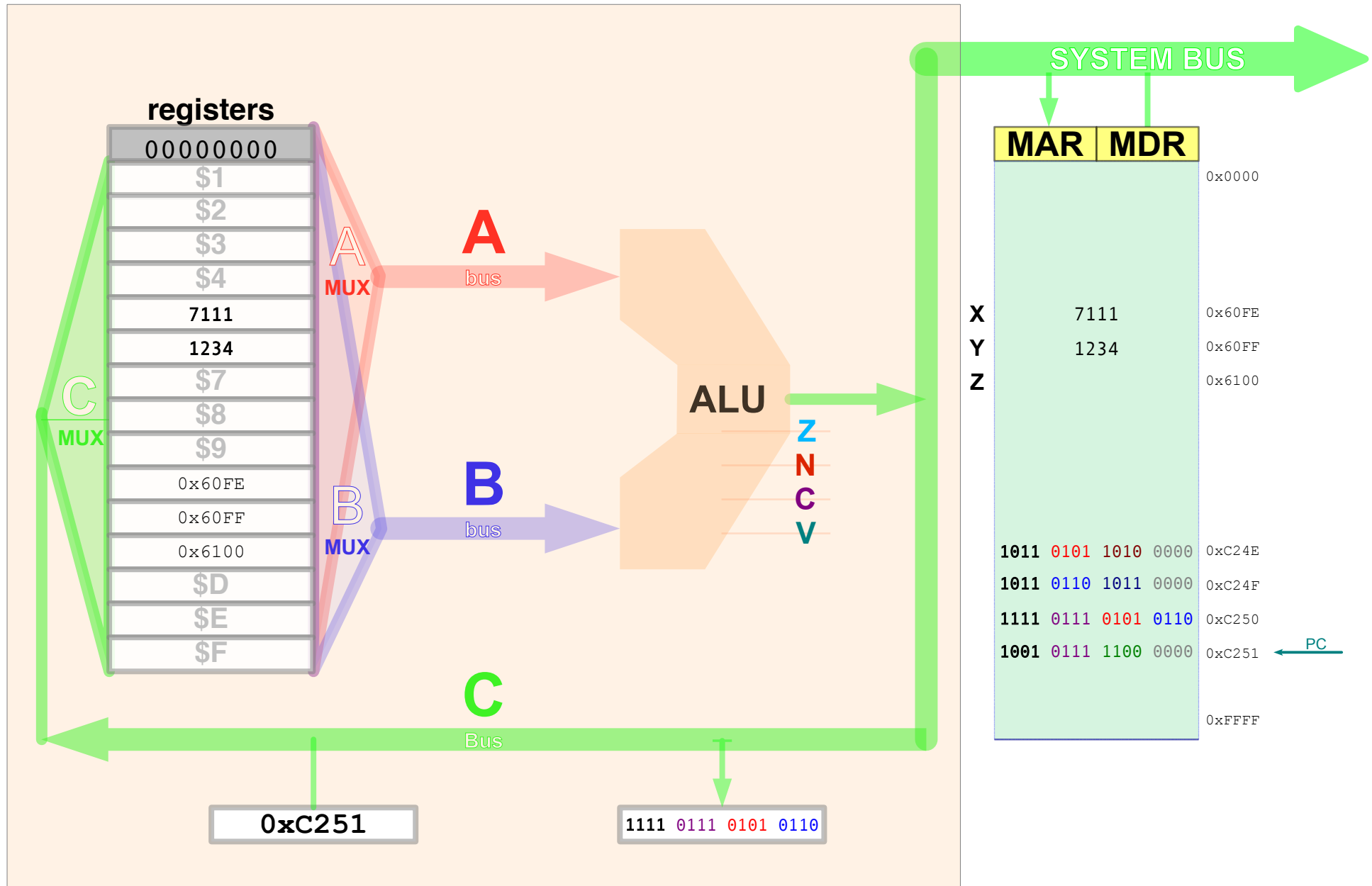

execute

# The T<sub>0</sub>Y Computer


fetch

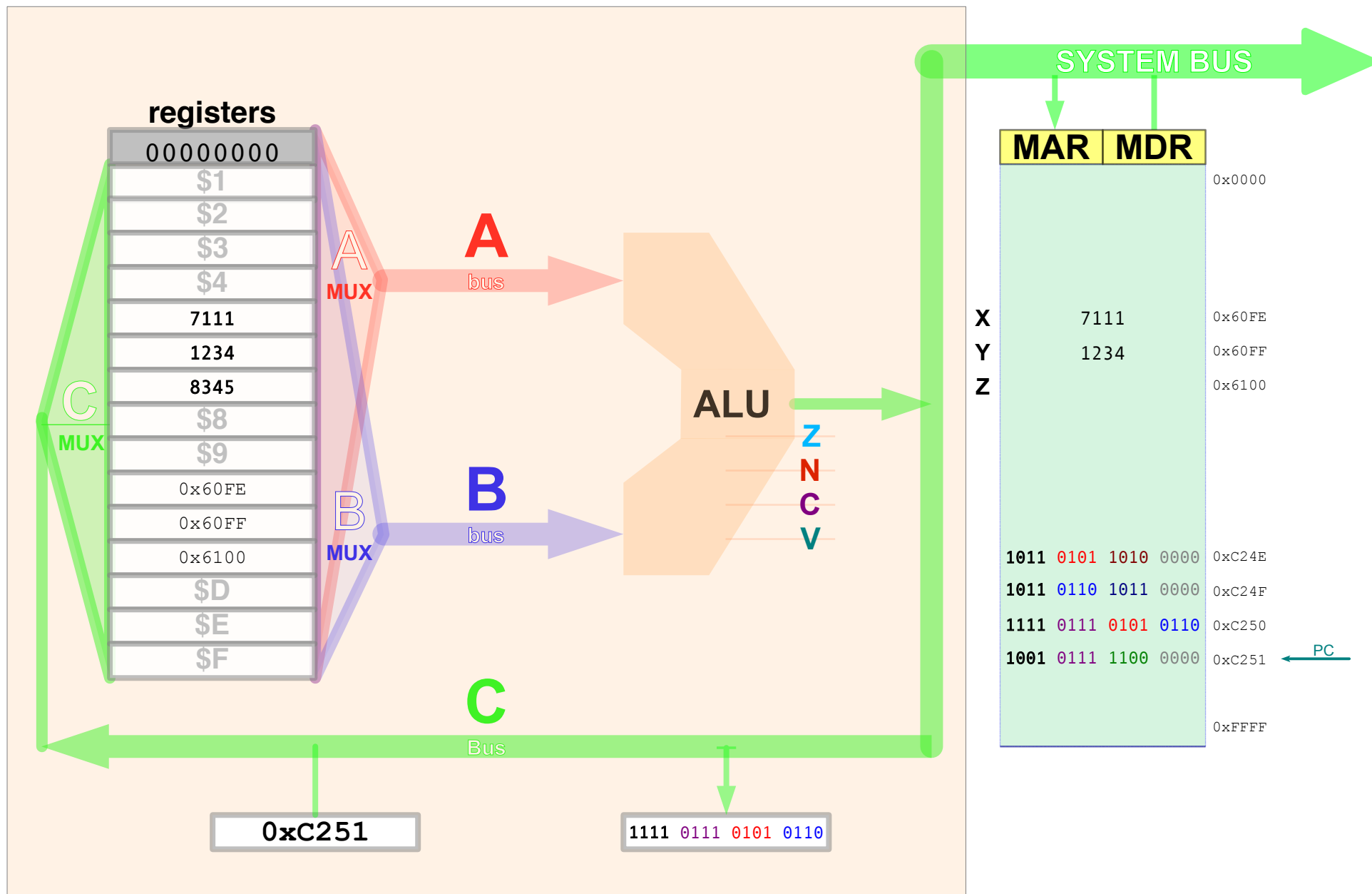

fetch

# The T<sub>0</sub>Y Computer

execute

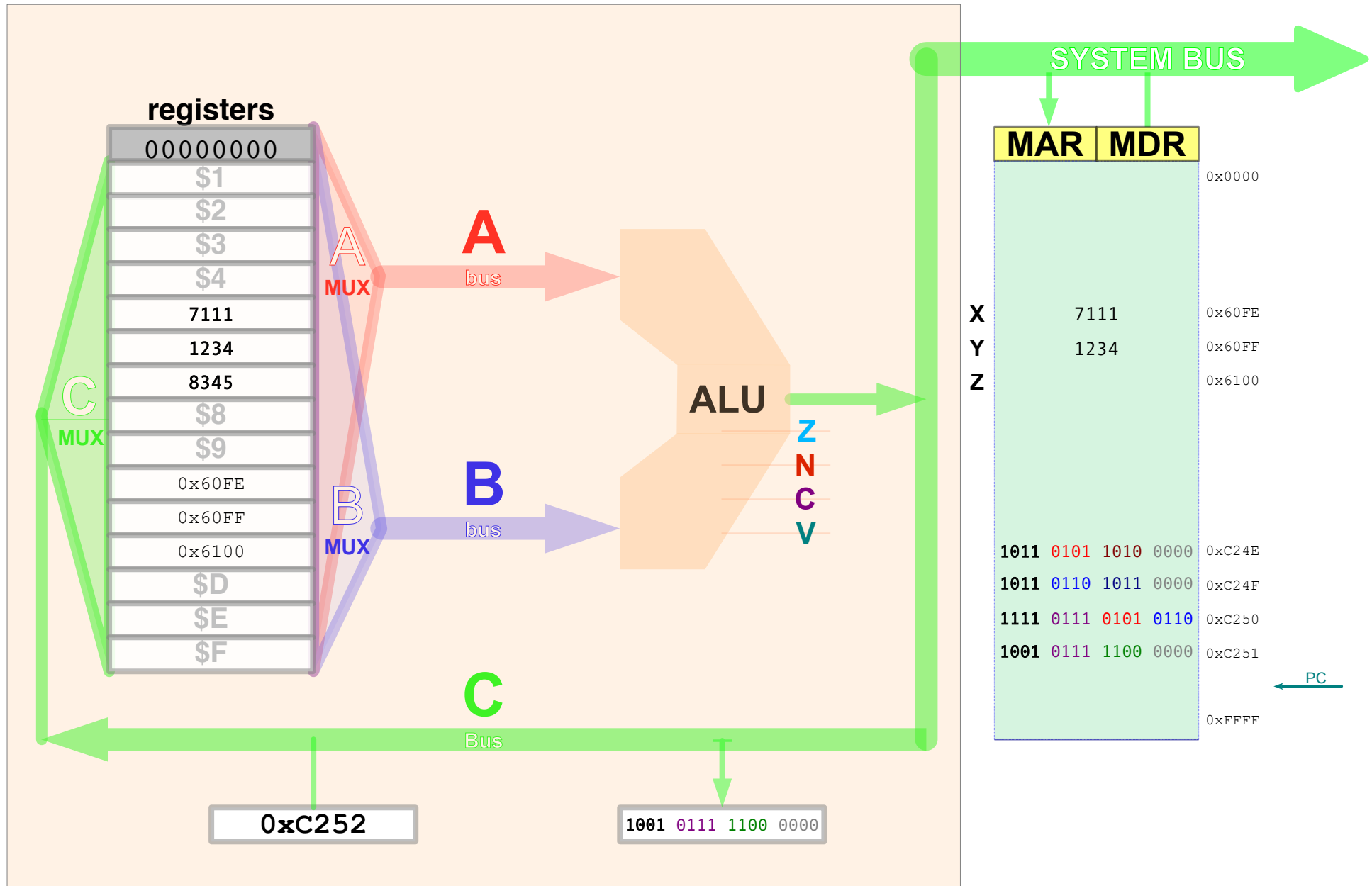


execute

# The T<sub>OY</sub> Computer



**fetch**

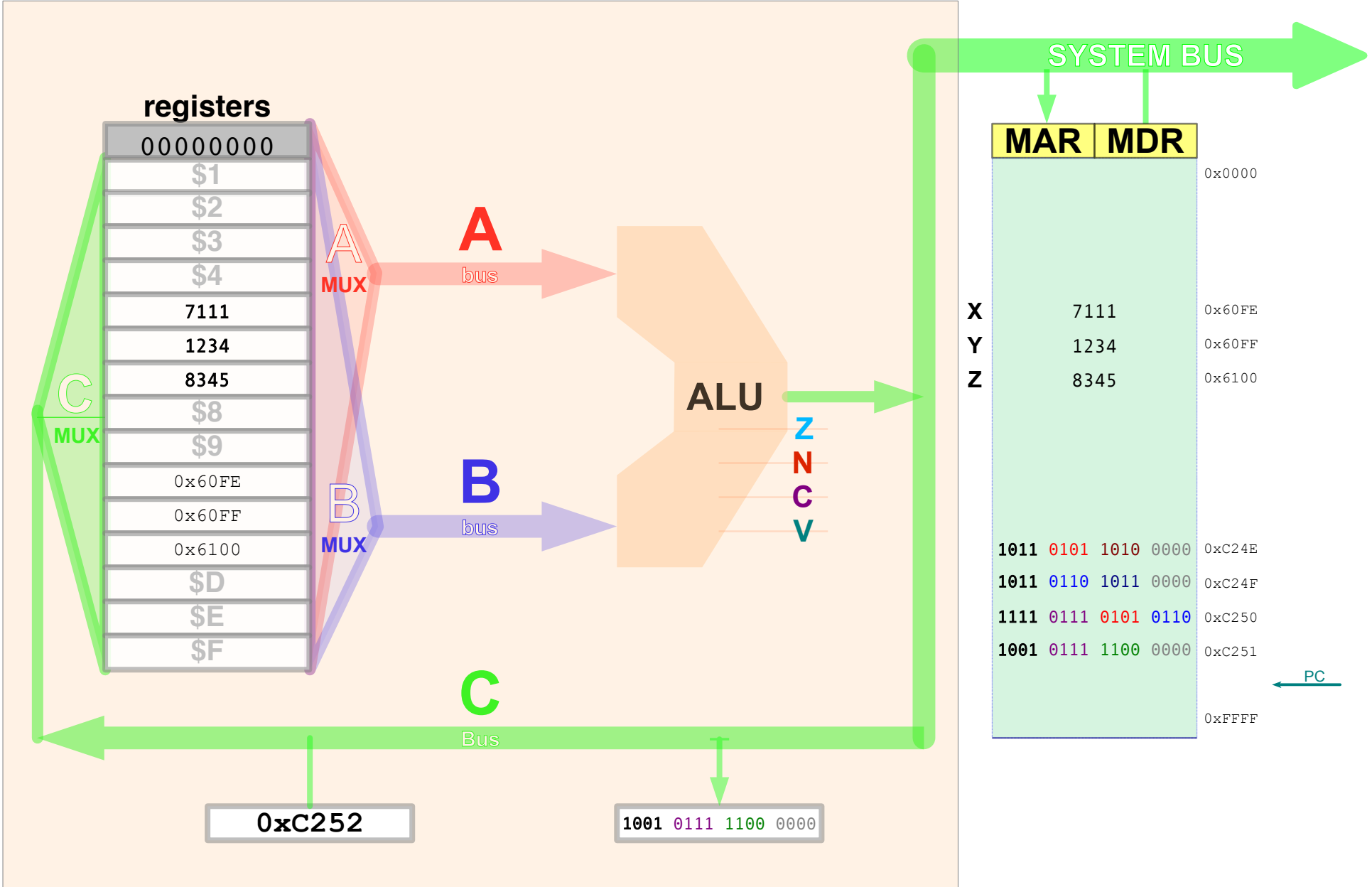

# HW 7: $\mathbf{W} = \mathbf{X} + \mathbf{Y} + \mathbf{Z}$

Assignment: Write a **TOY** assembly language program to add the values of 3 variables, **X**, **Y**, and **Z**, in memory and store the sum in a fourth, **W**.

Details: The variables occupy consecutive words of memory starting with **W**. The address of **W** is in register **\$3**. Register **\$4** contains the constant **1**. *Do not change* the values in registers **\$0** through **\$4**. You can use registers **\$5** through **\$F** as you please. Your program should consist entirely of addition (**add**), load (**l**), and store (**st**) instructions.

Hint: You will need to construct the addresses of variables **X**, **Y**, and **Z** in a register or in registers. There are various ways to accomplish this.



$$7 + B = ?$$

+

0 1 1 1


1 0 1 1

0

$$7 + B \neq 2$$

+				
	0 1 1 1			
	1 0 1 1			
	<hr/>			
	1	1	1	0
				0 0 1 0

Carry out  
incorrect!

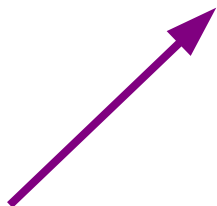

$$7 - B = ?$$

		0	1	1	1
		1	0	1	1
-					

$$7 - B = ?$$

		0	1	1	1
		<u>1</u>	<u>0</u>	<u>1</u>	<u>1</u>
+					1

$$7 - B = ?$$

+

0 1 1 1

0 1 0 0

1

$$7 - B \neq C$$

+		0	1	1	1
		0	1	0	0
	0	1	1	1	1
		1	1	0	0

no carry  
incorrect!

$$7 - B = C - 2^4 = -4$$

		0	1	1	1
		0	1	0	0
+	0	1	1	1	1
		1	1	0	0

$$\mathbf{A - C + 3 = A + 3 - C}$$

$$\mathbf{A - C + 3}$$

$$= 1010 - 1100 + 0011$$

$$= 1010 + 0100 + 0011$$

$$= \quad \quad 1110 + 0011$$

$$= \quad \quad \quad 0001$$

$$\mathbf{A + 3 - C}$$

$$= 1010 + 0011 - 1100$$

$$= \quad \quad 1101 - 1100$$

$$= \quad \quad 1101 + 0100$$

$$= \quad \quad \quad 0001$$



# Circuit Design Example: $n > 4$

Construct a circuit with Boolean inputs  $n_2$ ,  $n_1$ , and  $n_0$  that is 1 if, and only if,  $n \equiv n_2 \cdot 2^2 + n_1 \cdot 2^1 + n_0 \cdot 2^0 > 4$ .

$n_2$	$n_1$	$n_0$	$n$	$n > 4$
0	0	0	0	0
0	0	1	1	0
0	1	0	2	0
0	1	1	3	0
1	0	0	4	0
1	0	1	5	1
1	1	0	6	1
1	1	1	7	1

# Circuit Design Example: $n > 4$

Construct a circuit with Boolean inputs  $n_2$ ,  $n_1$ , and  $n_0$  that is 1 if, and only if,  $n \equiv n_2 \cdot 2^2 + n_1 \cdot 2^1 + n_0 \cdot 2^0 > 4$ .

$n_2$	$n_1$	$n_0$	$n$	$n > 4$
0	0	0	0	0
0	0	1	1	0
0	1	0	2	0
0	1	1	3	0
1	0	0	4	0
1	0	1	5	1
1	1	0	6	1
1	1	1	7	1


$$n_2 \bar{n}_1 n_0 + n_2 n_1 \bar{n}_0 + n_2 n_1 n_0$$

# Circuit Design Example: $n > 4$


Construct a circuit with Boolean inputs  $n_2$ ,  $n_1$ , and  $n_0$  that is 1 if, and only if,  $n \equiv n_2 \cdot 2^2 + n_1 \cdot 2^1 + n_0 \cdot 2^0 > 4$ .

$n_2$	$n_1$	$n_0$	$n$	$n > 4$
0	0	0	0	0
0	0	1	1	0
0	1	0	2	0
0	1	1	3	0
1	0	0	4	0
1	0	1	5	1
1	1	0	6	1
1	1	1	7	1

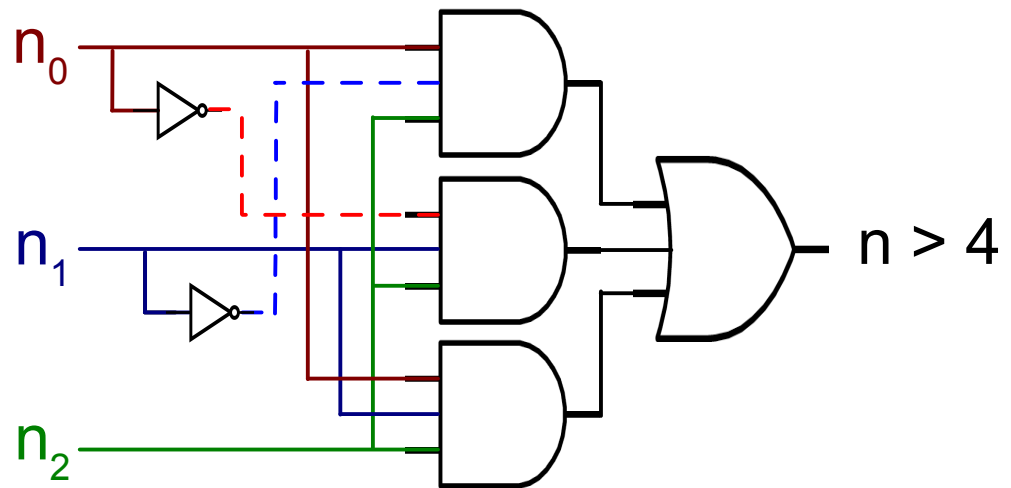
$$n_2 \bar{n}_1 n_0 + n_2 n_1 \bar{n}_0 + n_2 n_1 n_0$$


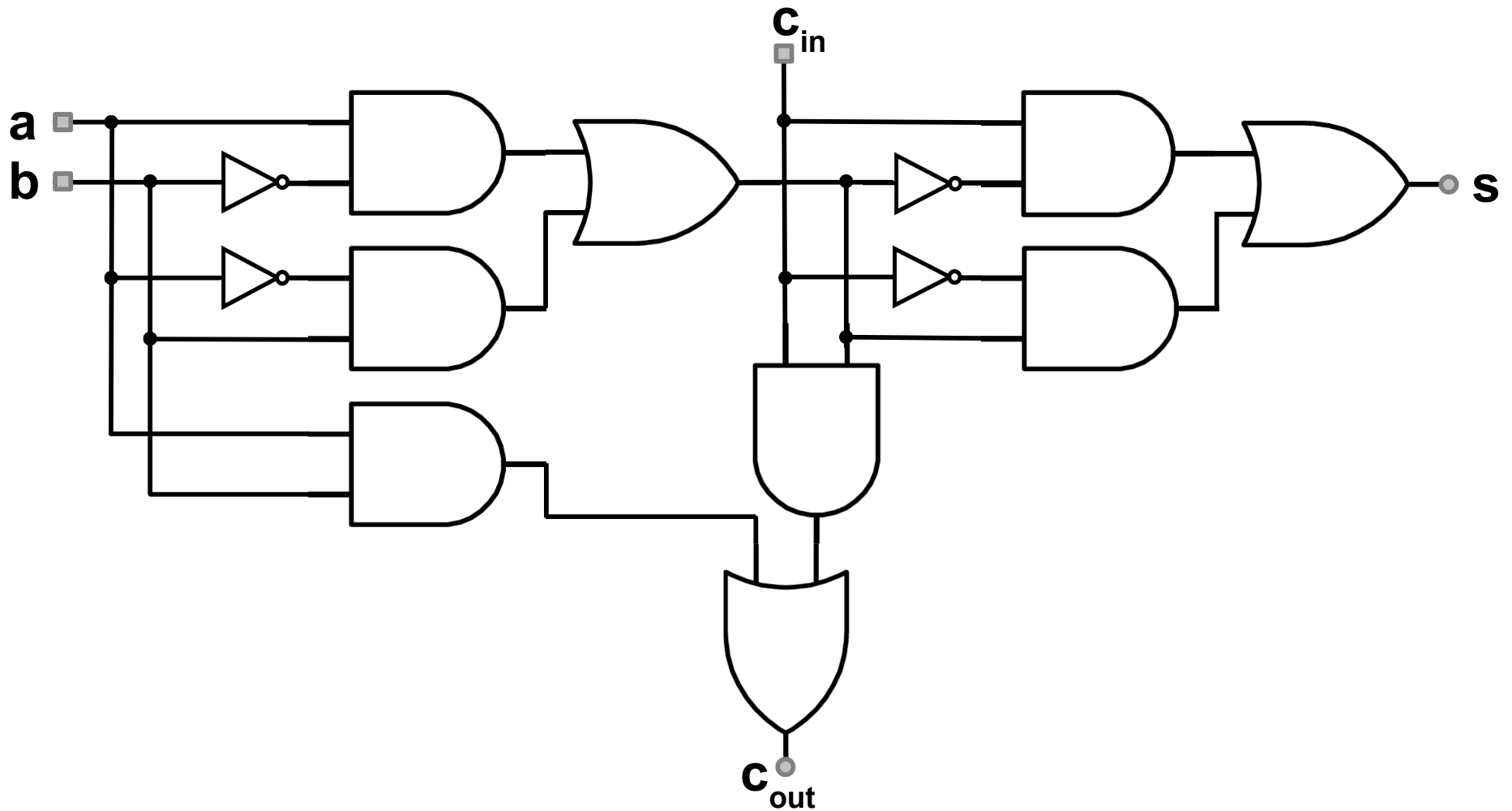
# Combinational Circuit $\rightarrow$ Boolean Formula



# Assign a Variable for each Gate

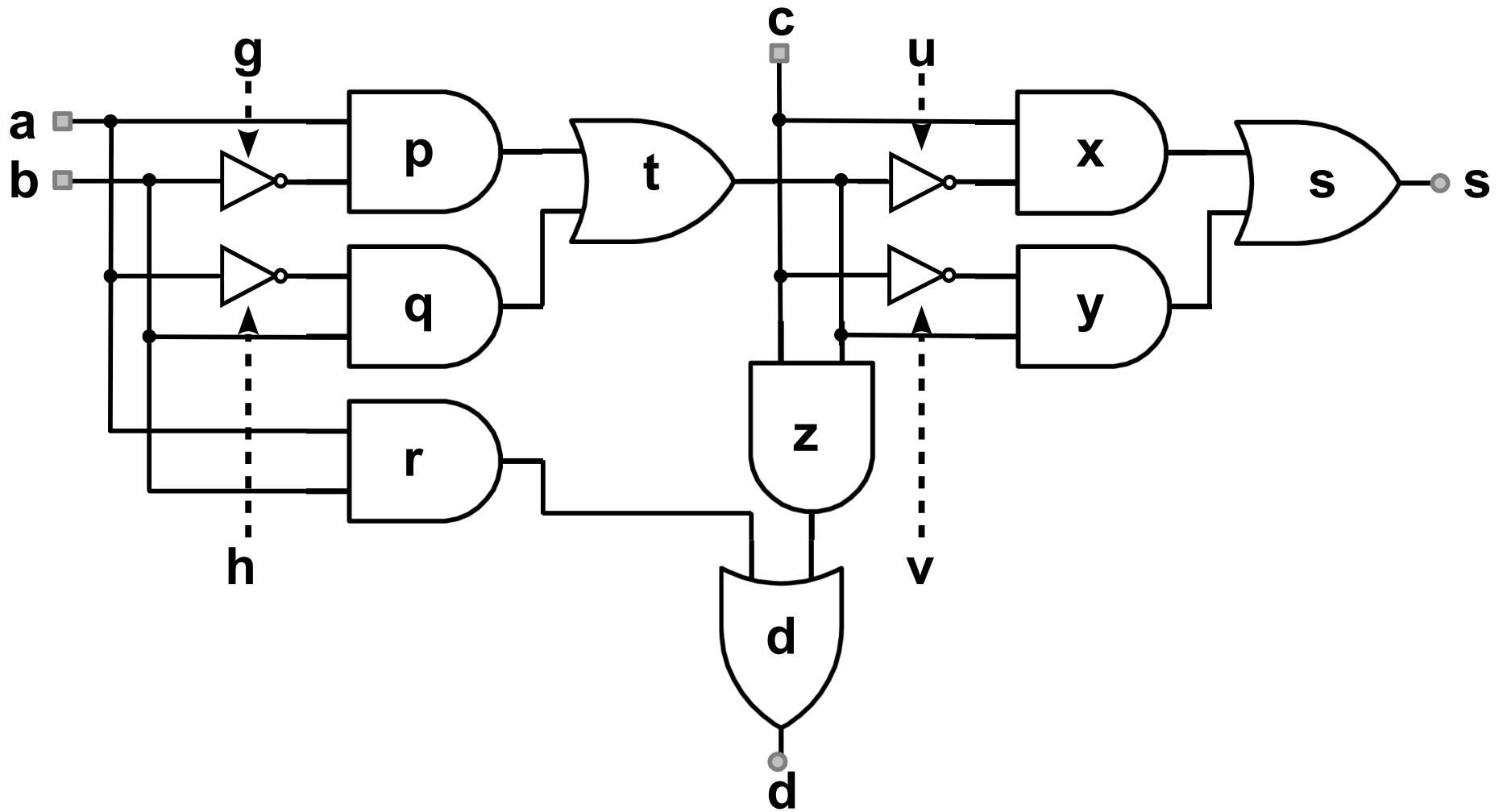


# Circuit $\rightarrow$ Formula

$$s = x + y$$

$$x = uc$$

$$y = tv$$

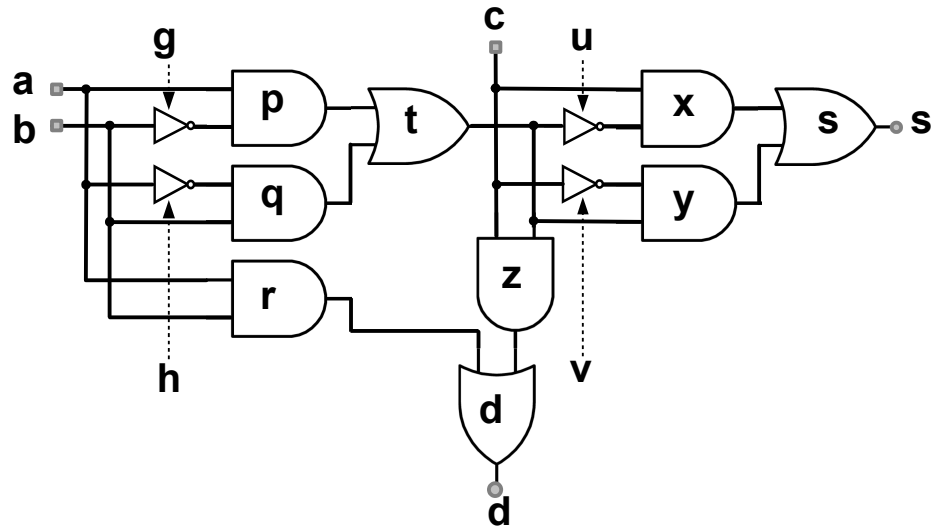

# Circuit $\rightarrow$ Formula

$$s = x + y$$

$$x = uc$$

$$y = tv$$

$$u = \bar{t}$$

$$v = \bar{c}$$


$$t = p + q$$

$$p = ag$$

$$q = hb$$

$$g = \bar{b}$$

$$h = \bar{a}$$

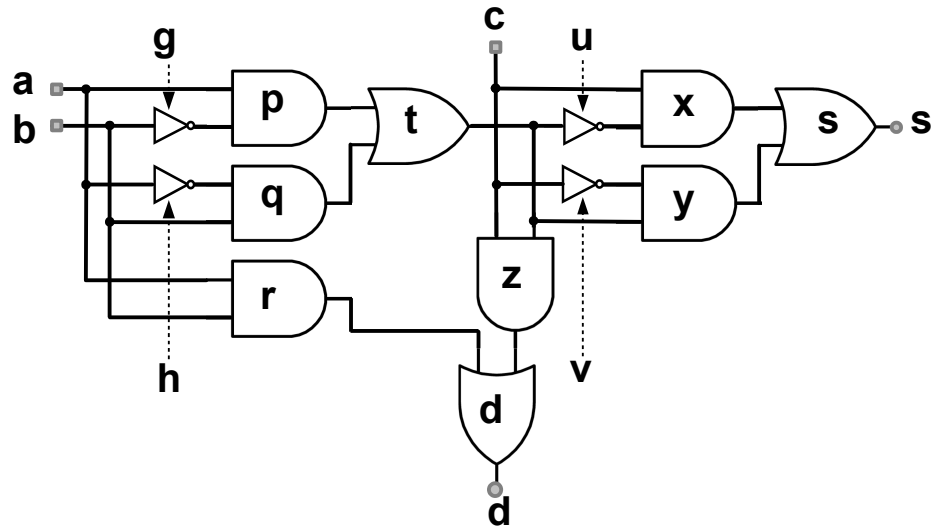

# Circuit $\rightarrow$ Formula

$$s = x + y$$

$$x = uc$$

$$y = tv$$

$$u = \bar{t}$$

$$v = \bar{c}$$

$$t = p + q$$

$$p = ag$$

$$q = hb$$

$$g = \bar{b}$$

$$h = \bar{a}$$


$$t = a\bar{b} + \bar{a}b$$

$$s = t\bar{c} + \bar{t}c$$

$$= a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{t}c$$

$$= a\bar{b}\bar{c} + \bar{a}b\bar{c} +$$

$$\sim(a\bar{b} + \bar{a}b) \cdot c$$

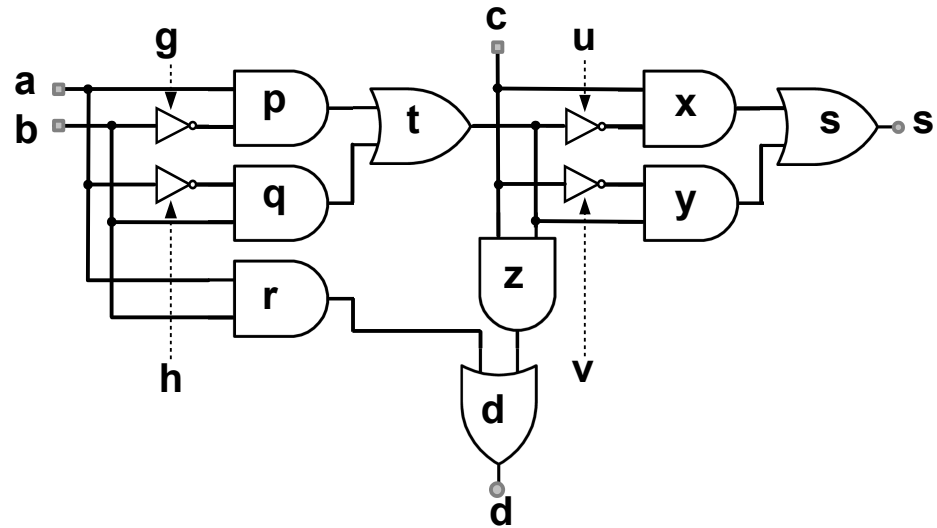



# Boolean Formula $\rightarrow$ Circuit

$$s = \overline{a}bc + a\overline{b}c + \sim(a\overline{b} + \overline{a}b) \cdot c$$

$$\overline{a}bc + a\overline{b}c + \sim(a\overline{b} + \overline{a}b) \cdot c \longrightarrow \textcircled{x1} \quad s$$


# Boolean Formula $\rightarrow$ Circuit

$$s = \overline{a}\overline{b}c + \overline{a}b\overline{c} + \sim(a\overline{b} + \overline{a}b) \cdot c$$



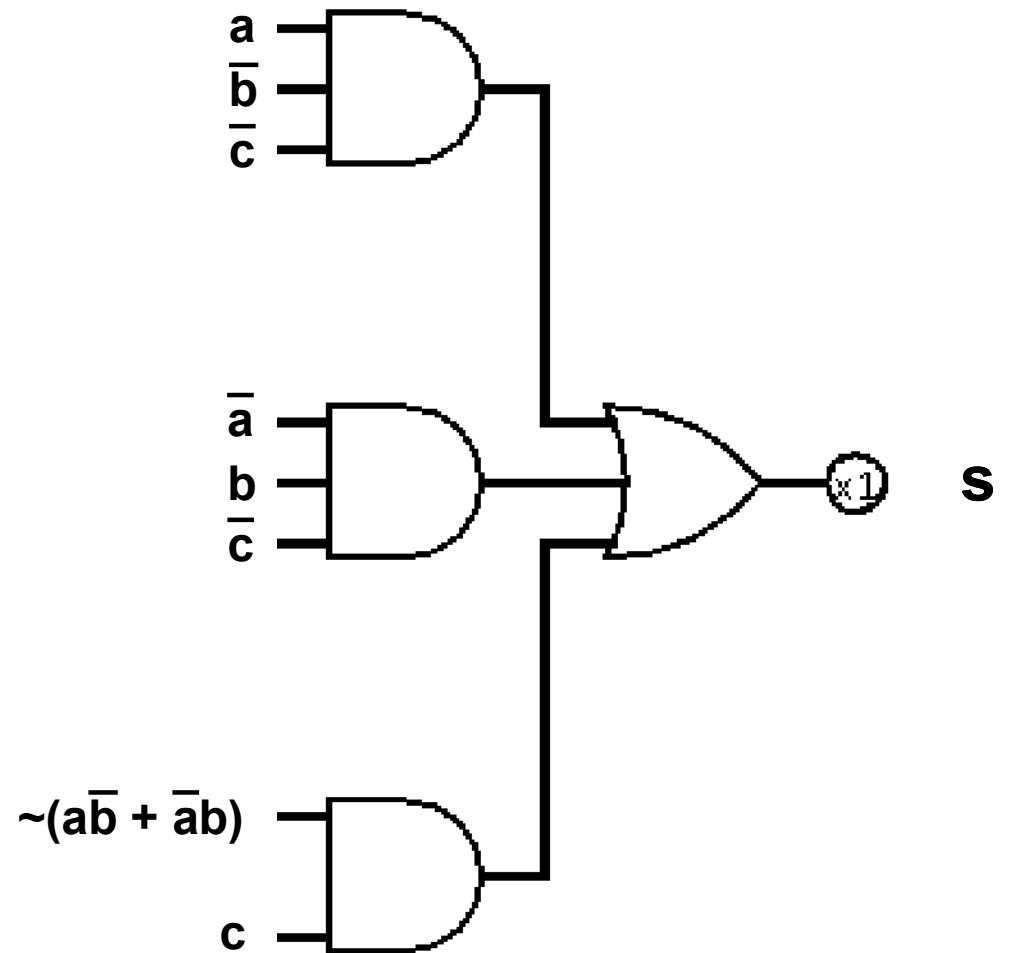
# Boolean Formula $\rightarrow$ Circuit

$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \sim(a\bar{b} + \bar{a}b) \cdot c$$



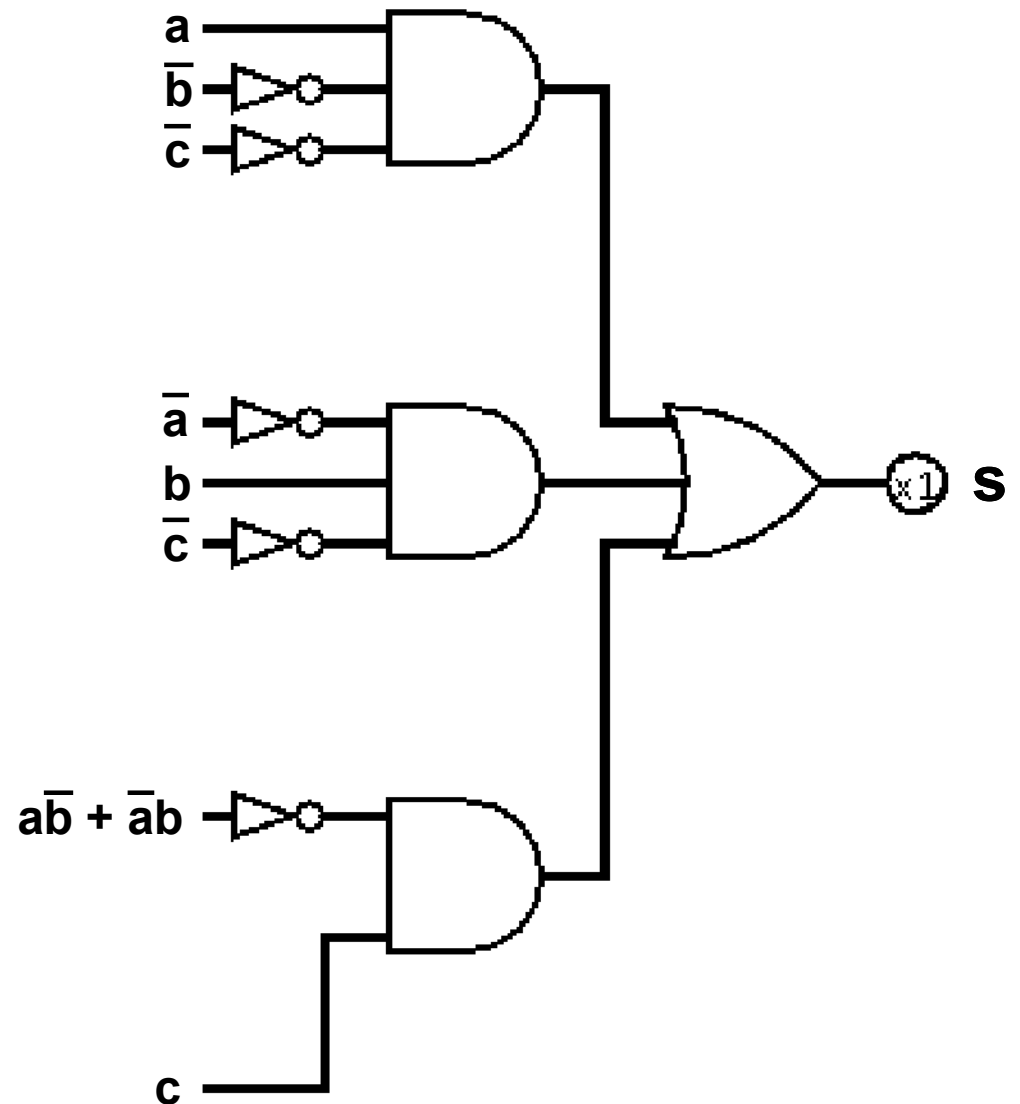
# Boolean Formula $\rightarrow$ Circuit

$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \sim(a\bar{b} + \bar{a}b) \cdot c$$



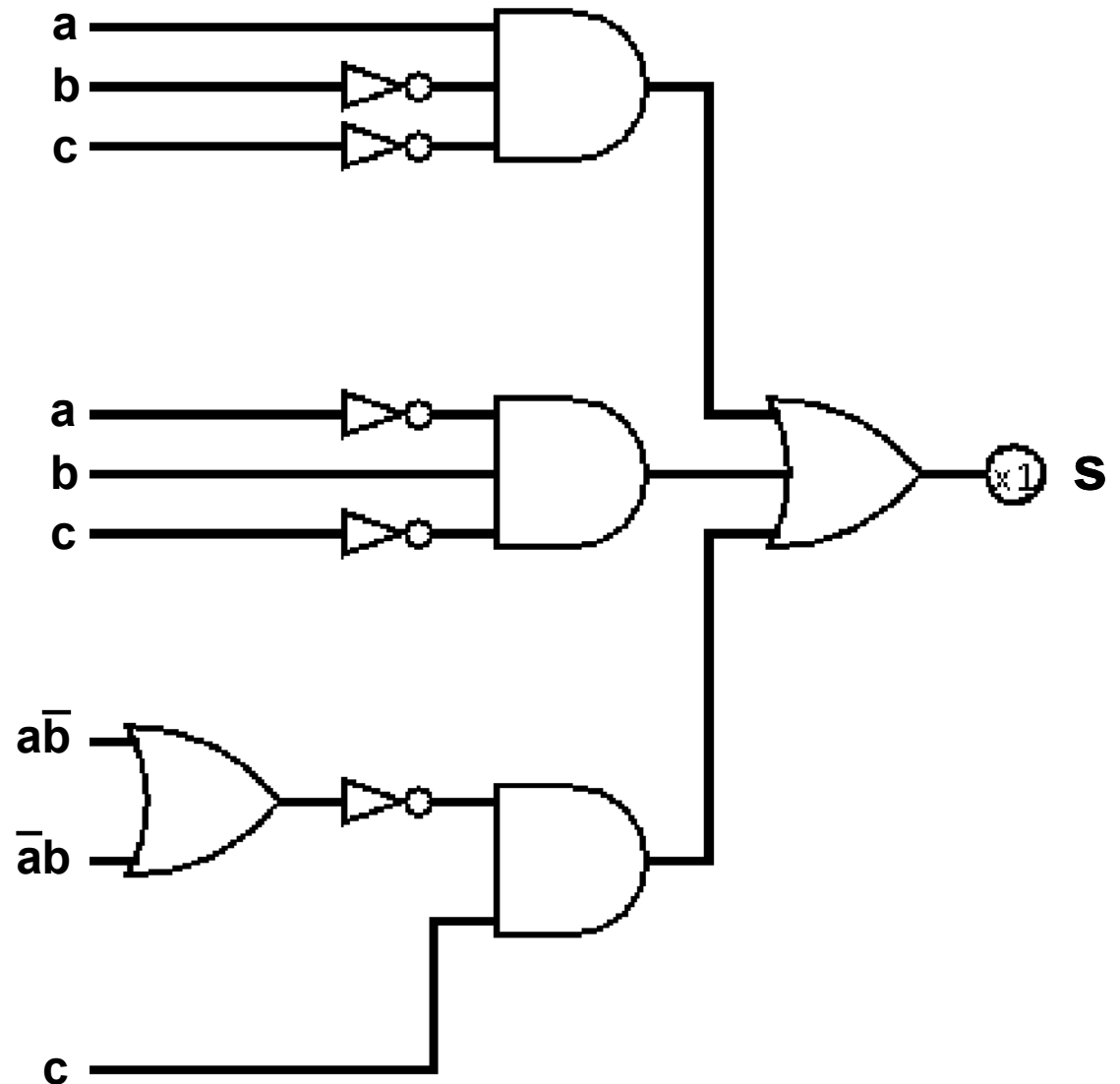
# Boolean Formula $\rightarrow$ Circuit

$$s = \overline{a}\overline{b}c + \overline{a}b\overline{c} + \sim(a\overline{b} + \overline{a}b) \cdot c$$



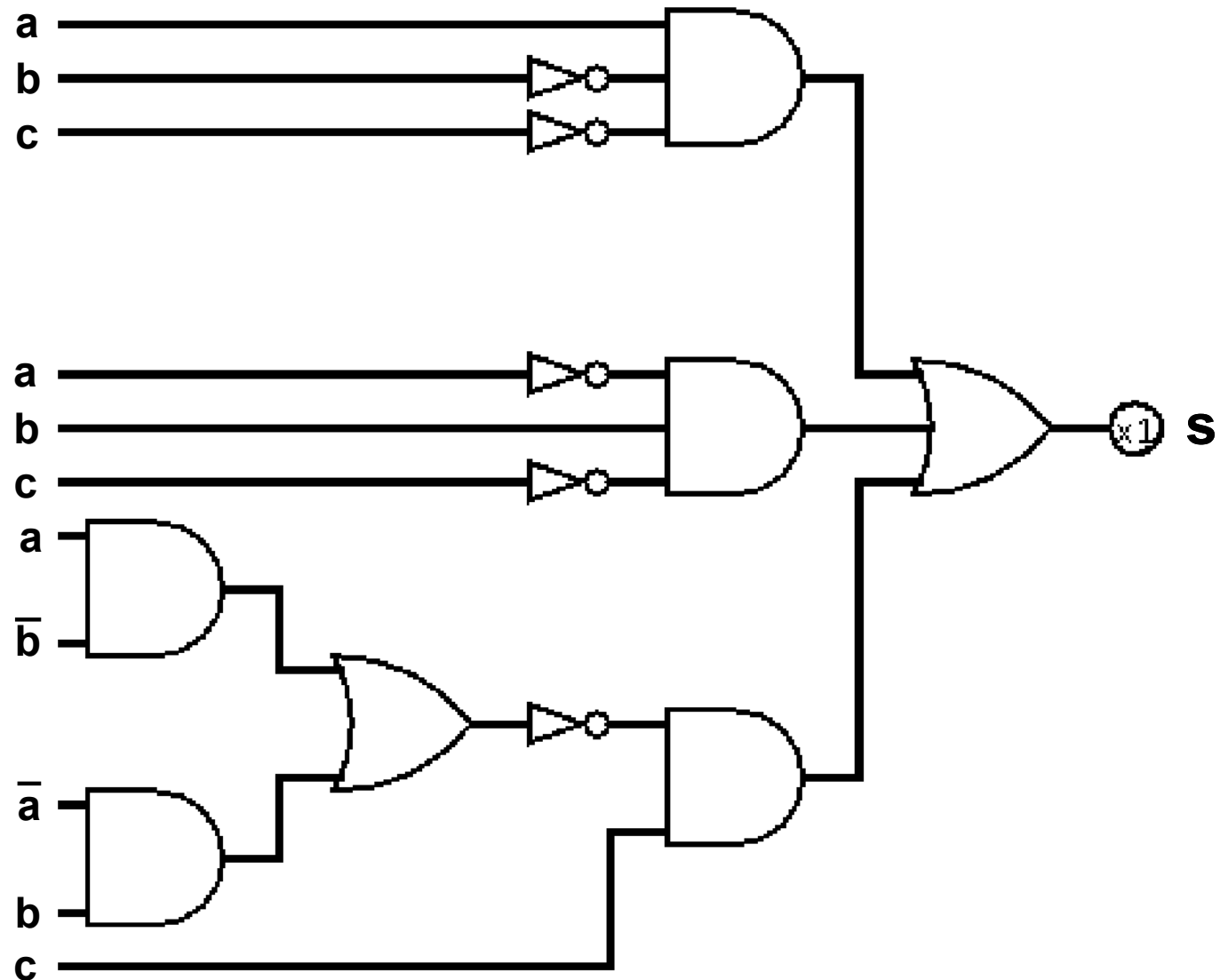
# Boolean Formula $\rightarrow$ Circuit

$$s = \overline{a}\overline{b}c + \overline{a}b\overline{c} + \sim(a\overline{b} + \overline{a}b) \cdot c$$



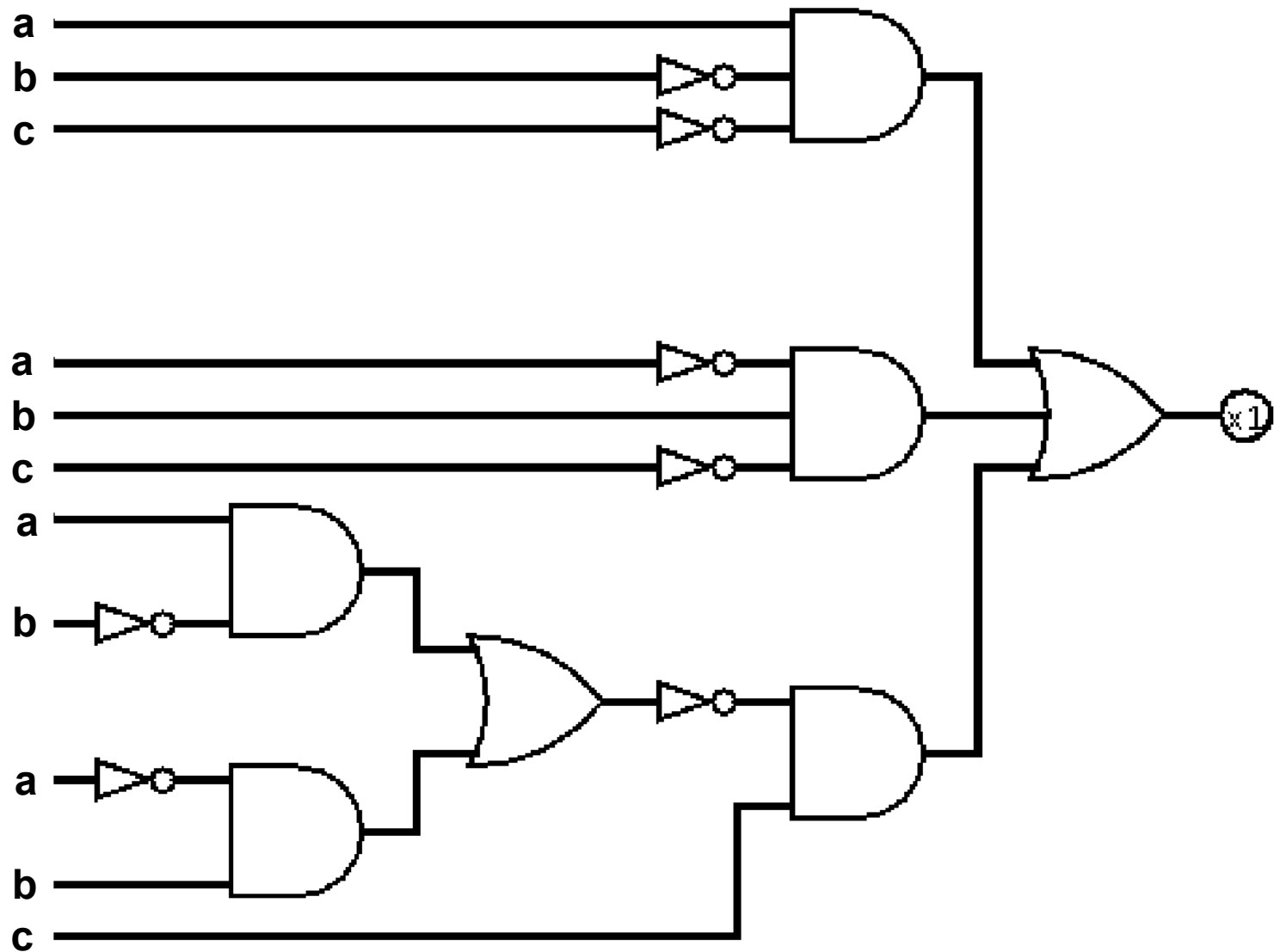
# Boolean Formula $\rightarrow$ Circuit

$$s = \overline{a}\overline{b}c + \overline{a}b\overline{c} + \sim(\overline{a}\overline{b} + \overline{a}b) \cdot c$$


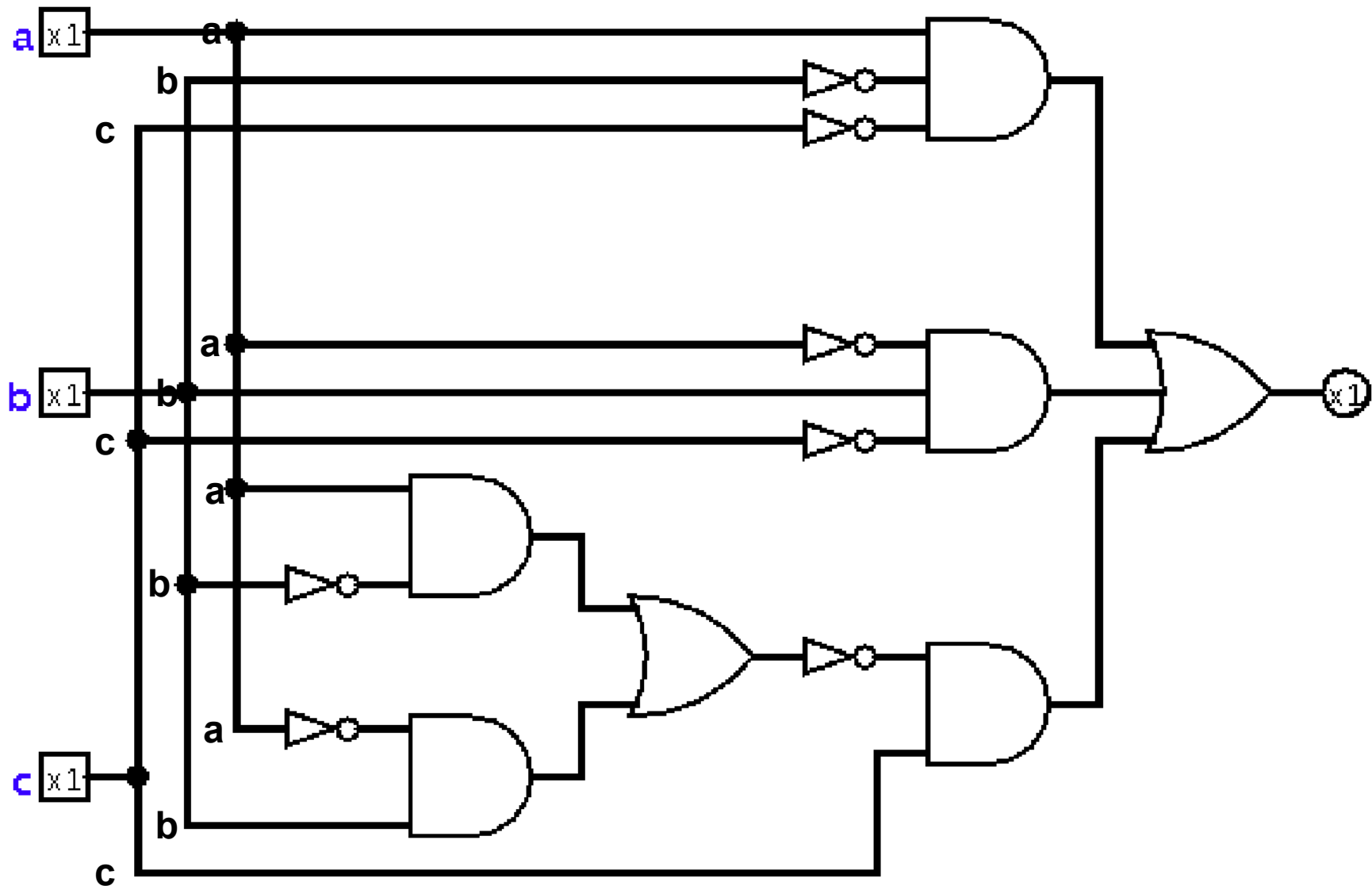
# Boolean Formula $\rightarrow$ Circuit

$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \sim(a\bar{b} + \bar{a}b) \cdot c$$





# Boolean Formula $\rightarrow$ Truth Table

$$s = \overline{a}bc + a\overline{b}c + \sim(a\overline{b} + \overline{a}b) \cdot c$$

[illegible]

# Formula Simplification

$$s = x + y$$

$$x = uc$$

$$y = tv$$

$$u = \bar{t}$$

$$v = \bar{c}$$

$$t = p + q$$

$$p = ag$$

$$q = hb$$

$$g = \bar{b}$$

$$h = \bar{a}$$


$$t = a\bar{b} + \bar{a}b$$

$$s = t\bar{c} + \bar{t}c$$

$$= a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{t}c$$

$$= a\bar{b}\bar{c} + \bar{a}b\bar{c} +$$

$$\sim(a\bar{b} + \bar{a}b) \cdot c$$

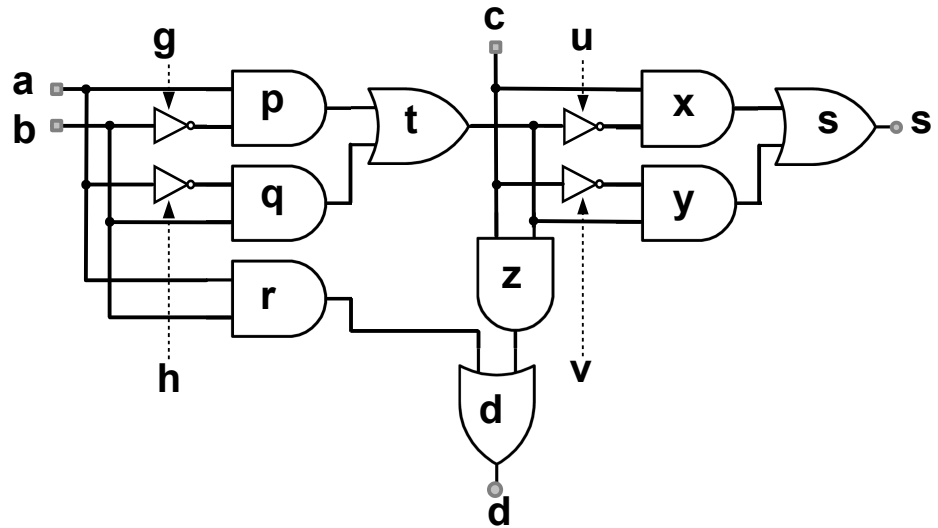

# Formula Simplification

$$s = x + y$$

$$x = uc$$

$$y = tv$$

$$u = \bar{t}$$

$$v = \bar{c}$$

$$t = p + q$$

$$p = ag$$

$$q = hb$$

$$g = \bar{b}$$


$$h = \bar{a}$$

$$t = a\bar{b} + \bar{a}b$$

$$s = t\bar{c} + \bar{t}c$$

$$= a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{t}c$$
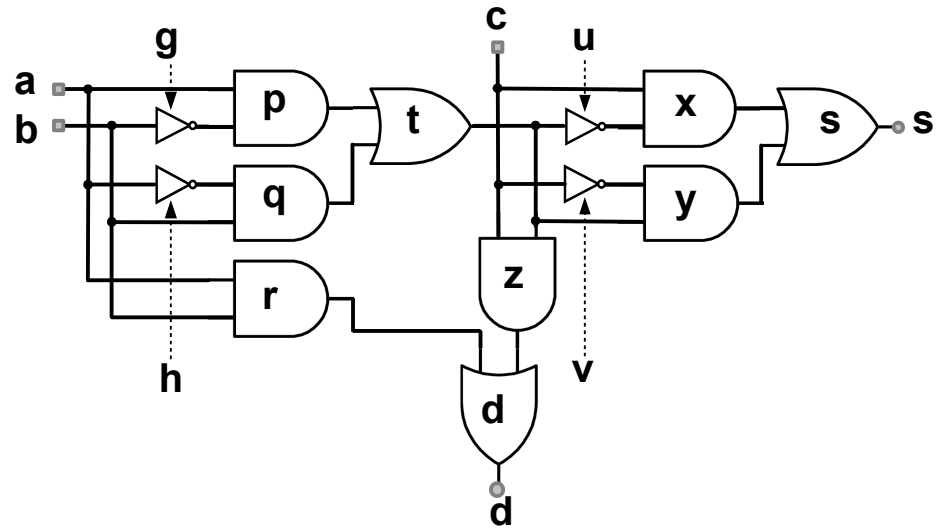
$$= a\bar{b}\bar{c} + \bar{a}b\bar{c} +$$



$$\begin{aligned} \bar{t}c &= \sim(a\bar{b} + \bar{a}b) \cdot c \\ &= \sim(a\bar{b}) \cdot \sim(\bar{a}b) \cdot c \\ &= (\bar{a} + b) \cdot (a + \bar{b}) \cdot c \\ &= \bar{a}ac + \bar{a}\bar{b}c + bac + b\bar{b}c \\ &= \bar{a}\bar{b}c + bac \\ &= abc + \bar{a}\bar{b}c \end{aligned}$$

# Truth Table $\rightarrow$ Boolean Formula

$$s = \overline{a}bc + a\overline{b}c + abc + a\overline{b}\overline{c}$$

[illegible]

# Boolean Formula Parse Tree

$$X = \bar{S}A + SB$$

